

Analog Electronics


Shishir Mallick

Lecturer

Dept. of CSE

Bangladesh University

Inverting Amplifier

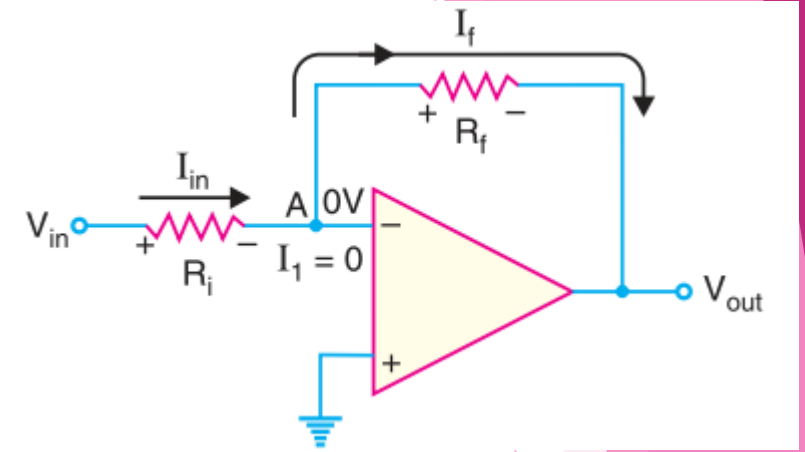

$$I_{in} = \frac{\text{Voltage across } R_i}{R_i} = \frac{V_{in} - V_A}{R_i} = \frac{V_{in} - 0}{R_i} = \frac{V_{in}}{R_i}$$


$$I_f = \frac{\text{Voltage across } R_f}{R_f} = \frac{V_A - V_{out}}{R_f} = \frac{0 - V_{out}}{R_f} = \frac{-V_{out}}{R_f}$$

$$\text{Since } I_f = I_{in}, \quad -\frac{V_{out}}{R_f} = \frac{V_{in}}{R_i}$$


$$\text{Voltage gain, } A_{CL} = \frac{V_{out}}{V_{in}} = -\frac{R_f}{R_i}$$

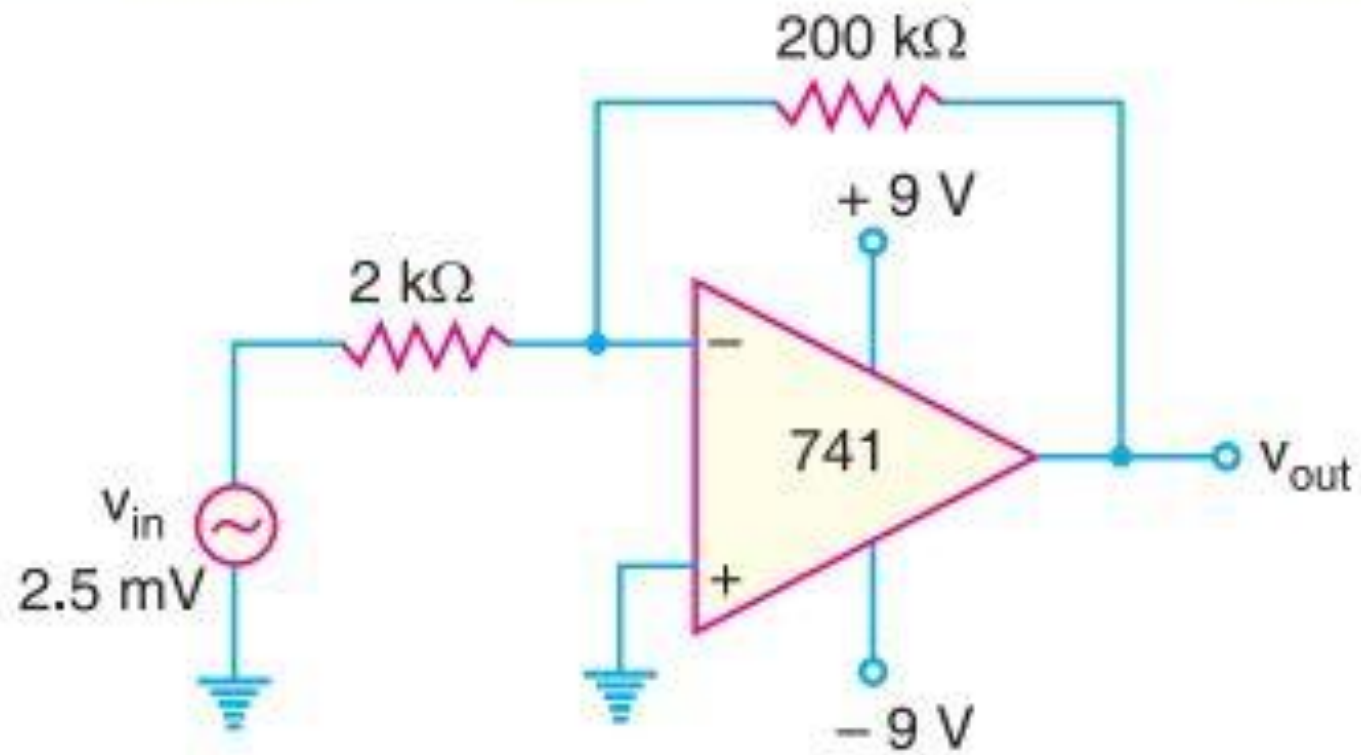Problem 16.1

Determine the output voltage for the circuit of Fig. 25.50.



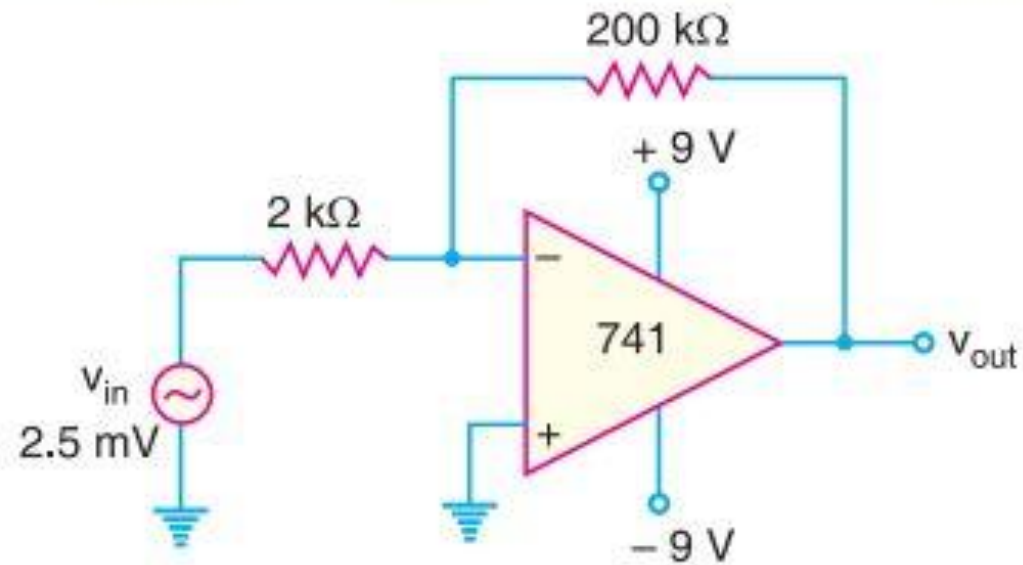Determine the output voltage for the circuit of Fig. 25.50.



$$A_{CL} = -\frac{R_f}{R_i} = -\frac{200\text{ k}\Omega}{2\text{ k}\Omega} = -100$$

$$\text{Output voltage, } v_{out} = A_{CL} \times v_{in} = (-100) \times (2.5\text{ mV}) = -250\text{ mV} = \mathbf{-0.25\text{ V}}$$

Non-inverting Amplifier

Current through R_i = Current through R_f


$$\frac{V_{in} - 0}{R_i} = \frac{V_{out} - V_{in}}{R_f}$$

$$V_{in} R_f = V_{out} R_i - V_{in} R_i$$

$$V_{in} (R_f + R_i) = V_{out} R_i$$


$$\frac{V_{out}}{V_{in}} = \frac{R_f + R_i}{R_i} = 1 + \frac{R_f}{R_i}$$

Closed-loop voltage gain, $A_{CL} = \frac{V_{out}}{V_{in}} = 1 + \frac{R_f}{R_i}$

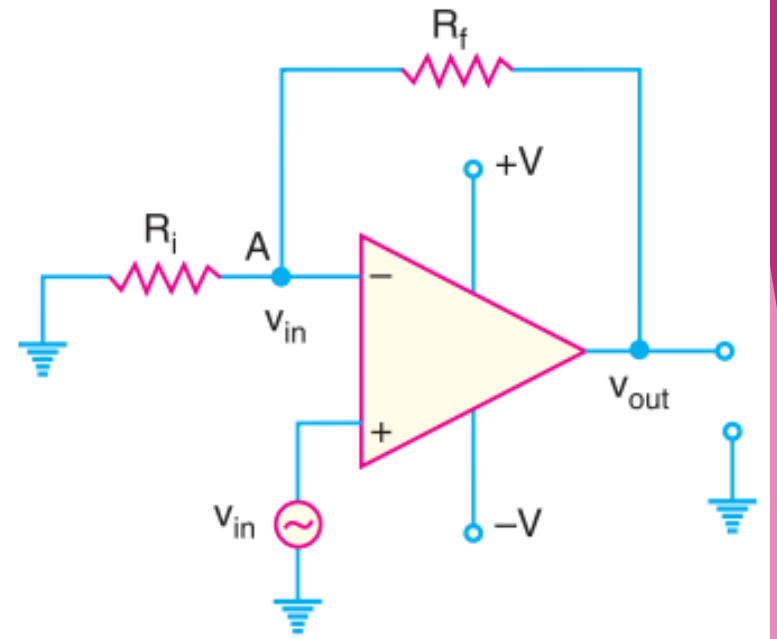


Problem 16.2

Example 25.32. Calculate the output voltage from the noninverting amplifier circuit shown in Fig. 25.57 for an input of $120\ \mu\text{V}$.

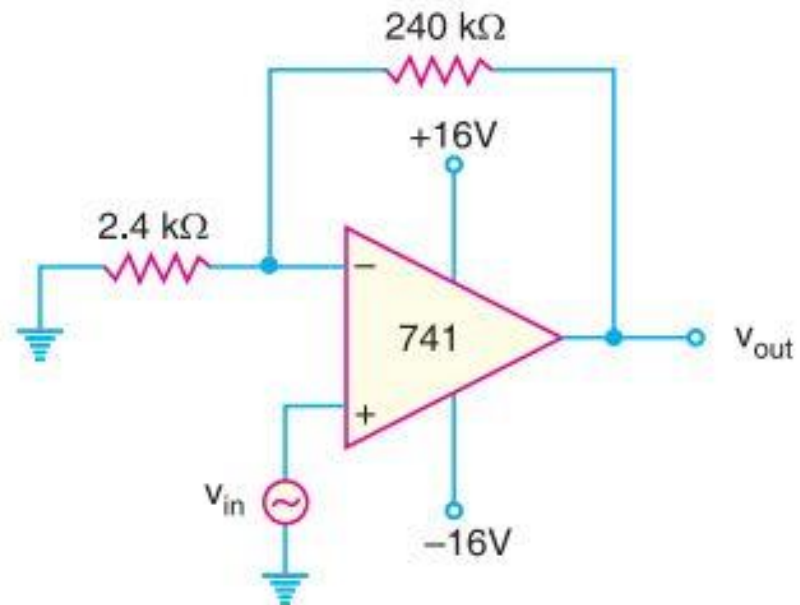

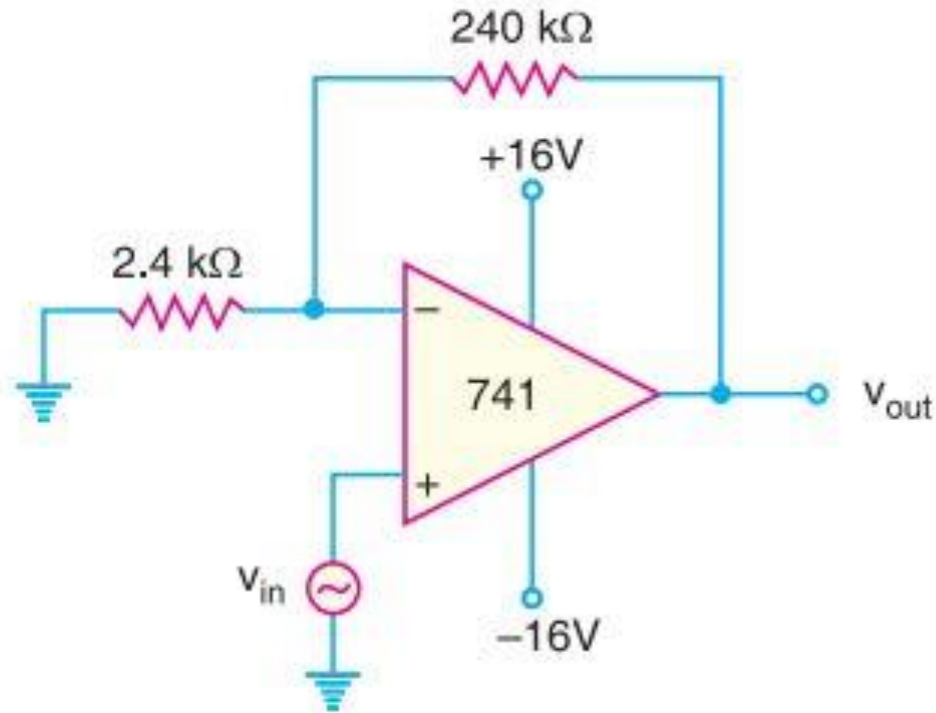
Example 25.32. Calculate the output voltage from the noninverting amplifier circuit shown in Fig. 25.57 for an input of $120\ \mu\text{V}$.



$$\text{Voltage gain, } A_{CL} = 1 + \frac{R_f}{R_i} = 1 + \frac{240\ \text{k}\Omega}{2.4\ \text{k}\Omega} = 1 + 100 = 101$$

$$\text{Output voltage, } v_{out} = A_{CL} \times v_{in} = (101) \times (120\ \mu\text{V}) = \mathbf{12.12\ \text{mV}}$$

Summing Amplifier

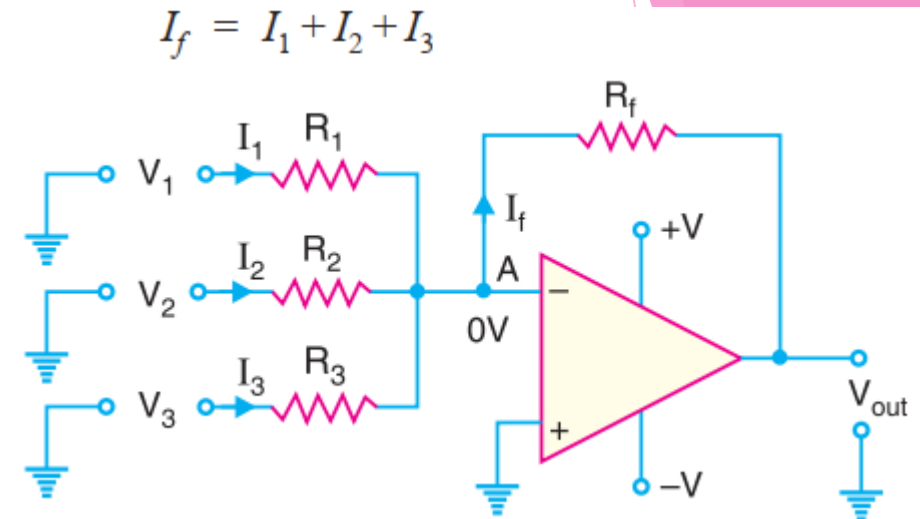

Output voltage, $V_{out} = -I_f R_f = -R_f(I_1 + I_2 + I_3)$

$$= -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$


$$\therefore V_{out} = -R_f \left(\frac{V_1}{R_1} + \frac{V_2}{R_2} + \frac{V_3}{R_3} \right)$$

If $R_1 = R_2 = R_3 = R$, then, we have,


$$V_{out} = -\frac{R_f}{R} (V_1 + V_2 + V_3)$$

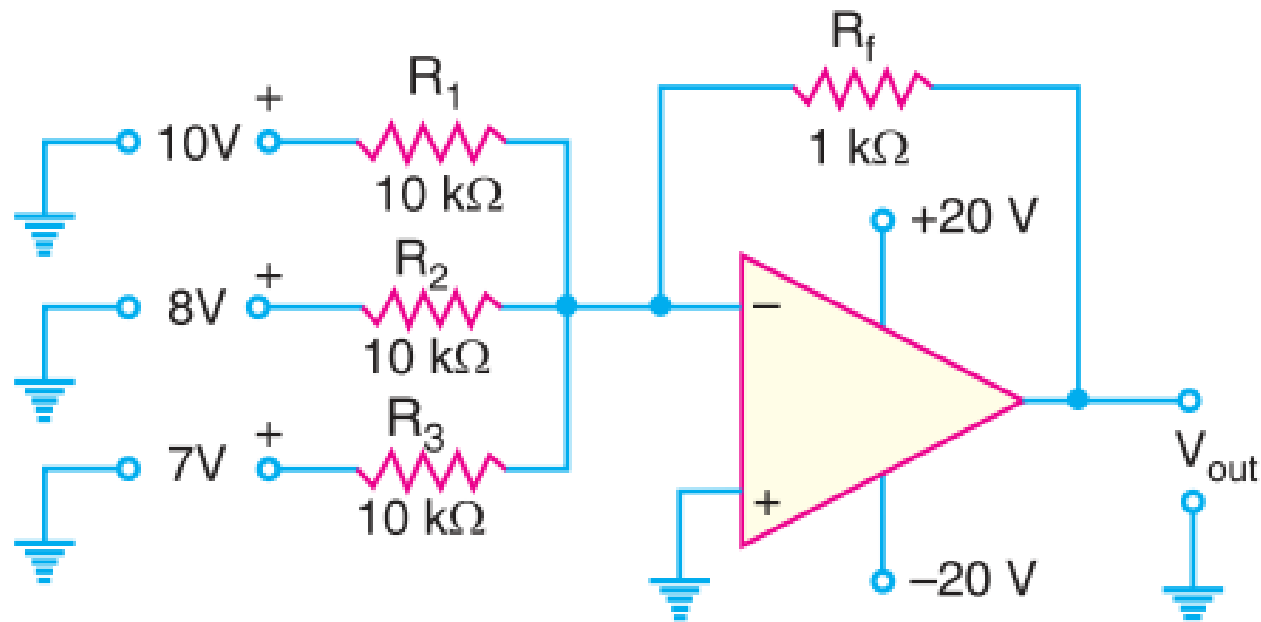Problem 16.3

Determine the output voltage for the summing amplifier shown



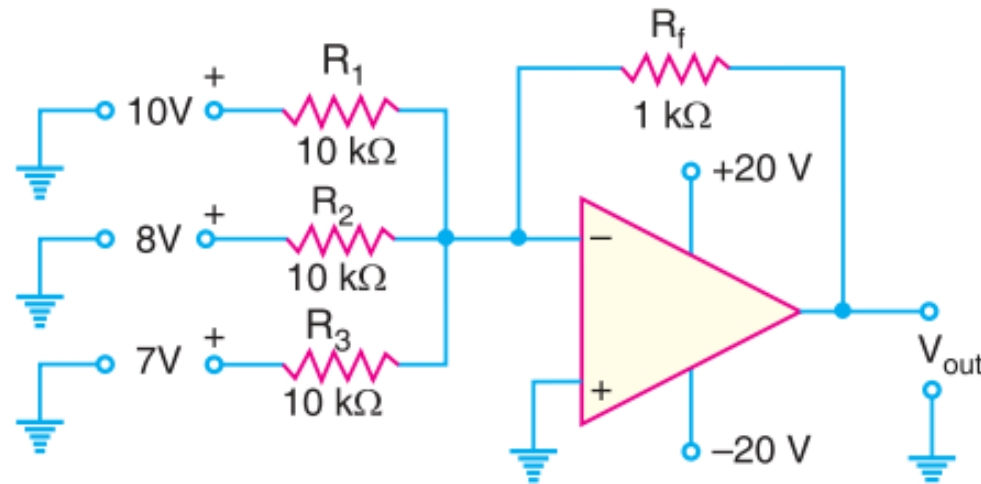Determine the output voltage for the summing amplifier shown




Solution. $R_f = 1\text{ k}\Omega$ and $R_1 = R_2 = R_3 = R = 10\text{ k}\Omega$. Therefore, gain of the amplifier $= -R_f/R = -1\text{ k}\Omega/10\text{ k}\Omega = -1/10$.

Now

$$V_{out} = -\frac{R_f}{R}(V_1 + V_2 + V_3) = -\frac{1\text{ k}\Omega}{10\text{ k}\Omega}(10 + 8 + 7) = -2.5\text{ V}$$

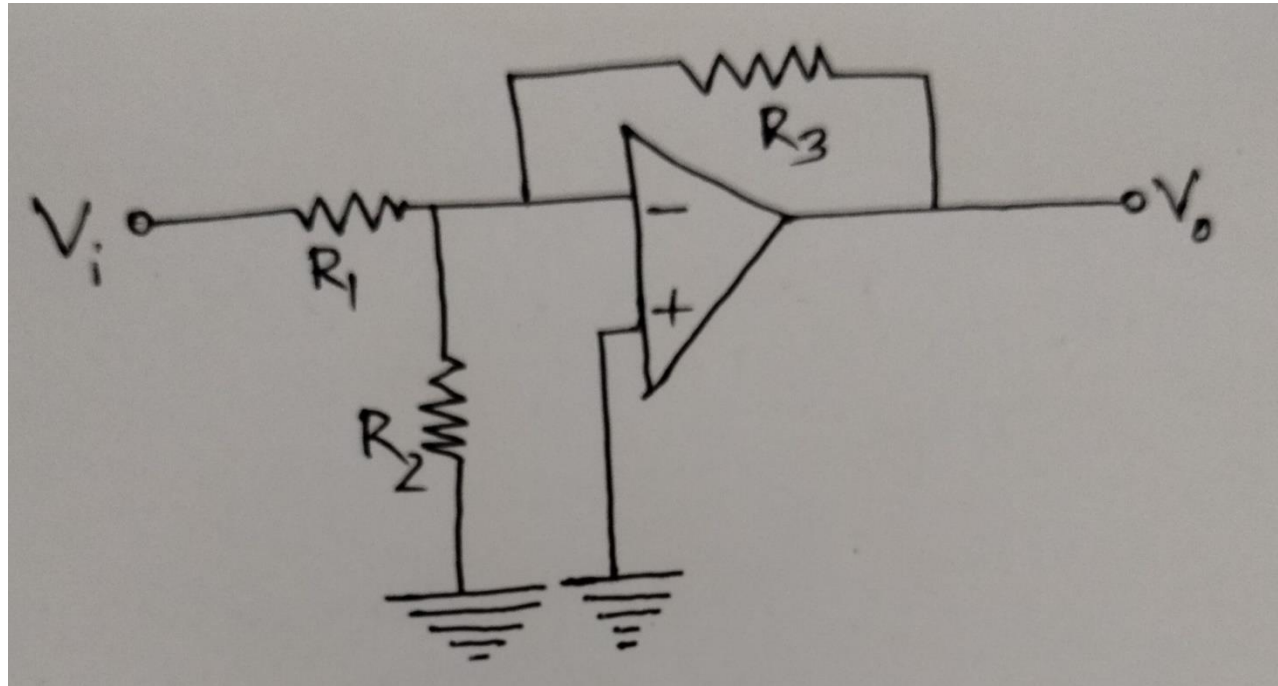Problem 16.4

For the following op amp circuit, find the voltage gain (v_o/v_i) where $R_1 = 10\text{ K}\Omega$, $R_2 = 10\text{ K}\Omega$ and $R_3 = 100\text{ K}\Omega$.



OP-Amp Integrator


$$i = i_c$$

Now

$$i = \frac{v_i - 0}{R} = \frac{v_i}{R}$$

Also voltage across capacitor is $v_c = 0 - v_o = -v_o$
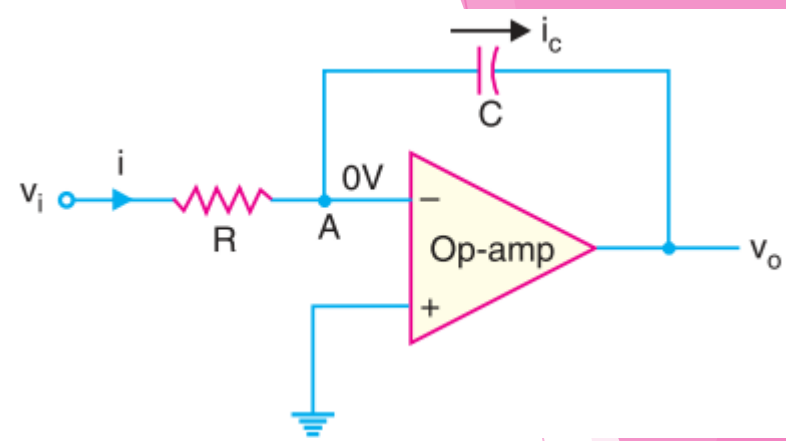
$$\therefore i_c = \frac{C dv_c}{dt} = -C \frac{dv_o}{dt}$$




From eqs. (i) and (ii),
$$\frac{v_i}{R} = -C \frac{dv_o}{dt}$$

or
$$\frac{dv_o}{dt} = -\frac{1}{RC} v_i$$

To find the output voltage, we integrate both sides of eq. (iii) to get,

$$v_o = -\frac{1}{RC} \int_0^t v_i dt$$

OP-Amp Differentiator

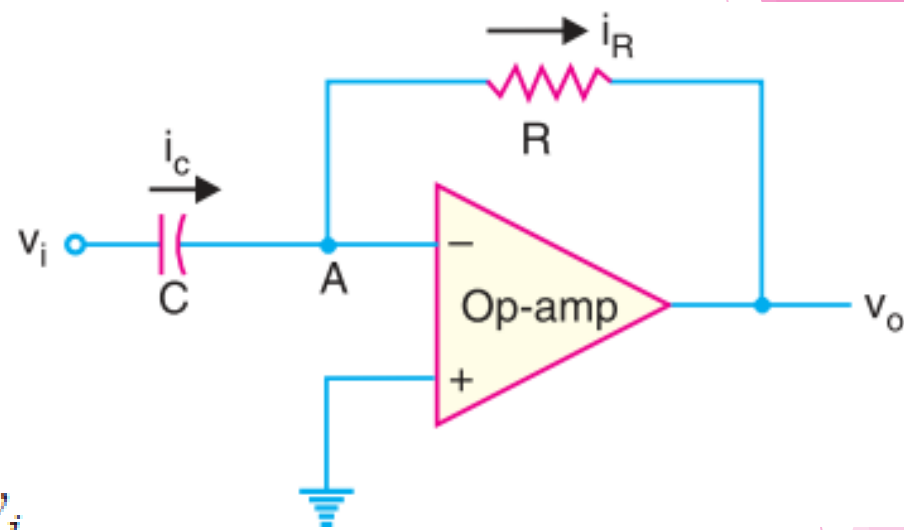

$$i_R = \frac{0 - v_o}{R} = -\frac{v_o}{R} \quad \text{and} \quad v_c = v_i - 0 = v_i$$

$$i_c = C \frac{dv_c}{dt} = C \frac{dv_i}{dt}$$

$$-\frac{v_o}{R} = C \frac{dv_i}{dt}$$

$$v_o = -RC \frac{dv_i}{dt}$$