

Analog Electronics

Shishir Mallick

Lecturer

Dept. of CSE

Bangladesh University

Operational Amplifier

An operational amplifier (OP-Amp) is a circuit that can perform such mathematical operations as addition, subtraction, integration and differentiation.

Properties of Operational Amplifier

- An operational amplifier is a multistage amplifier. The input stage of an *OP*-amp is a differential amplifier stage.
- An inverting input and a non-inverting input.
- A high input impedance at both inputs.
- A low output impedance ($< 200 \Omega$).
- A large open-loop voltage gain, typically 10^5 .
- The voltage gain remains constant over a wide frequency range.
- Very large *CMRR* ($> 90 \text{ dB}$).

Differential Amplifier (DA)

A differential amplifier is a circuit that can accept two input signals and amplify the difference between these two input signals.

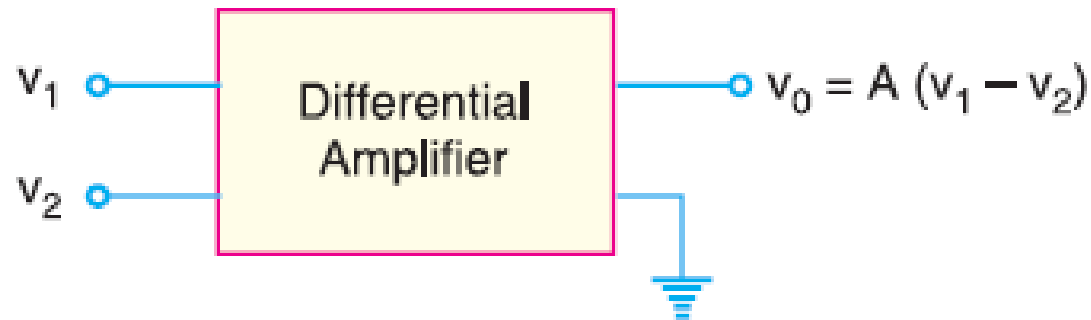


Fig. 4.1

Fig. 4.1 shows the block diagram of a differential amplifier. There are two input voltages v_1 and v_2 . This amplifier amplifies the difference between the two input voltages.

- Therefore, the output voltage is $V_0 = A(v_1 - v_2)$ where A is the voltage gain of the amplifier.

Differential Amplifier (DA)

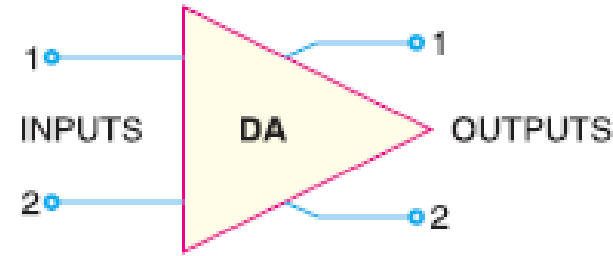
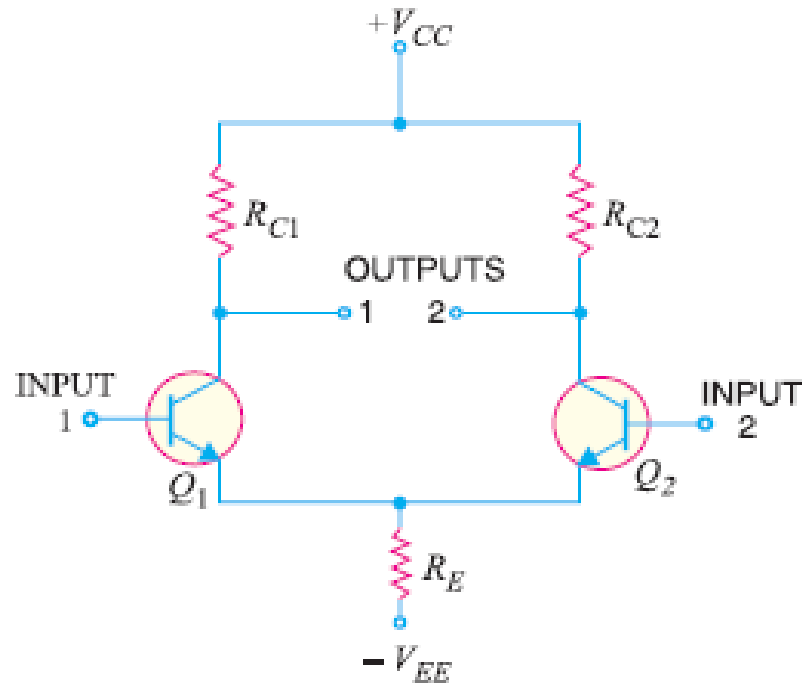


Fig 4.2 Basic circuit of a differential amplifier

- ▶ The differential amplifier (DA) is a two-input terminal device using at least two transistors.
- ▶ There are two output terminals marked 1 (v_{out1}) and 2 (v_{out2}).
- ▶ The DA transistors Q_1 and Q_2 are matched so that their characteristics are the same.
- ▶ The collector resistors (R_{C1} and R_{C2}) are also equal.
- ▶ The equality of the matched circuit components makes the DA circuit arrangement completely symmetrical.

Differential Amplifier (DA)

The DA transistors Q_1 and Q_2 are matched so that their characteristics are the same. The collector resistors (R_{C1} and R_{C2}) are also equal. The equality of the matched circuit components makes the DA circuit arrangement completely symmetrical.

We can apply signal to a differential amplifier (DA) in the following two ways :

- (a) The signal is applied to one input of DA and the other input is grounded. In that case, it is called *single-ended input* arrangement.
- (b) The signals are applied to both inputs of DA . In that case, it is called *dual-ended* or *double-ended input* arrangement.

We can take output from DA in the following two ways :


- (a) The output can be taken from one of the output terminals and the ground. In that case, it is called *single-ended output* arrangement.
- (b) The output can be taken between the two output terminals (*i.e.*, between the collectors of Q_1 and Q_2). In that case, it is called *double-ended output* arrangement or *differential output*.

Generally, the differential amplifier (DA) is operated for single-ended output. In other words, we take the output either from output terminal 1 and ground or from output terminal 2 and ground. Any input/output terminal that is grounded is at $0V$.


Differential Amplifier (DA)

Common-mode signals: When the input signals to a *DA* are in phase and exactly equal in amplitude, they are called *common-mode signals*.

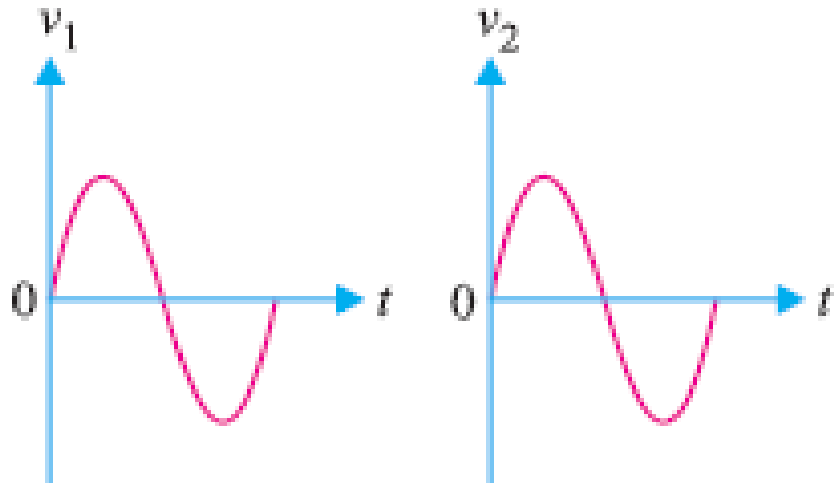Differential-mode signals. When the input signals to a *DA* are 180° out of phase and exactly equal in amplitude, they are called *differential-mode signals*.



Common-mode signals

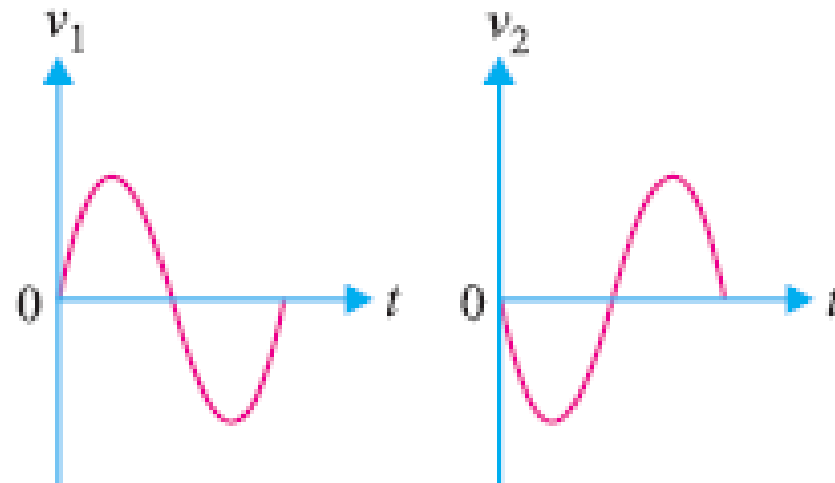

Differential-mode signals

Common-mode Rejection Ratio (CMRR)

A differential amplifier should have high differential voltage gain (A_{DM}) and very low common-mode voltage gain (A_{CM}). The ratio A_{DM}/A_{CM} is called common-mode rejection ratio (*CMRR*) *i.e.*,


$$CMRR = \frac{A_{DM}}{A_{CM}}$$

Very often, the *CMRR* is expressed in decibels (*dB*). The decibel measure for *CMRR* is given by;

$$CMRR_{dB} = 20\log_{10} \frac{A_{DM}}{A_{CM}} = 20\log_{10} CMRR$$

Common-mode Rejection Ratio (CMRR)


Importance of CMRR: The *CMRR* is the ability of a *DA* to reject the common-mode signals. The larger the *CMRR*, the better the *DA* is at eliminating common-mode signals. Common mode signals are usually *undesired signals* caused by external interference. For example, any *RF* signals picked up by the *DA* inputs would be considered undesirable. The *CMRR* indicates the *DA*'s ability to reject such unwanted signals.

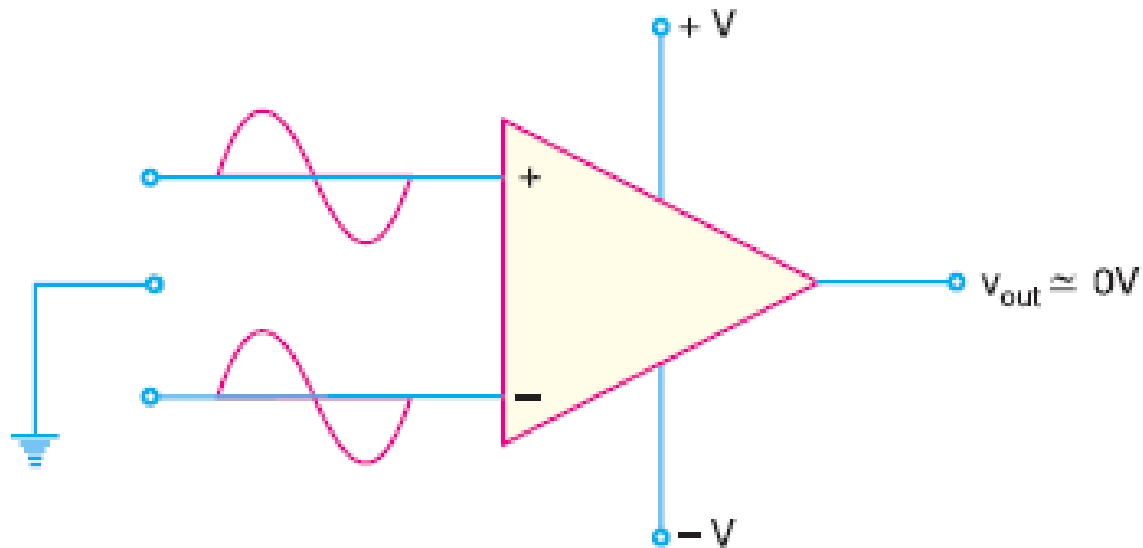

Common-mode Rejection Ratio (CMRR)

- ▶ How does a differential amplifier reject hum and static voltages induced into its input leads???


Common-mode Rejection Ratio (CMRR)

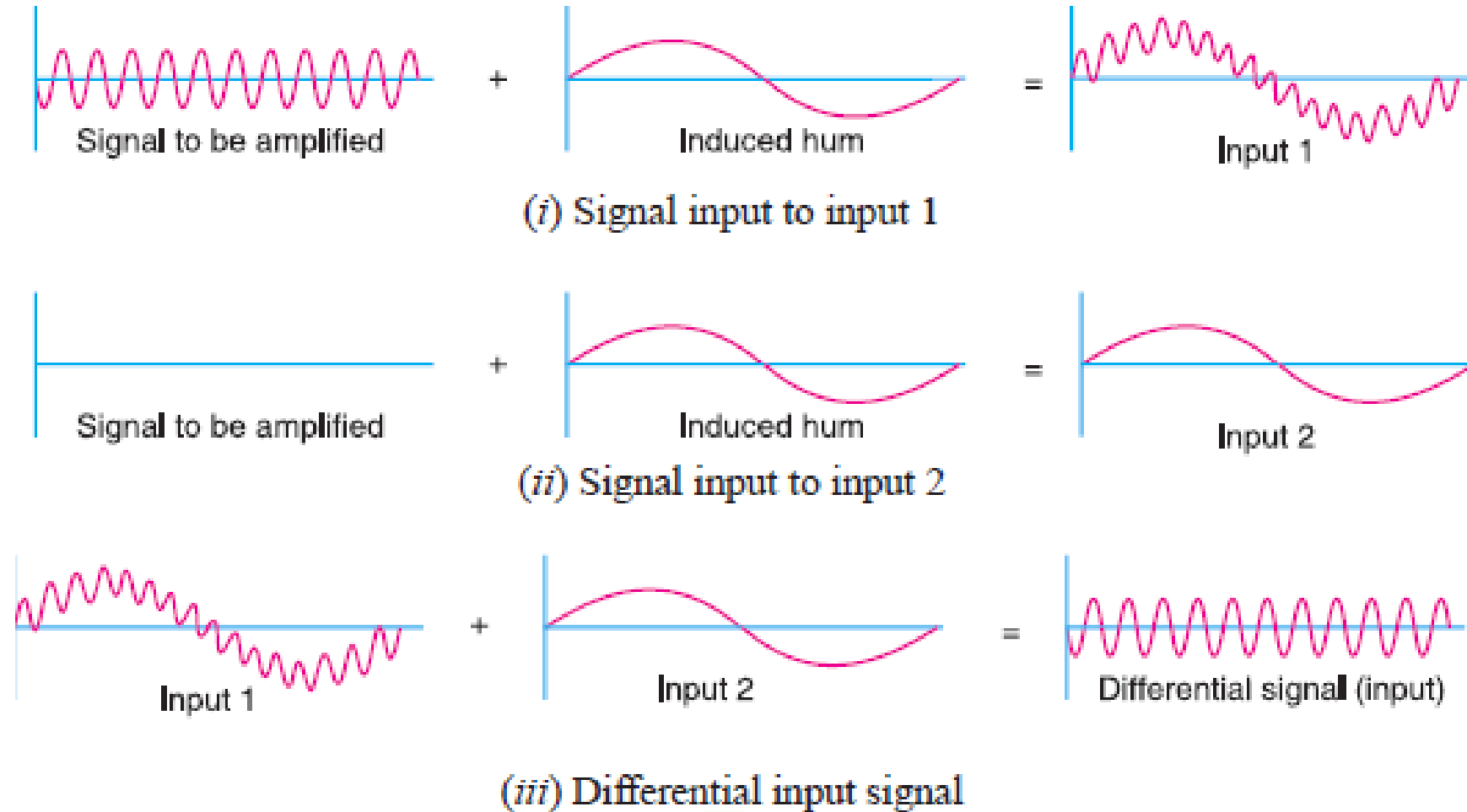


In Fig. 4.5, the signal is applied to input 1 of the *DA*. However, a low frequency *hum* voltage is also induced into the lead wire. The resultant waveform is shown in Fig. 4.5 (i).

However, a *DA* also has second input (input 2). Therefore, the lead of second input has the same phase 50 Hz hum induced into it. This is the only voltage (*i.e.*, hum) applied to input 2 as shown in Fig. 4.5 (ii).


Common-mode Rejection Ratio (CMRR)

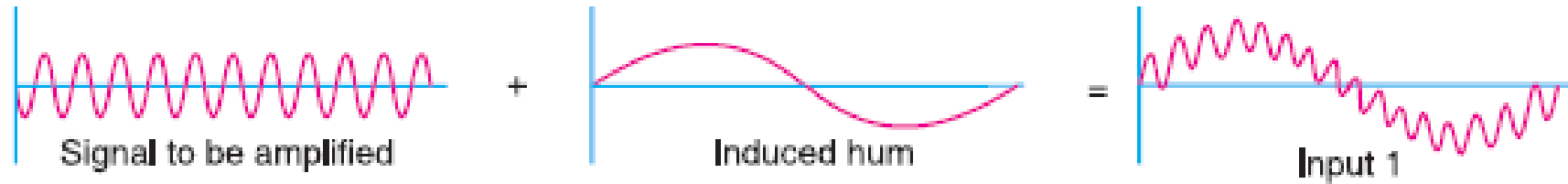

(i) Signal input to input 1

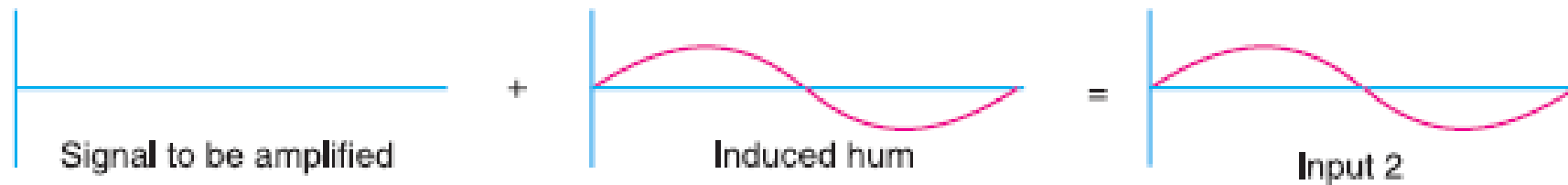

(ii) Signal input to input 2

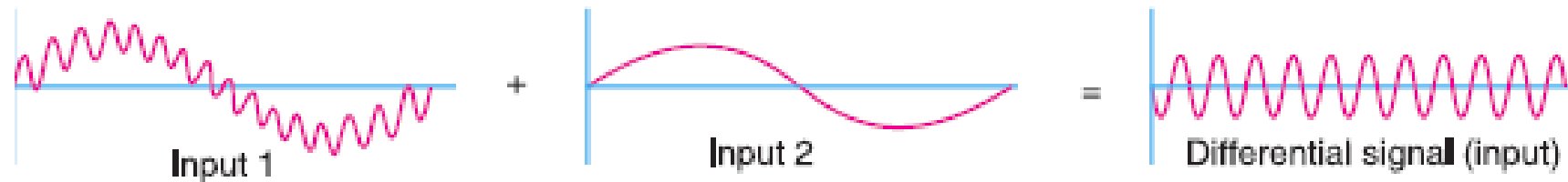

(iii) Differential input signal

As shown in Fig. 4.5 (iii), the hum components of the two inputs form a common-mode signal which is largely rejected by the *DA*. If the input hum signals are equal at the input, then differential input to *DA* will be devoid of hum. Therefore, the amplified output of *DA* will be free from the hum.

Example 25.2. *A certain differential amplifier has a differential voltage gain of 2000 and a common mode gain of 0.2. Determine CMRR and express it in dB.*

Example 25.3. *A differential amplifier has an output of 1V with a differential input of 10 mV and an output of 5 mV with a common-mode input of 10 mV. Find the CMRR in dB.*

Common-mode Rejection Ratio (CMRR)

Example 25.2. *A certain differential amplifier has a differential voltage gain of 2000 and a common mode gain of 0.2. Determine CMRR and express it in dB.*

Solution.

$$CMRR = \frac{A_{DM}}{A_{CM}} = \frac{2000}{0.2} = 10,000$$

$$CMRR_{dB} = 20 \log_{10} 10,000 = 80\text{dB}$$

Example 25.3. *A differential amplifier has an output of 1V with a differential input of 10 mV and an output of 5 mV with a common-mode input of 10 mV. Find the CMRR in dB.*

Solution. Differential gain, $A_{DM} = 1\text{V}/10\text{ mV} = 100$

Common-mode gain, $A_{CM} = 5\text{ mV}/10\text{ mV} = 0.5$

$\therefore CMRR_{dB} = 20 \log_{10} (100/0.5) = 46\text{ dB}$

Example 25.4. *A differential amplifier has a voltage gain of 150 and a CMRR of 90 dB. The input signals are 50 mV and 100 mV with 1 mV of noise on each input. Find (i) the output signal (ii) the noise on the output.*

Common-mode Rejection Ratio (CMRR)

Example 25.4. A differential amplifier has a voltage gain of 150 and a CMRR of 90 dB. The input signals are 50 mV and 100 mV with 1 mV of noise on each input. Find (i) the output signal (ii) the noise on the output.

Solution.

(i) Output signal, $v_{out} = A_{DM}(v_1 - v_2) = 150 (100 \text{ mV} - 50 \text{ mV}) = 7.5 \text{ V}$

(ii) $CMRR_{dB} = 20 \log_{10} (150/A_{CM})$

or $90 = 20 \log_{10} (150/A_{CM})$

$\therefore A_{CM} = 4.7 \times 10^{-3}$

Noise on output $= A_{CM} \times 1 \text{ mV} = 4.7 \times 10^{-3} \times 1 \text{ mV} = 4.7 \times 10^{-6} \text{ V}$

Slew Rate

The slew rate of an *OP*-amp is a measure of *how fast the output voltage can change* and is measured in volts per microsecond ($\text{V}/\mu\text{s}$). If the slew rate of an *OP*-amp is $0.5\text{V}/\mu\text{s}$, it means that the output from the amplifier can change by 0.5 V every μs . Since frequency is a function of time, the *slew rate* can be used to determine the maximum operating frequency of the *OP*-amp as follows:

$$\text{Maximum operating frequency, } f_{\max} = \frac{\text{Slew rate}}{2\pi V_{pk}}$$

Here V_{pk} is the peak output voltage.

Problem

What is the maximum operating frequency of an amplifier having an input signal to a peak output voltage of 100 mV and slew rate of $0.5 \text{ V}/\mu\text{s}$.

Problem

What is the maximum operating frequency of an amplifier having an input signal to a peak output voltage of 100 mV and slew rate of 0.5 V/μs.

The maximum operating frequency (f_{max}) of the amplifier is given by;

$$\begin{aligned} f_{max} &= \frac{\text{Slew rate}}{2\pi V_{pk}} = \frac{0.5 \text{ V} / \mu\text{s}}{2\pi \times 0.1} && (\because 100 \text{ mV} = 0.1\text{V}) \\ &= \frac{500 \text{ kHz}}{2\pi \times 0.1} = \mathbf{796 \text{ kHz}} && (\because 0.5\text{V}/\mu\text{s} = 500 \text{ kHz}) \end{aligned}$$