

Analog Electronics



Shishir Mallick

Lecturer

Dept. of CSE

Bangladesh University

References

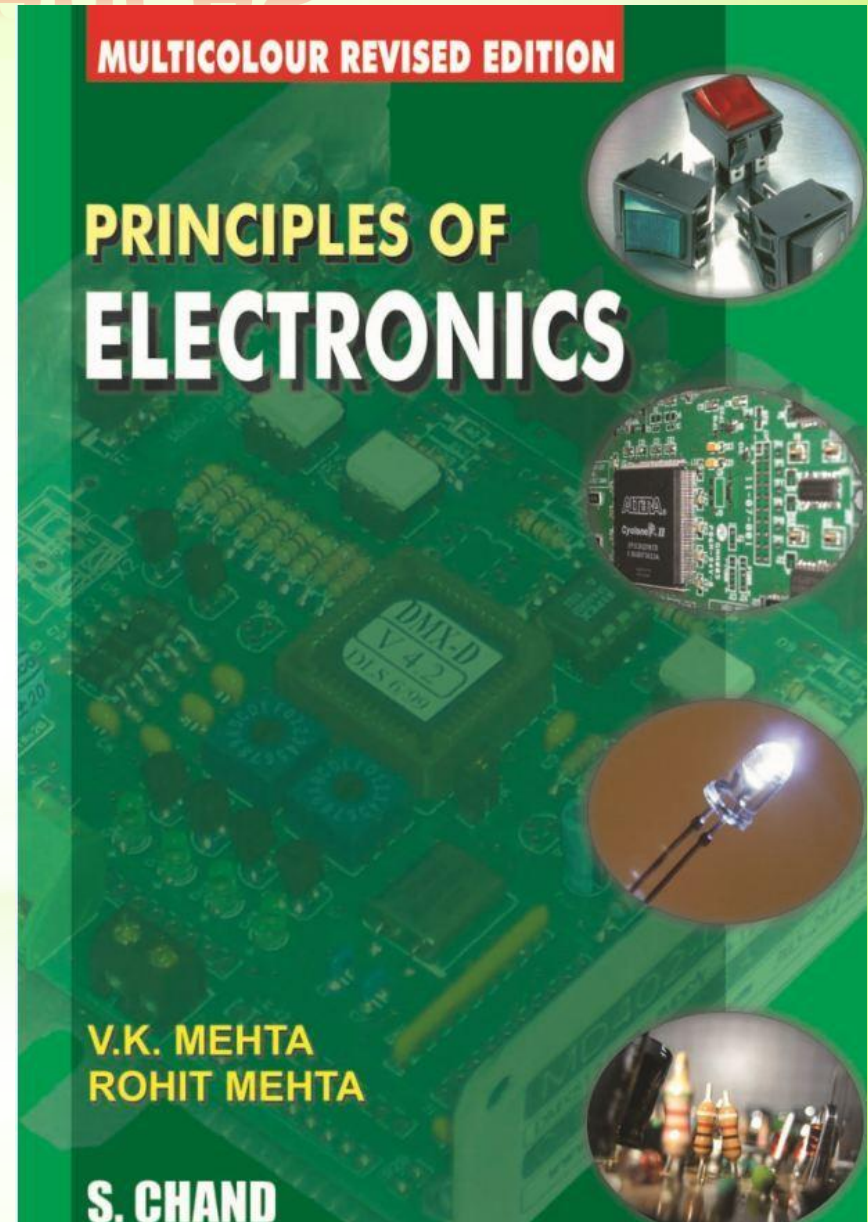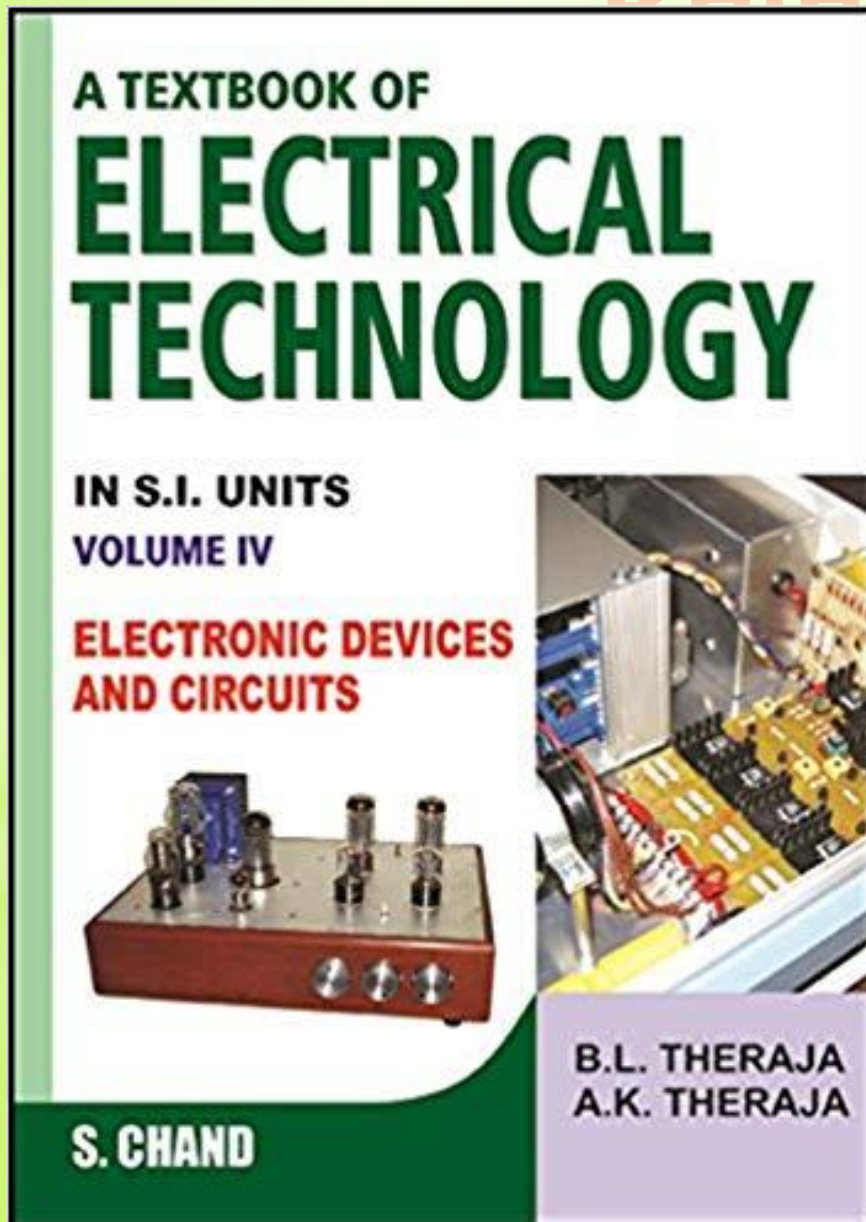




Clipping Circuit

The circuit with which the waveform is shaped by removing a portion of the applied wave is known as a clipping circuit.

Problem 1


For the simple parallel clipper of Fig. 52.31, find the shape of the output voltage V_O across the diode if the input sine wave signal is as shown in Fig. 52.31 (a). What will happen when diode and resistor are inter-changed ?

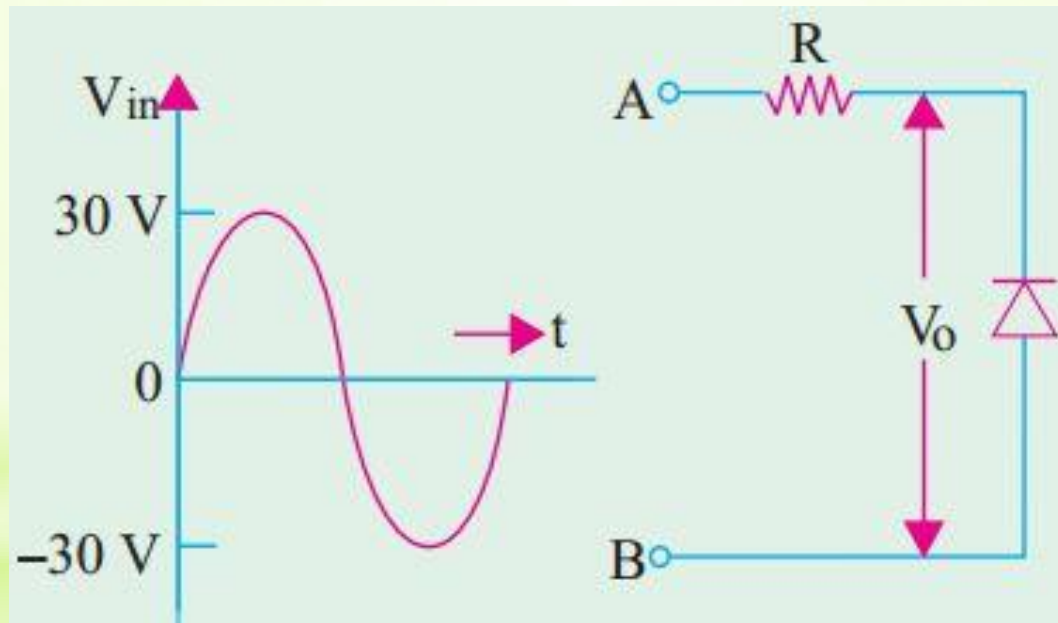

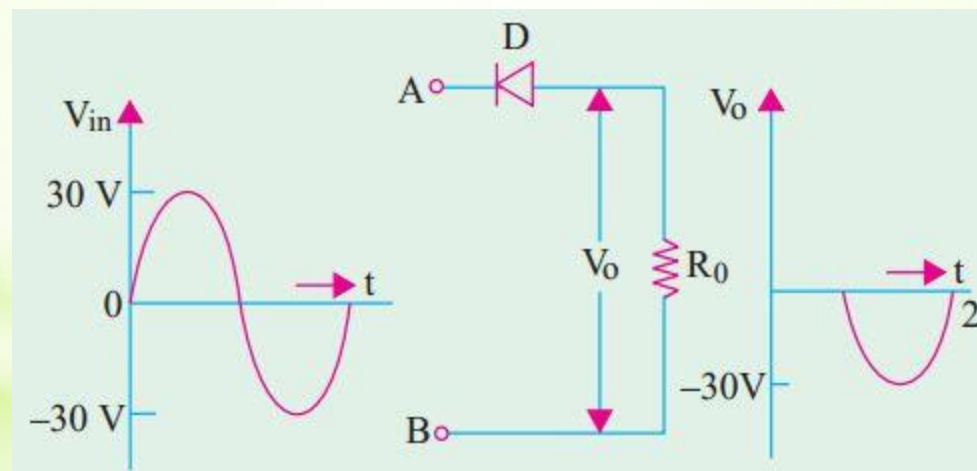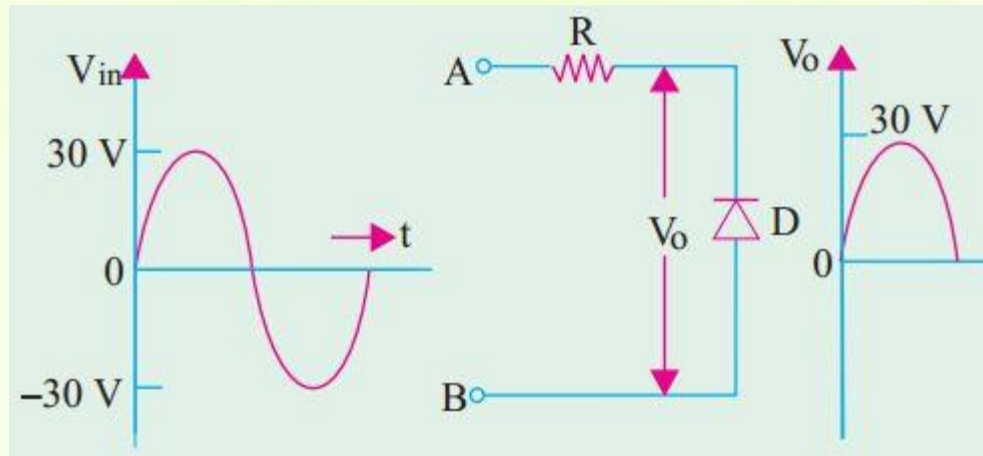

Problem 2

A sinusoidal voltage of peak value 50 V is applied to a diode as shown in Fig. 52.21. Sketch the waveform of voltage V_O treating the diode as an ideal one.

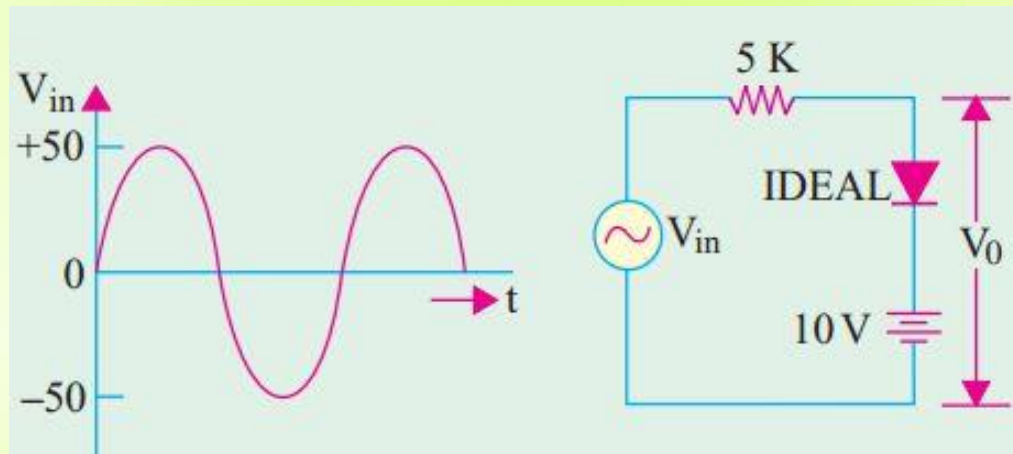

Example. 52.13. A sinusoidal voltage of peak value 50 V is applied to a diode as shown in Fig. 52.21. Sketch the waveform of voltage V_O treating the diode as an ideal one.

Solution. First, consider the positive half-cycle of the input signal. The diode acts as a short in the forward direction and the moment V_{in} exceeds battery voltage of 10 V, current will start flowing through the circuit. The value of V_O will remain steady at 10 V, the balance of 40 V dropping across 5 K resistance. It is seen that value of V_O is set by the battery voltage.


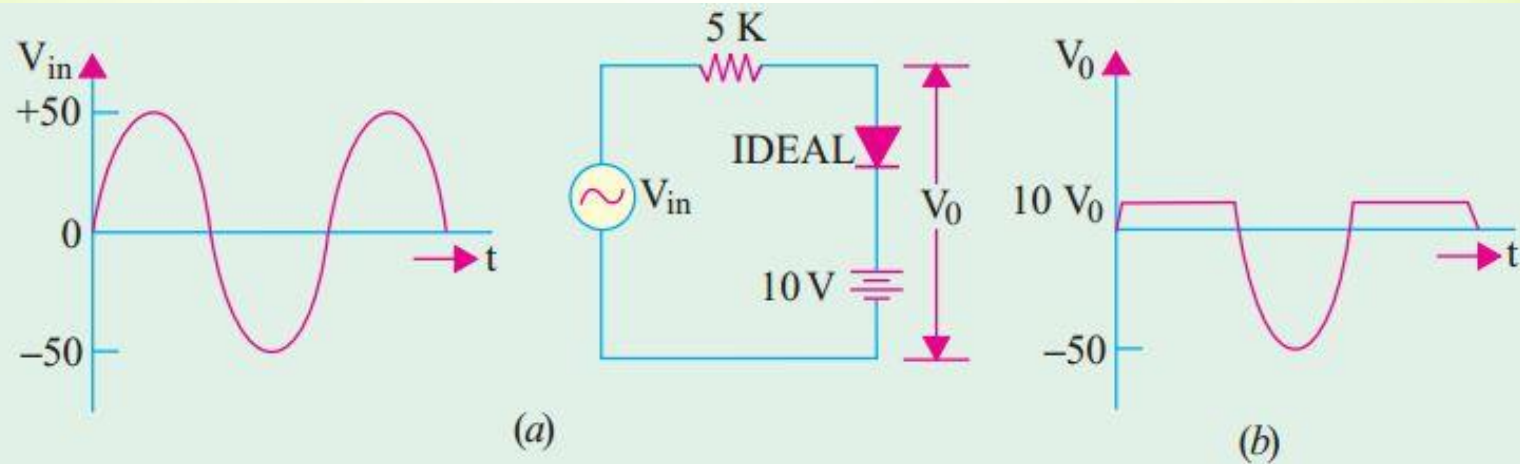


Fig. 52.21

Next, consider the negative input half-cycle. Now, the diode acts like an open switch. Consequently, there is no circuit current and thus no voltage drop across 5 K resistor. Hence, V_O equals source voltage of peak value 50 V.

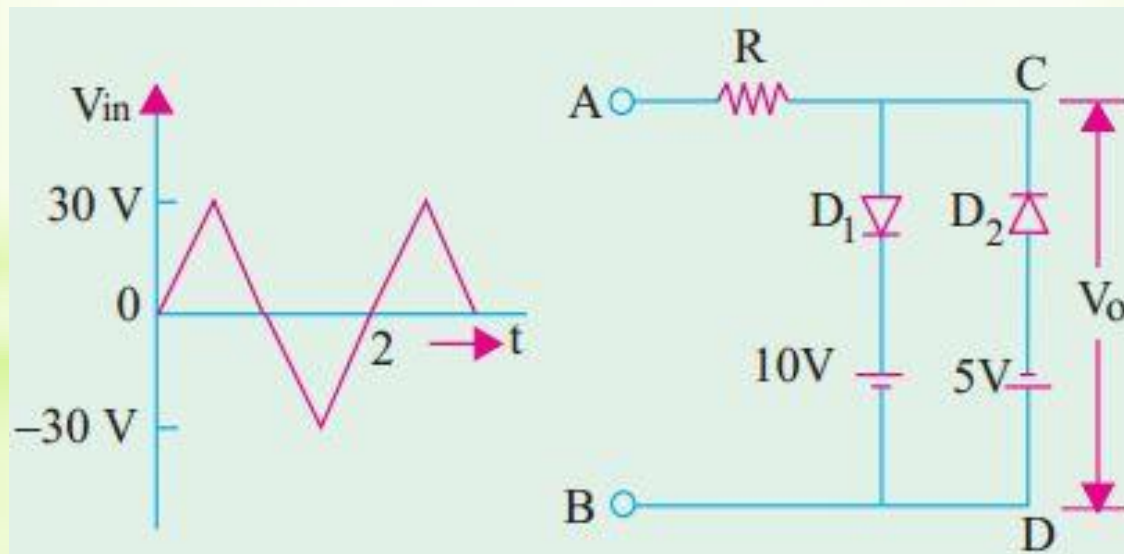Problem 3

The triangular voltage of Fig. 52.36 (a) is applied to the biased parallel clipper circuit of Fig 52.36 (b). Find the wave-shape of the output voltage.



Solution. During the positive half-cycle, D_1 would conduct but D_2 will act as an open-circuit. However, value of V_0 cannot exceed 10V because points C and D are electrically connected across the 10 V battery since D_1 is shorted. Hence, signal voltage above 10 V level would be clipped off as shown in Fig. 52.36 (c).


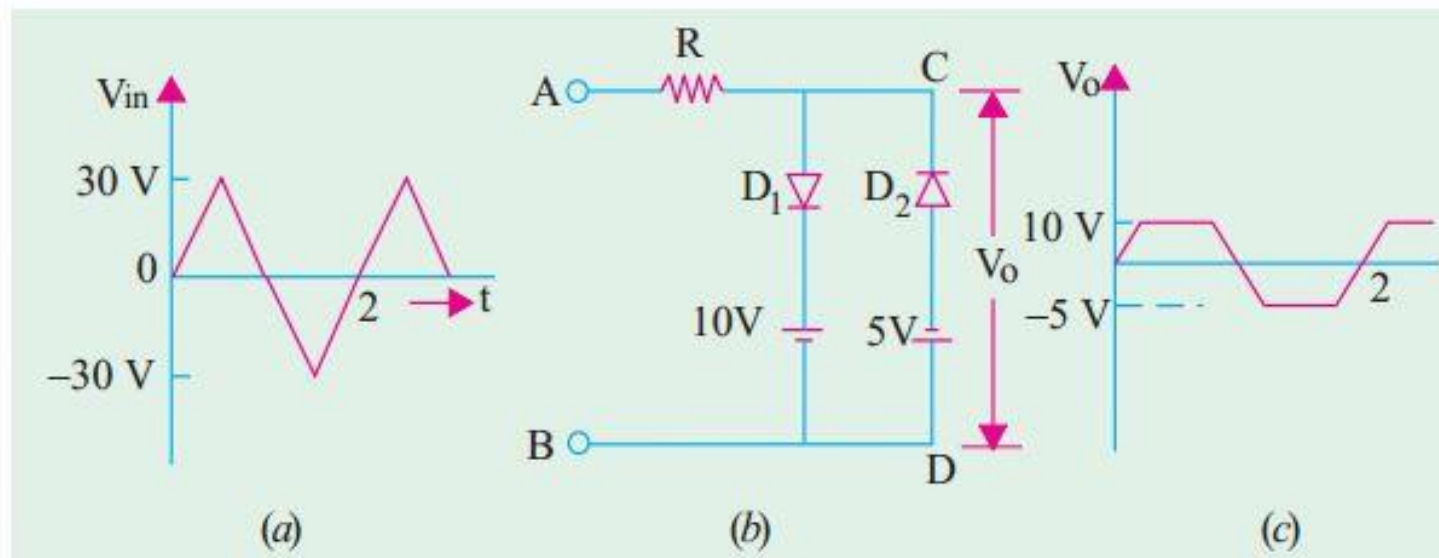




Fig. 52.36

Problem 4

The negative shunt clipper shown in Fig. 4 has a peak input voltage of +10 V. What is the peak output voltage from this circuit?

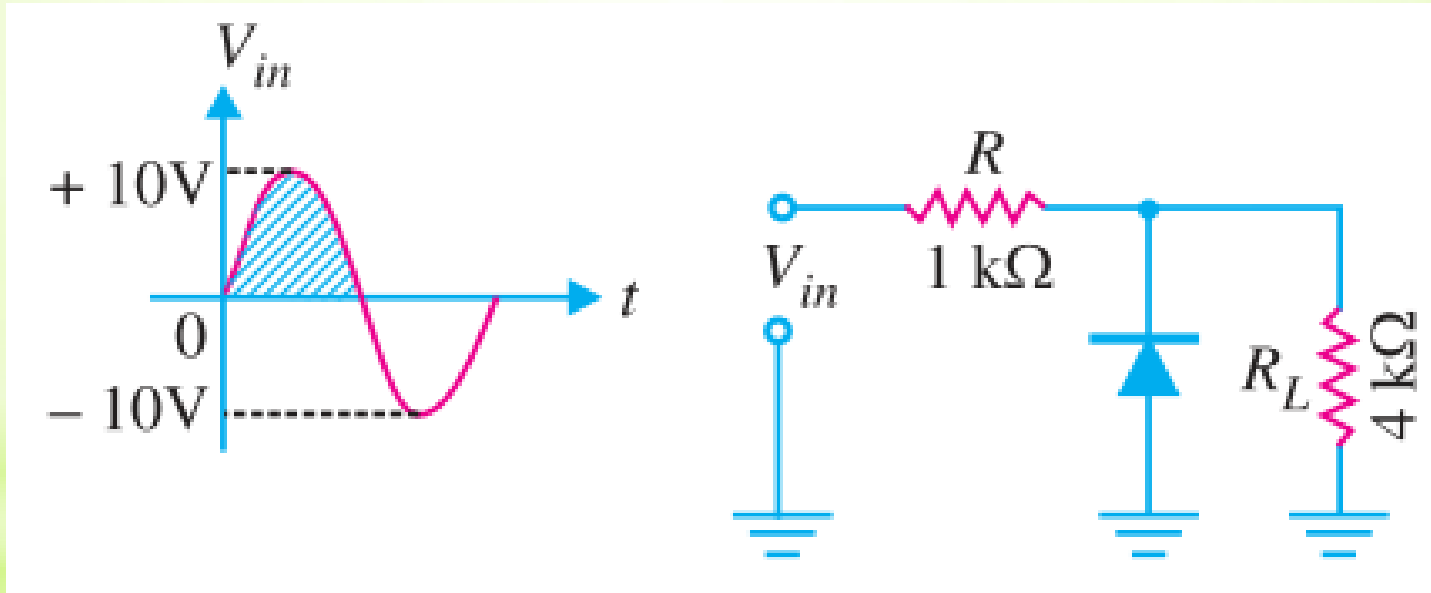


Problem 4

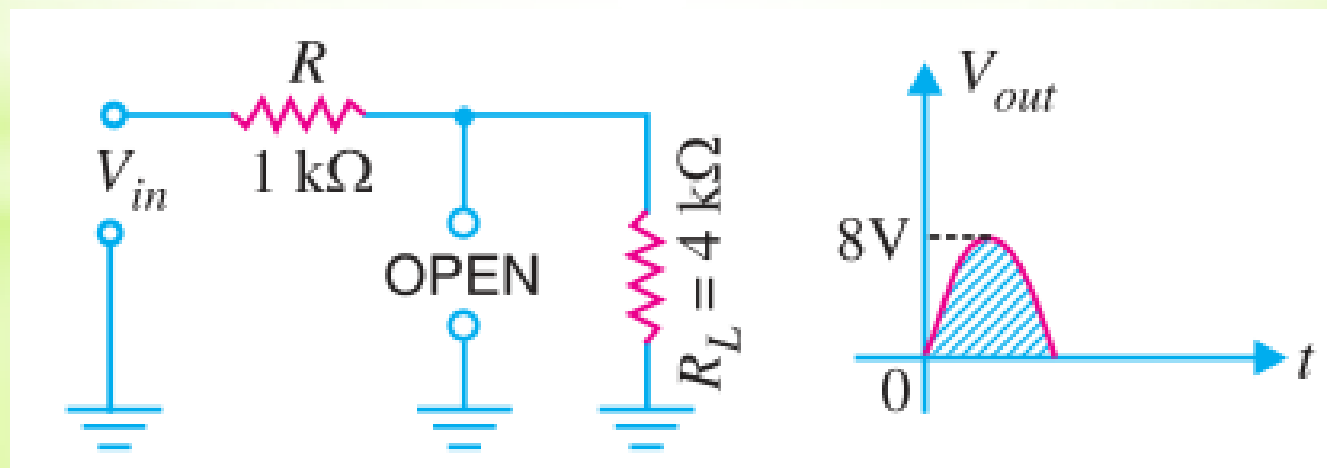
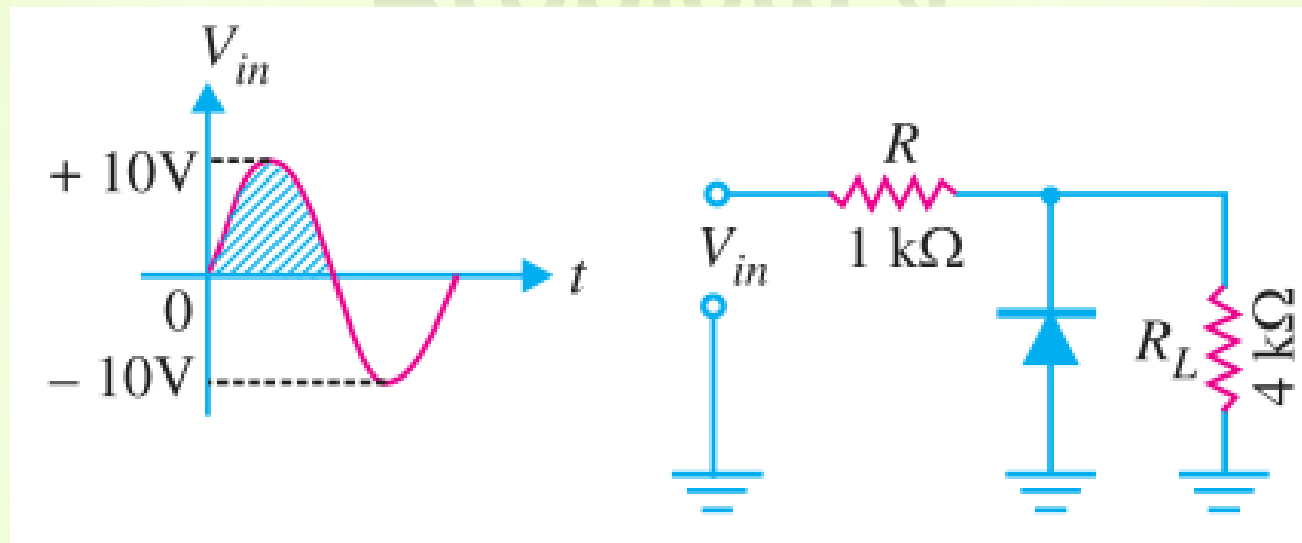


Problem 5

what will be the output voltage and voltage across R when the input voltage is -10 V ?


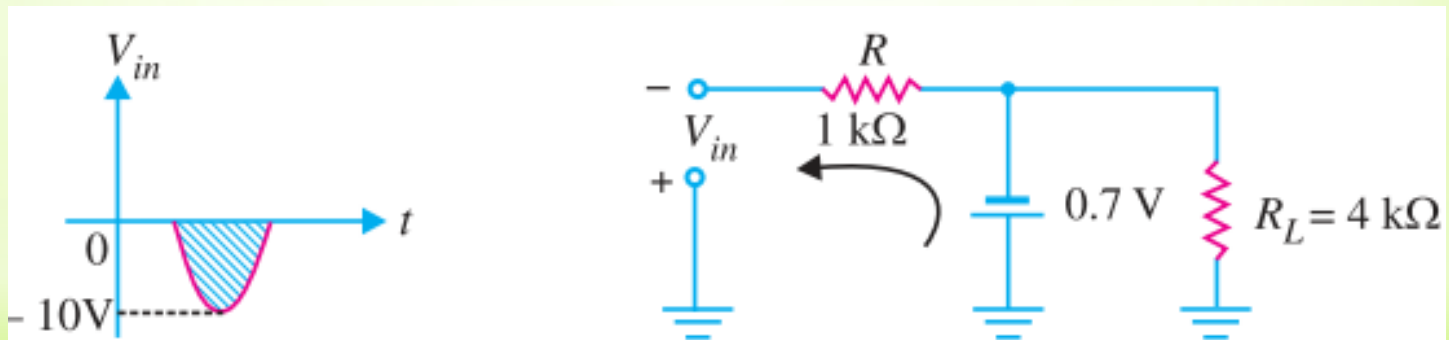


Problem 5


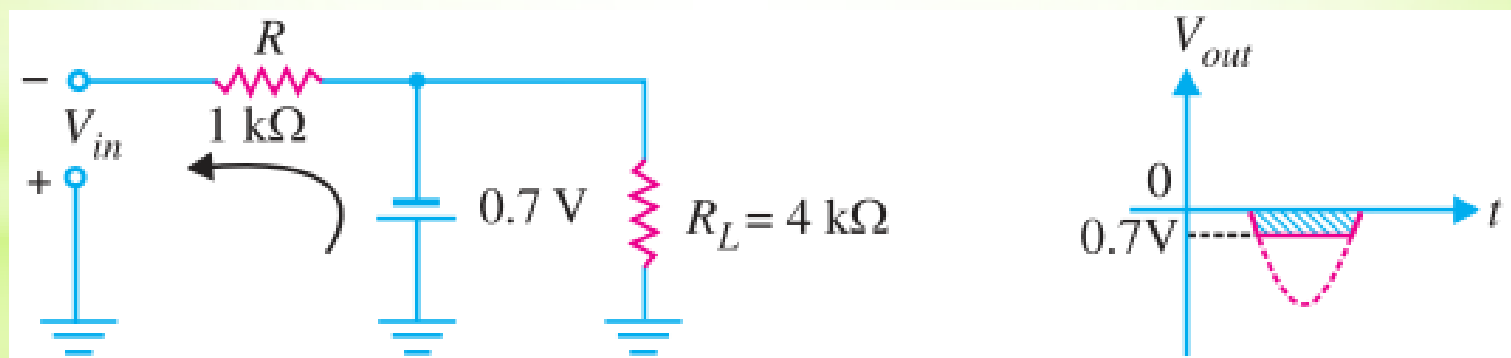
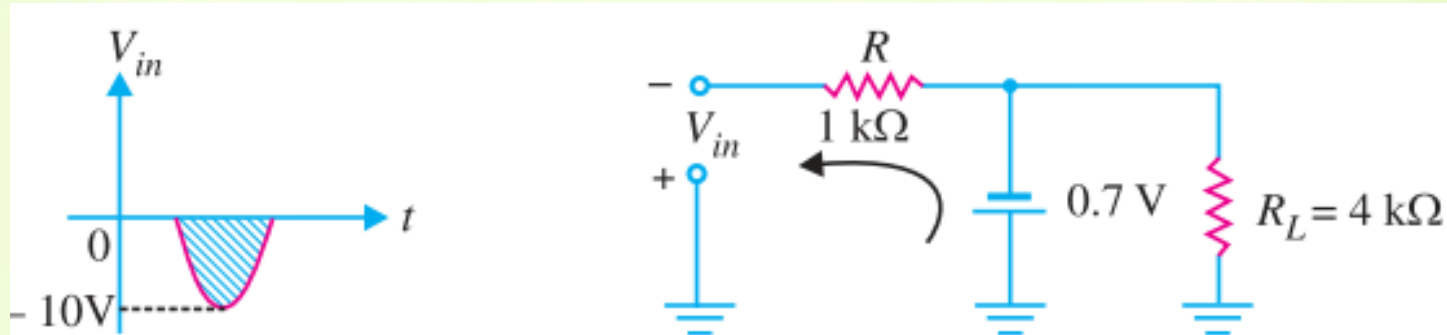


Problem 6

For the input wave to the clipping circuit shown in Fig. 6, find the output waveform.

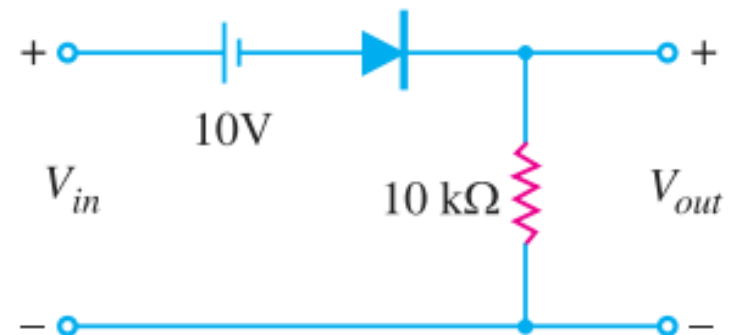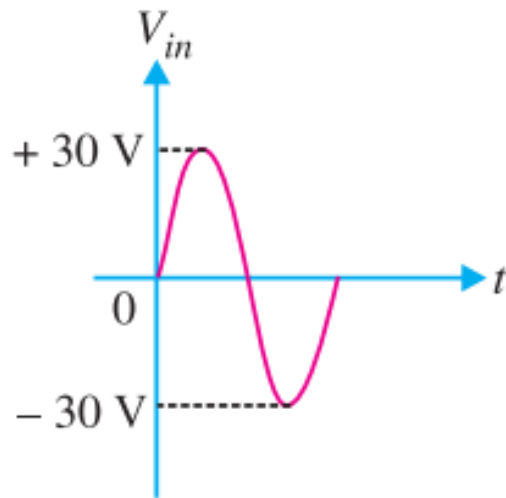

Problem 6

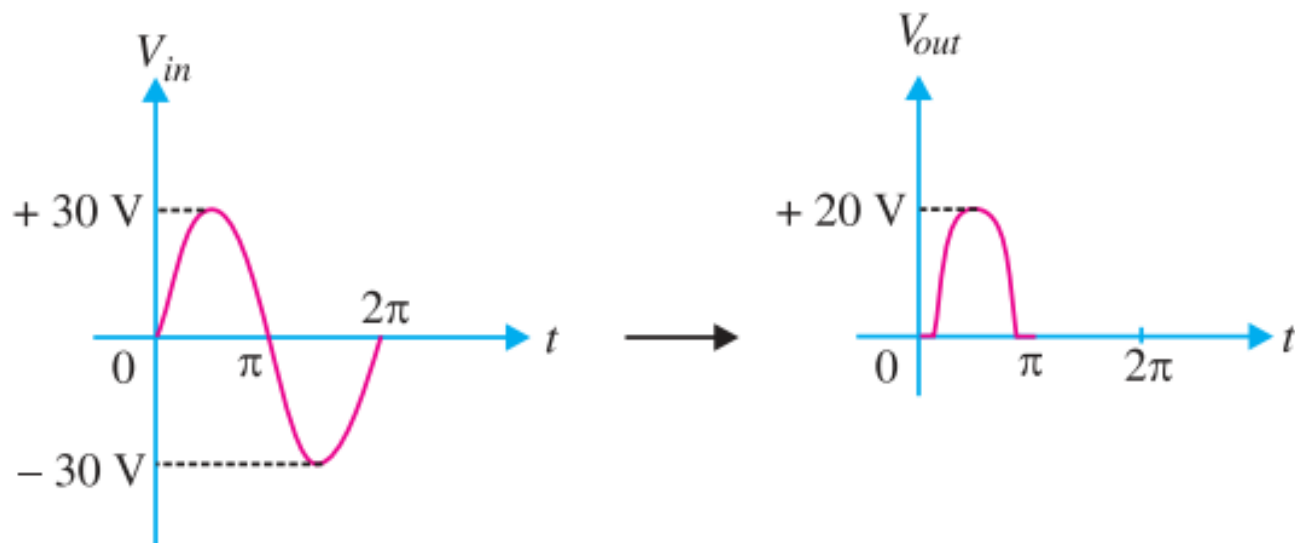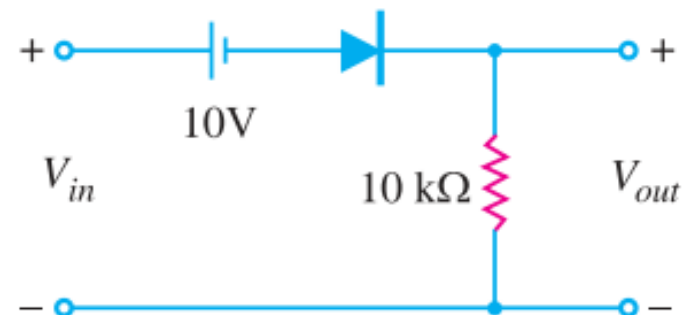
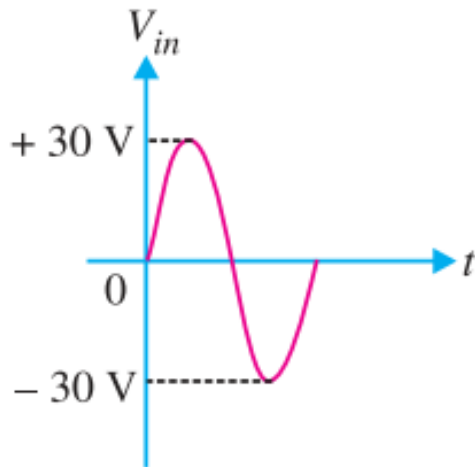


Clamping Circuits

A circuit that places either the positive or negative peak of a signal at a desired d.c. level is known as a **clamping circuit**.

Problem 7

Determine v_o for the following network with the input shown (for ideal diode).

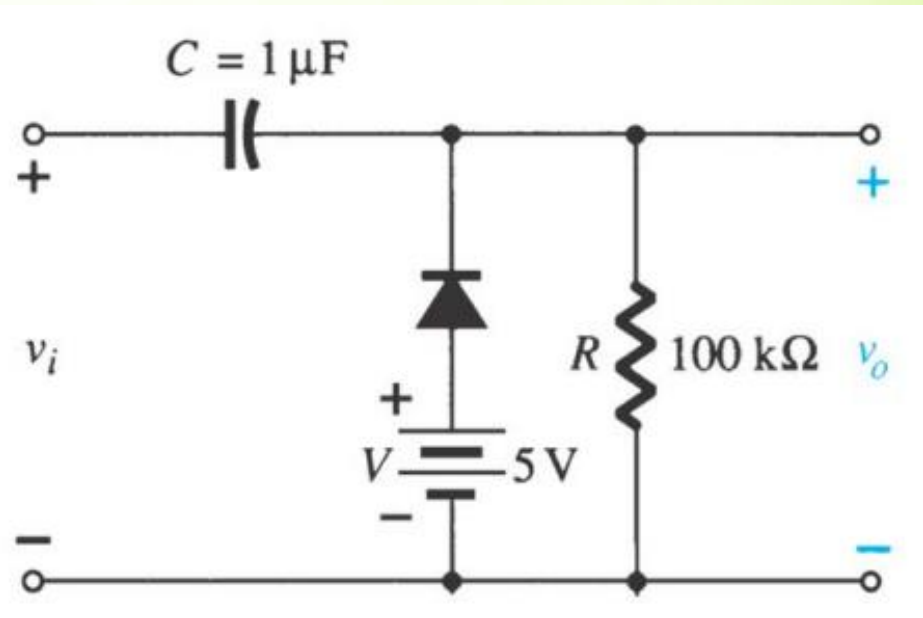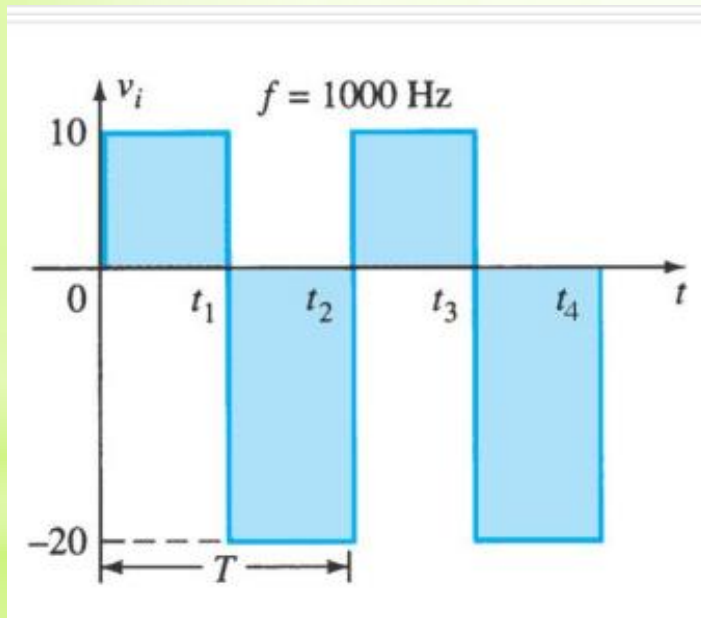

Problem 7

