

# Analog Electronics



Shishir Mallick

Lecturer

Dept. of CSE


Bangladesh University

# References

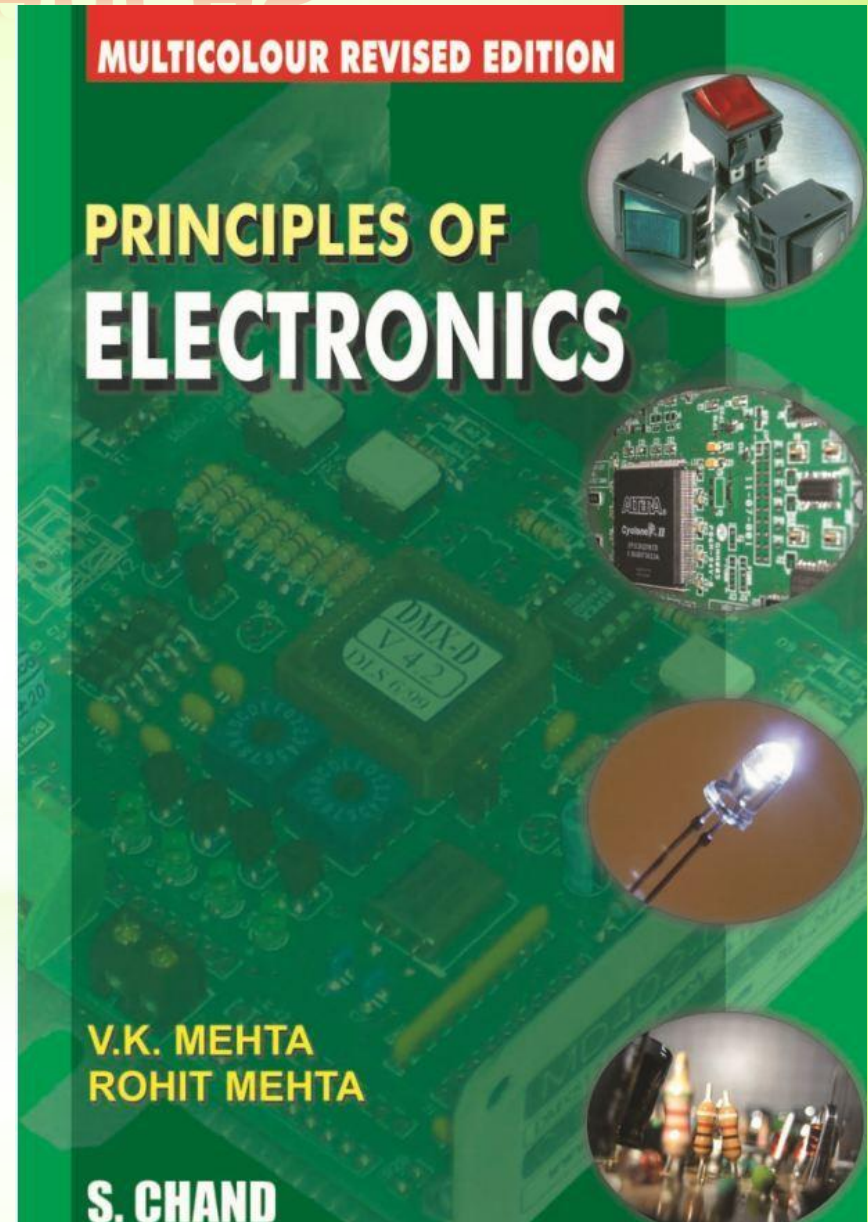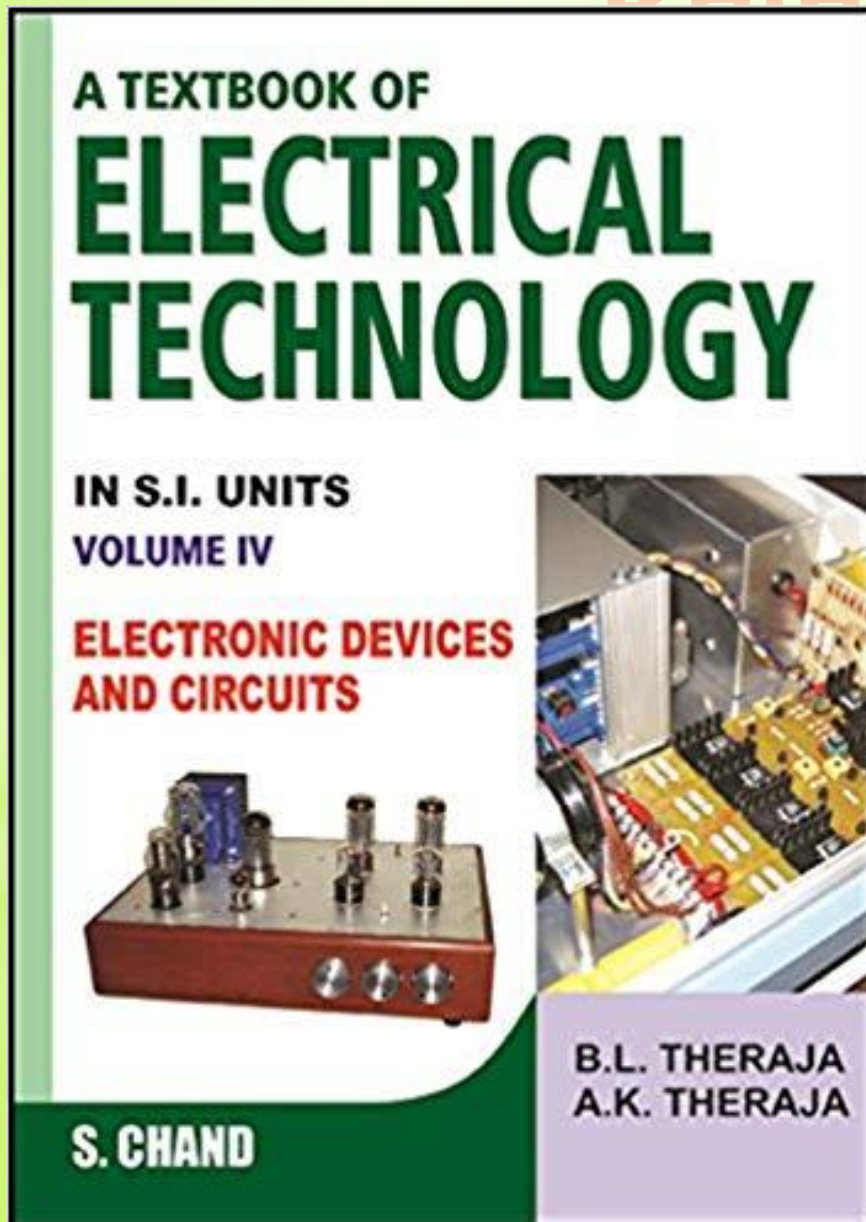

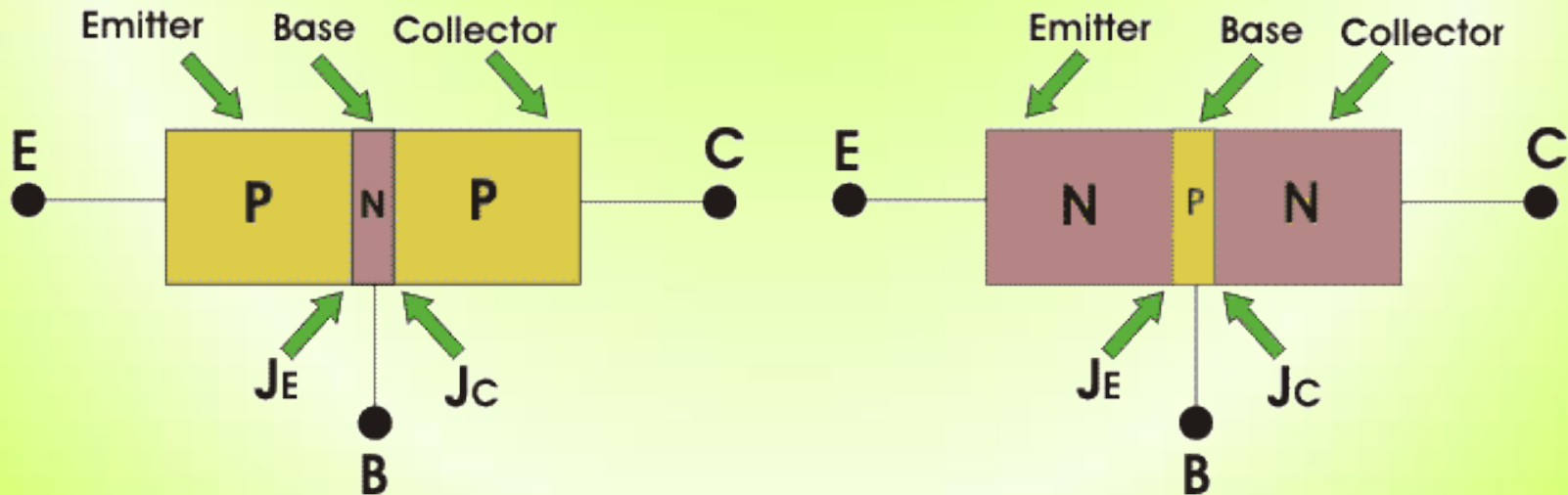
# Transistor


A **transistor** consists of two p-n junctions formed by sandwiching either p-type or n-type semiconductor between a pair of opposite types.



# Transistor Symbols

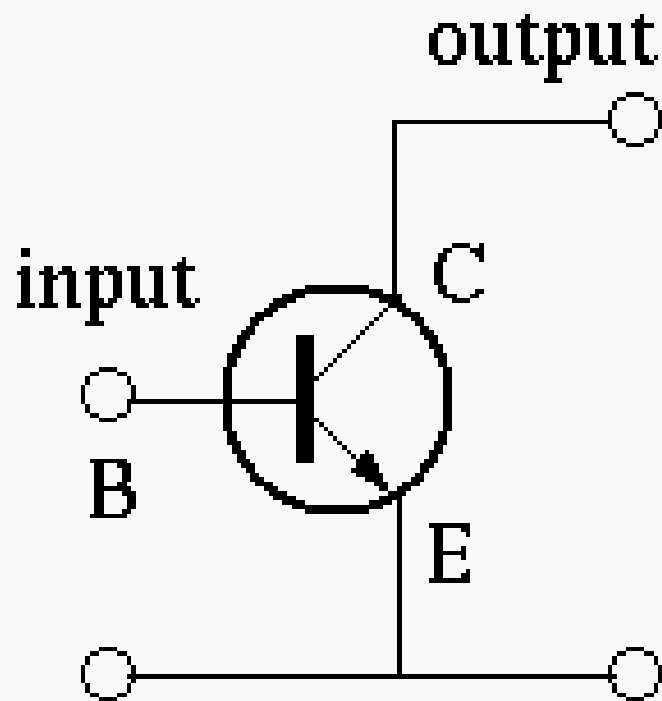

npn transistor

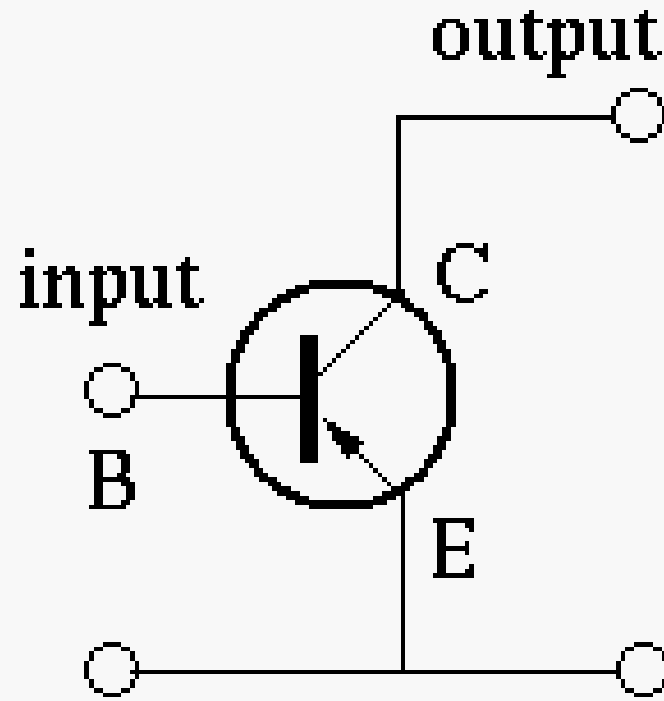


pnp transistor

# Transistor Action
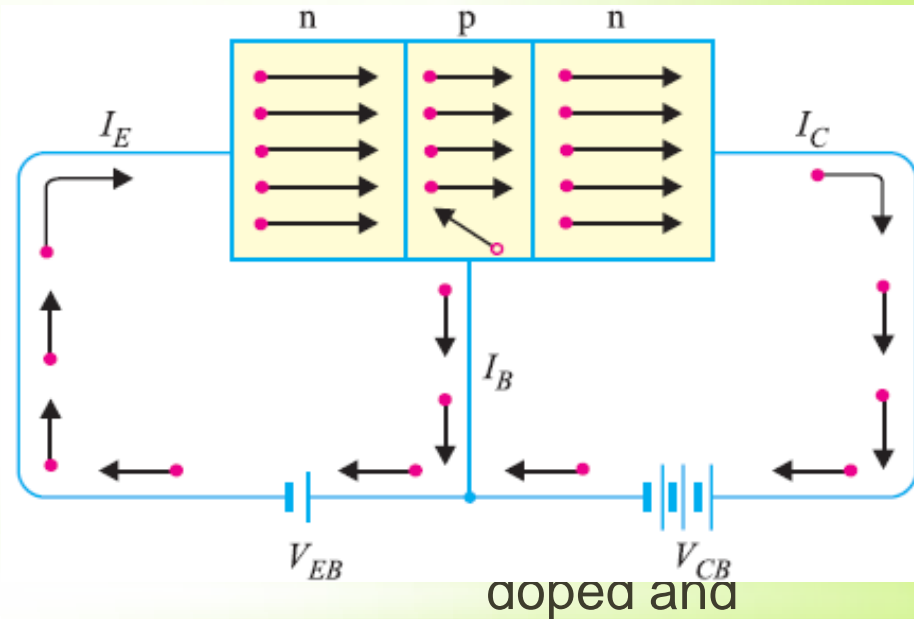
# Working of npn transistor


- forward bias to emitter base junction.
- reverse bias to collector-base
- forward bias causes the electrons the  $n$ -type emitter to flow base. This constitutes  $I_E$ .
- As these electrons flow through the type base, they tend to combine holes. As the base is lightly doped and very thin, therefore, only a few electrons (less than 5%) combine with holes to constitute base current  $I_B$ .
- The remainder cross over into the collector region to constitute collector current  $I_C$ .



$$I_E = I_B + I_C$$



# Working of pnp transistor

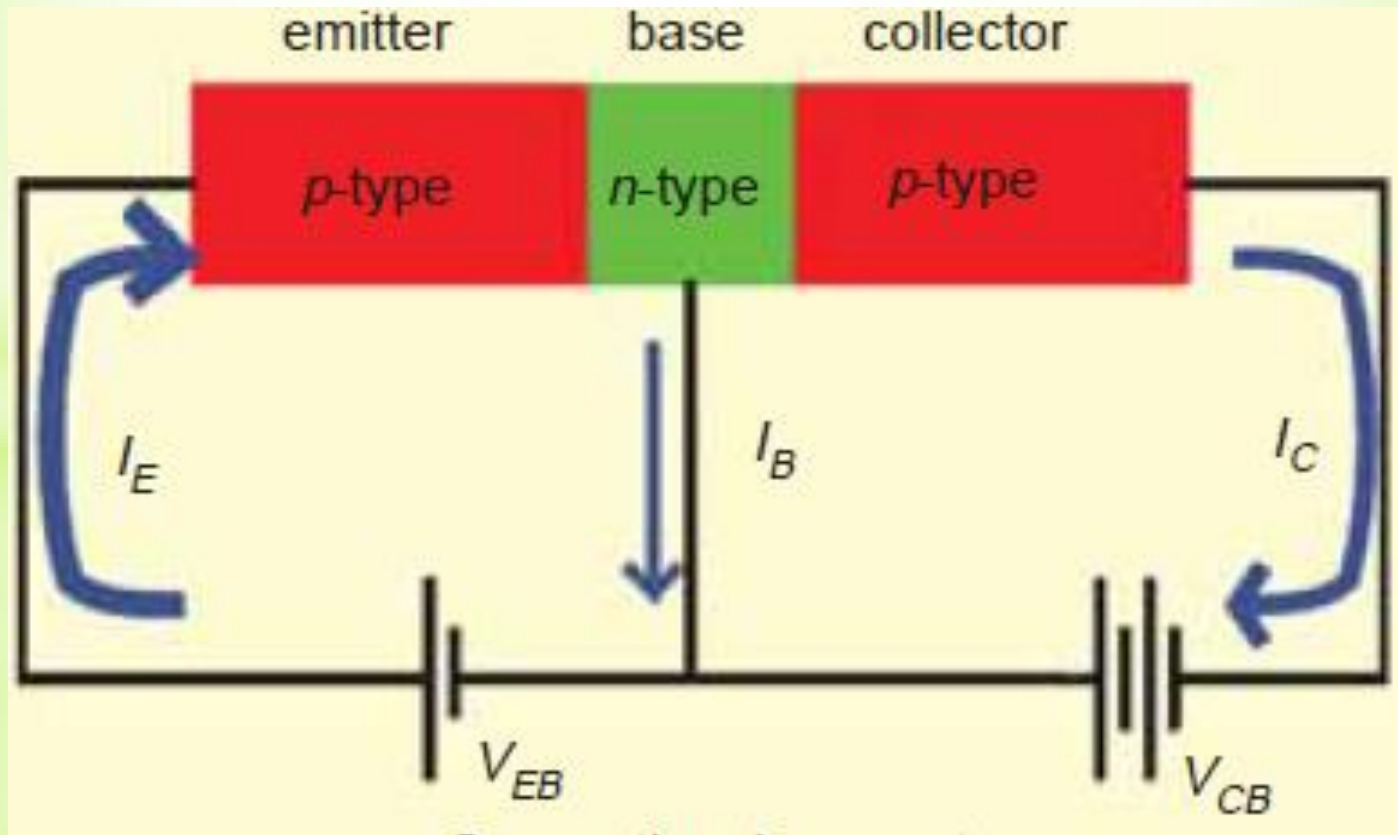



# Transistor Connections

- ❖ common base connection
- ❖ common emitter connection
- ❖ common collector connection


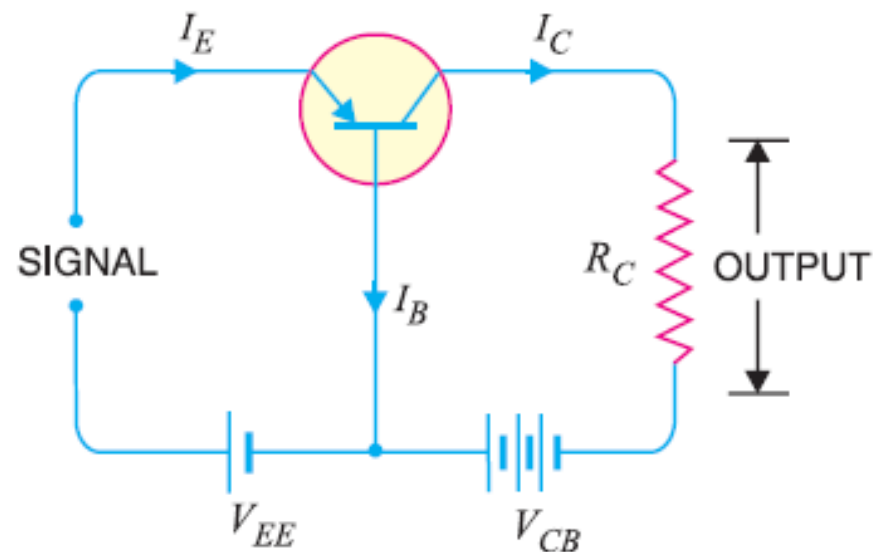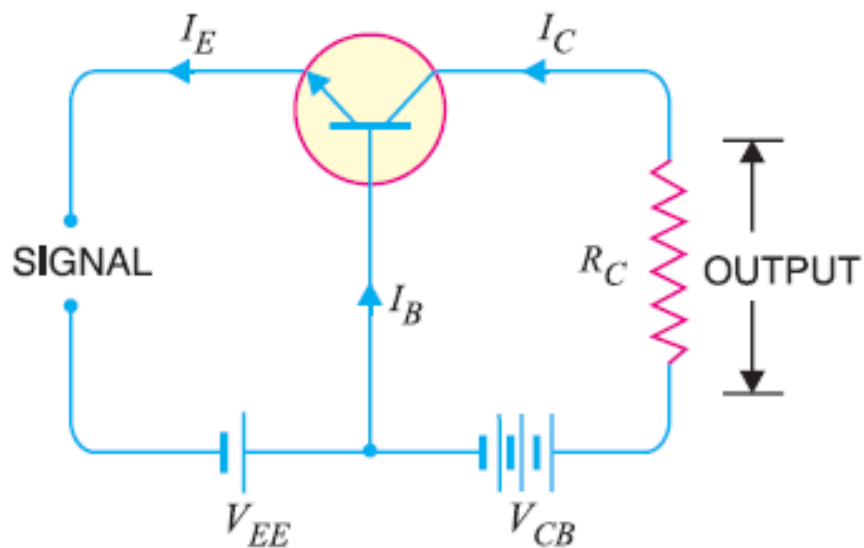
# Common Base Connection

In this circuit arrangement, input is applied between emitter and base and output is taken from collector and base. Here, base of the transistor is common to both input and output circuits and hence the name common base connection. In Fig. 8.9 (i), a common base *npn* transistor circuit is shown whereas Fig. 8.9 (ii) shows the common base *pnp* transistor circuit.



# Current amplification factor ( $\alpha$ )

It is the ratio of output current to input current. In a common base connection, the input current is the emitter current  $I_E$  and output current is the collector current  $I_C$ .

***The ratio of change in collector current to the change in emitter current at constant collector base voltage  $V_{CB}$  is known as current amplification factor.***

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \text{ at constant } V_{CB}$$

$\alpha$  is always less than unity.

**Example 8.3:** In a common base connection, current amplification factor is 0.9. If the emitter current is 1mA, determine the value of base current.

**Example 8.3.** In a common base connection, current amplification factor is 0.9. If the emitter current is 1mA, determine the value of base current.

**Solution.**

$$\text{Here, } \alpha = 0.9, \quad I_E = 1 \text{ mA}$$

Now

$$\alpha = \frac{I_C}{I_E}$$

or

$$I_C = \alpha I_E = 0.9 \times 1 = 0.9 \text{ mA}$$


Also

$$I_E = I_B + I_C$$

$\therefore$

$$\text{Base current, } I_B = I_E - I_C = 1 - 0.9 = \mathbf{0.1 \text{ mA}}$$

**Example 8.7.** For the common base circuit shown in Fig. 8.13, determine  $I_C$  and  $V_{CB}$ . Assume the transistor to be of silicon.

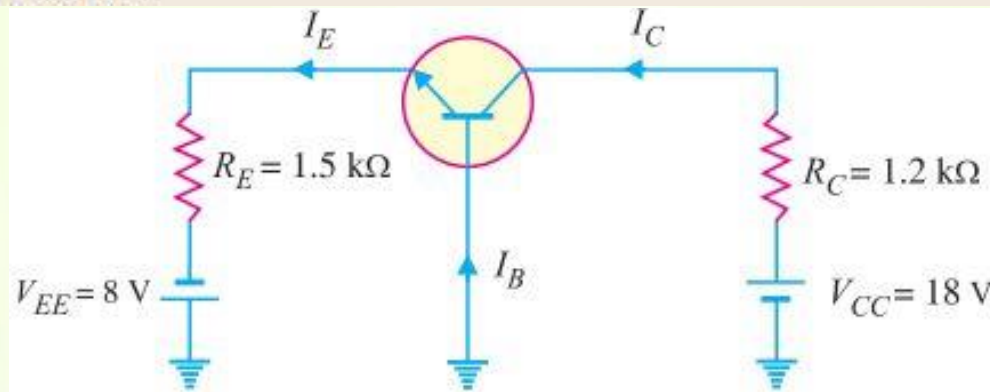

**Example 8.7.** For the common base circuit shown in Fig. 8.13, determine  $I_C$  and  $V_{CB}$ . Assume the transistor to be of silicon.

**Solution.** Since the transistor is of silicon,  $V_{BE} = 0.7\text{V}$ . Applying Kirchhoff's voltage law to the emitter-side loop, we get,

$$V_{EE} = I_E R_E + V_{BE}$$

or 
$$I_E = \frac{V_{EE} - V_{BE}}{R_E}$$

$$= \frac{8\text{V} - 0.7\text{V}}{1.5\text{ k}\Omega} = 4.87\text{ mA}$$


$$\therefore I_C \simeq I_E = \mathbf{4.87\text{ mA}}$$

Applying Kirchhoff's voltage law to the collector-side loop, we have,

$$V_{CC} = I_C R_C + V_{CB}$$

$$\therefore V_{CB} = V_{CC} - I_C R_C$$

$$= 18\text{ V} - 4.87\text{ mA} \times 1.2\text{ k}\Omega = \mathbf{12.16\text{ V}}$$

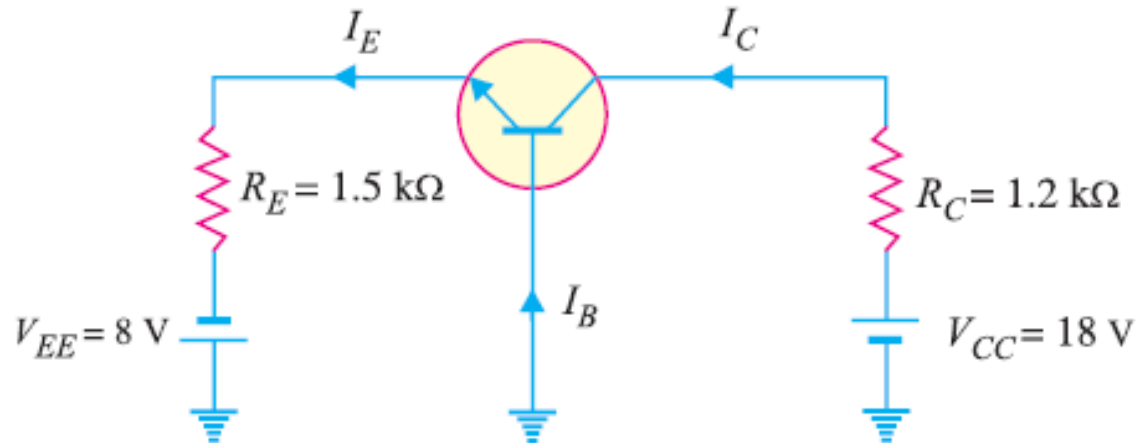


**Fig. 8.13**

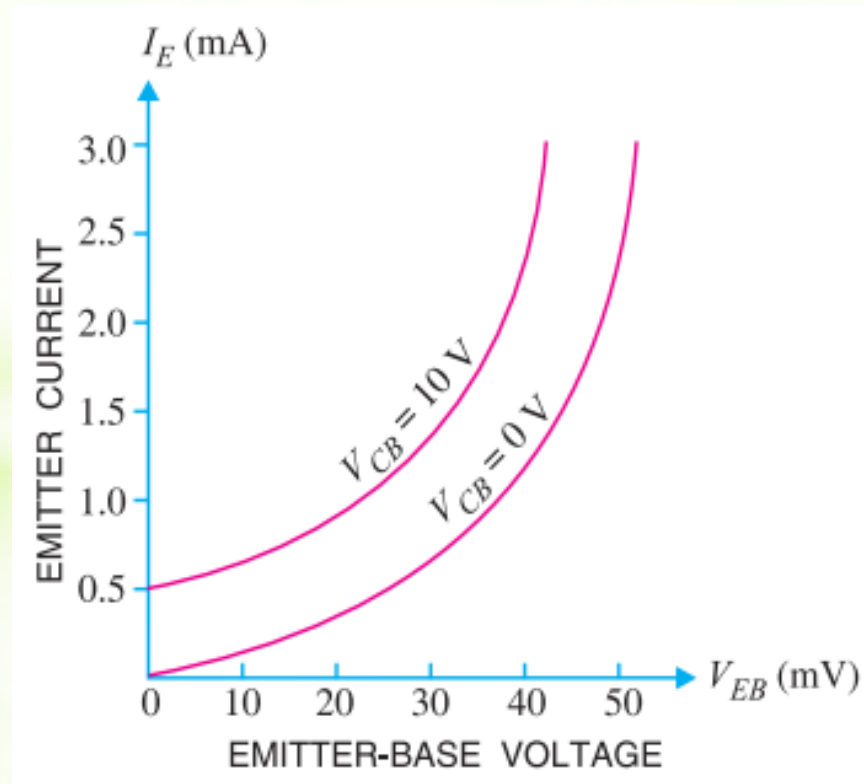


# Characteristics of Common Base Connection

## Input characteristic





# Characteristics of Common Base Connection

## Output characteristic

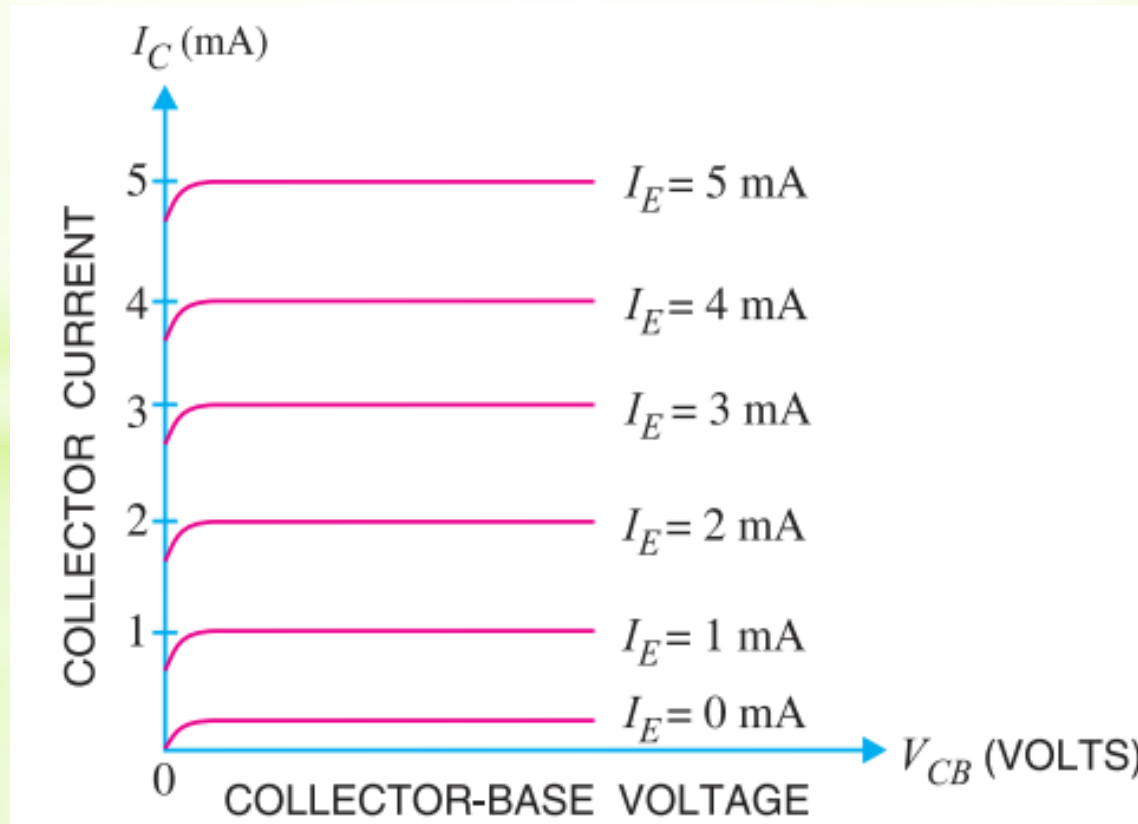
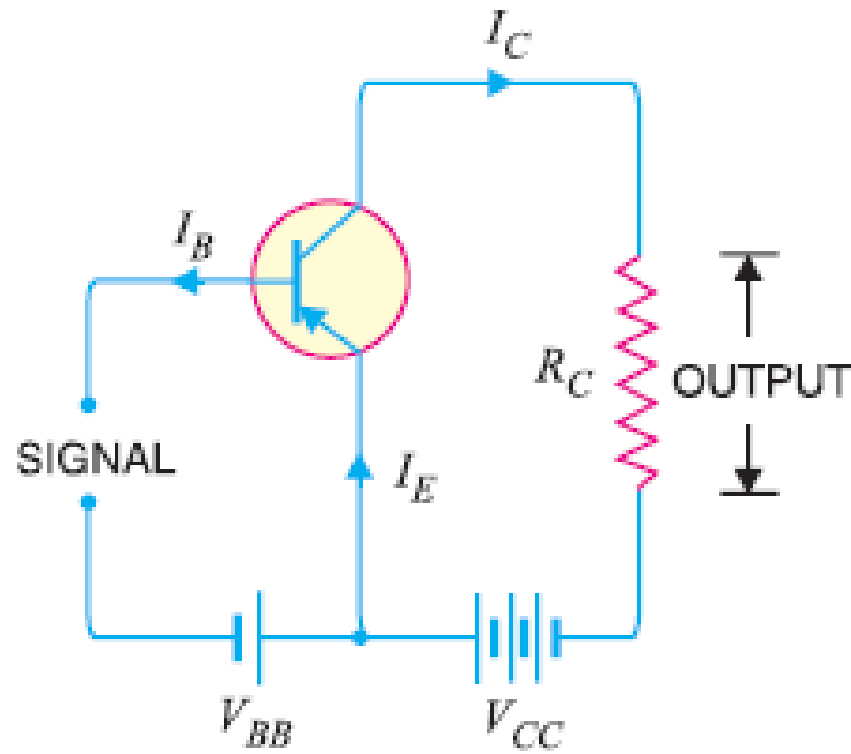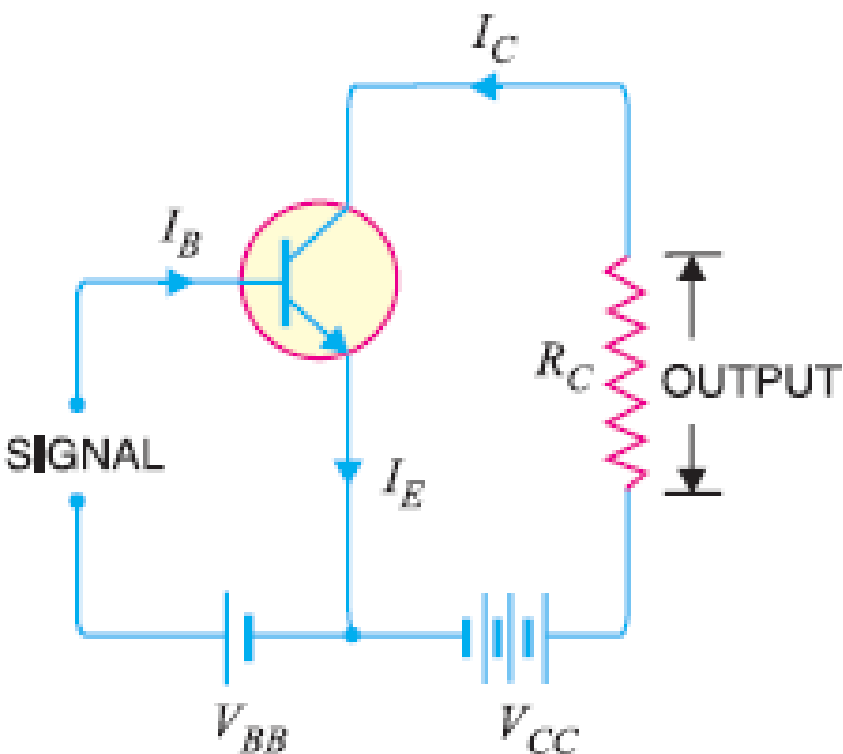
# Common Emitter Connection

In this circuit arrangement, input is applied between base and emitter and output is taken from the collector and emitter. Here, emitter of the transistor is common to both input and output circuits and hence the name common emitter connection. Fig. 8.16 (i) shows common emitter *npn* transistor circuit whereas Fig. 8.16 (ii) shows common emitter *pnp* transistor circuit.



# Base current amplification factor ( $\beta$ )

**1. Base current amplification factor ( $\beta$ ).** In common emitter connection, input current is  $I_B$  and output current is  $I_C$ .

*The ratio of change in collector current ( $\Delta I_C$ ) to the change in base current ( $\Delta I_B$ ) is known as base current amplification factor i.e.*

$$\beta^* = \frac{\Delta I_C}{\Delta I_B}$$

**Relation between  $\beta$  and  $\alpha$ .** A simple relation exists between  $\beta$  and  $\alpha$ . This can be derived as follows :

$$\beta = \frac{\Delta I_C}{\Delta I_B} \quad \dots(i)$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \quad \dots(ii)$$

Now

$$I_E = I_B + I_C$$

or

$$\Delta I_E = \Delta I_B + \Delta I_C$$

or

$$\Delta I_B = \Delta I_E - \Delta I_C$$

Substituting the value of  $\Delta I_B$  in exp. (i), we get,

$$\beta = \frac{\Delta I_C}{\Delta I_E - \Delta I_C} \quad \dots(iii)$$


Dividing the numerator and denominator of R.H.S. of exp. (iii) by  $\Delta I_E$ , we get,

$$\beta = \frac{\frac{\Delta I_C}{\Delta I_E}}{\frac{\Delta I_E}{\Delta I_E} - \frac{\Delta I_C}{\Delta I_E}} = \frac{\alpha}{1 - \alpha} \quad \left[ \because \alpha = \frac{\Delta I_C}{\Delta I_E} \right]$$

$\therefore$

$$\beta = \frac{\alpha}{1 - \alpha}$$

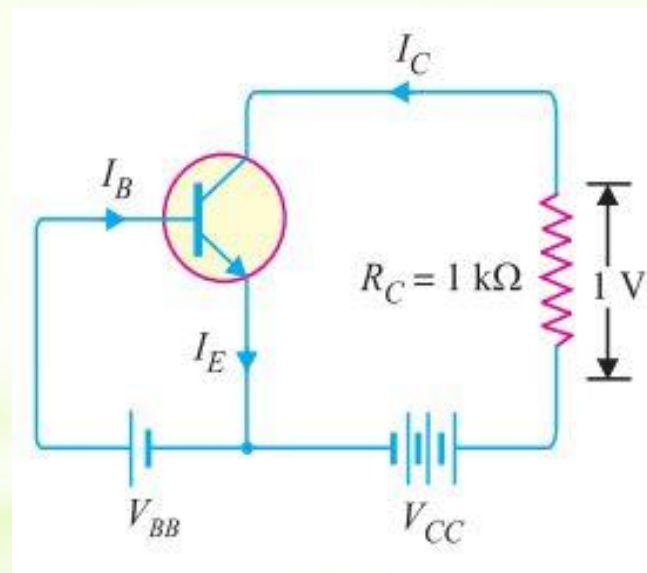**Example 8.11.** For a transistor,  $\beta = 45$  and voltage drop across  $1\text{k}\Omega$  which is connected in the collector circuit is 1 volt. Find the base current for common emitter connection.






**Example 8.11.** For a transistor,  $\beta = 45$  and voltage drop across  $1\text{ k}\Omega$  which is connected in the collector circuit is 1 volt. Find the base current for common emitter connection.

**Solution.** Fig. 8.21 shows the required common emitter connection. The voltage drop across  $R_C (= 1\text{ k}\Omega)$  is 1 volt.

$$\therefore I_C = \frac{1\text{ V}}{1\text{ k}\Omega} = 1\text{ mA}$$

$$\text{Now } \beta = \frac{I_C}{I_B}$$


$$\therefore I_B = \frac{I_C}{\beta} = \frac{1}{45} = 0.022\text{ mA}$$

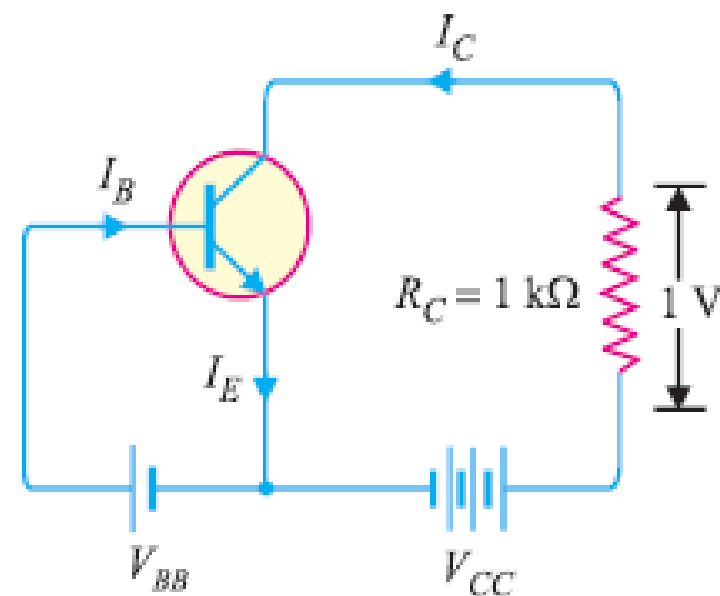

**Fig. 8.21**

**Example 8.12.** A transistor is connected in common emitter (CE) configuration in which collector supply is  $8V$  and the voltage drop across resistance  $R_C$  connected in the collector circuit is  $0.5V$ . The value of  $R_C = 800\ \Omega$ . If  $\alpha = 0.96$ , determine :

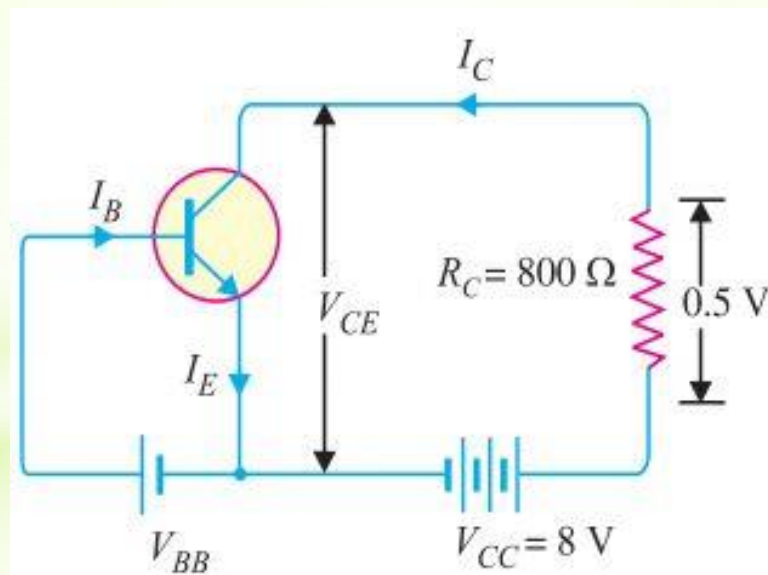- (i) collector-emitter voltage
- (ii) base current



**Example 8.12.** A transistor is connected in common emitter (CE) configuration in which collector supply is 8V and the voltage drop across resistance  $R_C$  connected in the collector circuit is 0.5V. The value of  $R_C = 800\ \Omega$ . If  $\alpha = 0.96$ , determine :

- (i) collector-emitter voltage
- (ii) base current

**Solution.** Fig. 8.22 shows the required common emitter connection with various values.

- (i) Collector-emitter voltage,

$$V_{CE} = V_{CC} - 0.5 = 8 - 0.5 = 7.5\text{ V}$$

- (ii) The voltage drop across  $R_C (= 800\ \Omega)$  is 0.5 V.

$$\therefore I_C = \frac{0.5\text{ V}}{800\ \Omega} = \frac{5}{8}\text{ mA} = 0.625\text{ mA}$$

$$\text{Now } \beta = \frac{\alpha}{1 - \alpha} = \frac{0.96}{1 - 0.96} = 24$$

$$\therefore \text{Base current, } I_B = \frac{I_C}{\beta} = \frac{0.625}{24} = 0.026\text{ mA}$$



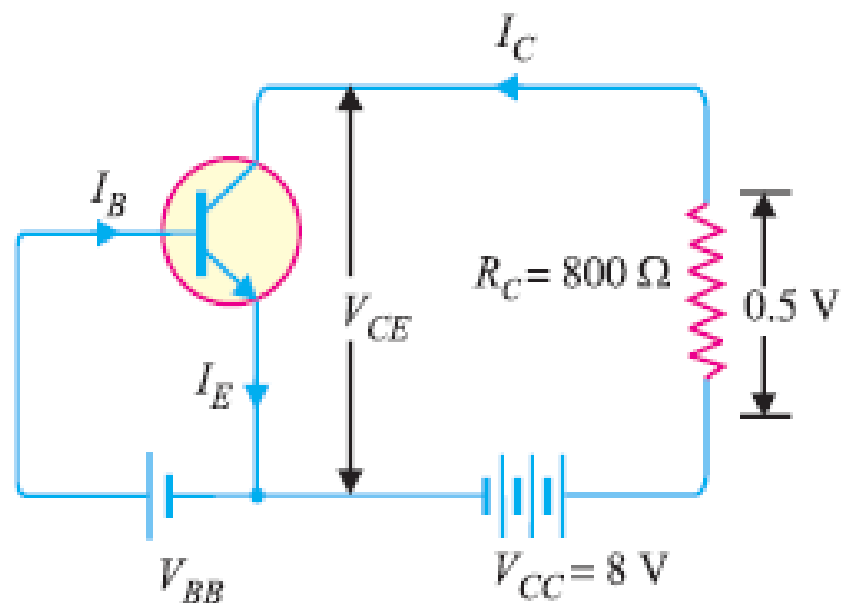


Fig. 8.22

**Example 8.17** Determine  $V_{CB}$  in the transistor \* circuit shown in Fig. 8.26 (i). The transistor is of silicon and has  $\beta = 150$ .

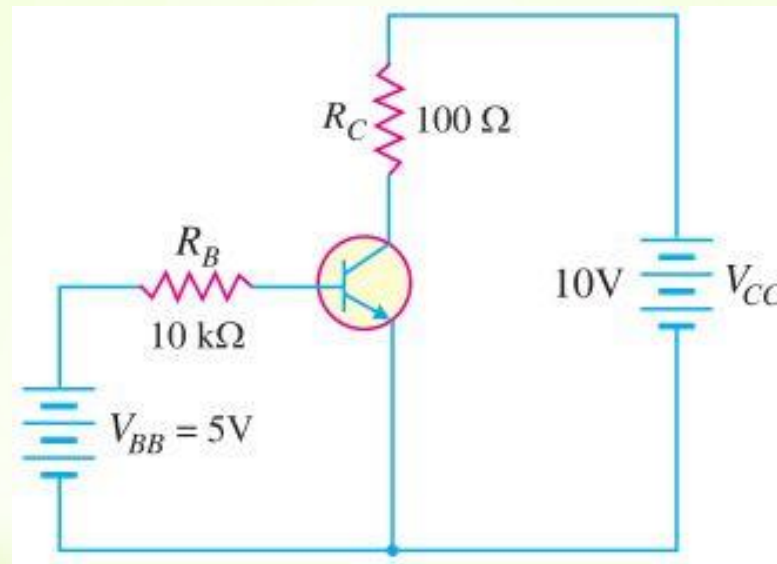

**Example 8.17** Determine  $V_{CB}$  in the transistor \* circuit shown in Fig. 8.26 (i). The transistor is of silicon and has  $\beta = 150$ .

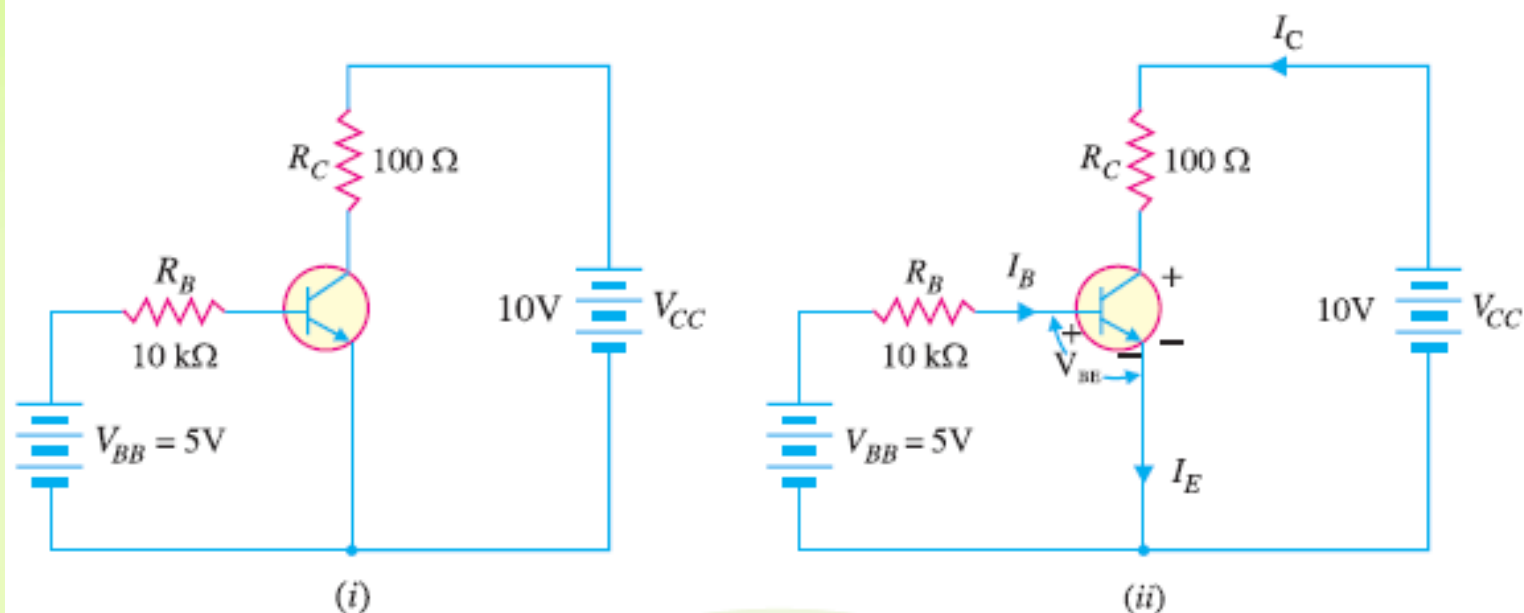

**Fig. 8.26**

**Solution.** Fig. 8.26 (i) shows the transistor circuit while Fig. 8.26 (ii) shows the various currents and voltages along with polarities.

Applying Kirchhoff's voltage law to base-emitter loop, we have,

$$V_{BB} - I_B R_B - V_{BE} = 0$$

or 
$$I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{5V - 0.7V}{10 \text{ k}\Omega} = 430 \mu\text{A}$$

$\therefore I_C = \beta I_B = (150)(430 \mu\text{A}) = 64.5 \text{ mA}$


Now 
$$V_{CE} = V_{CC} - I_C R_C$$
$$= 10V - (64.5 \text{ mA})(100\Omega) = 10V - 6.45V = 3.55V$$

We know that :  $V_{CE} = V_{CB} + V_{BE}$

$\therefore V_{CB} = V_{CE} - V_{BE} = 3.55 - 0.7 = \mathbf{2.85V}$
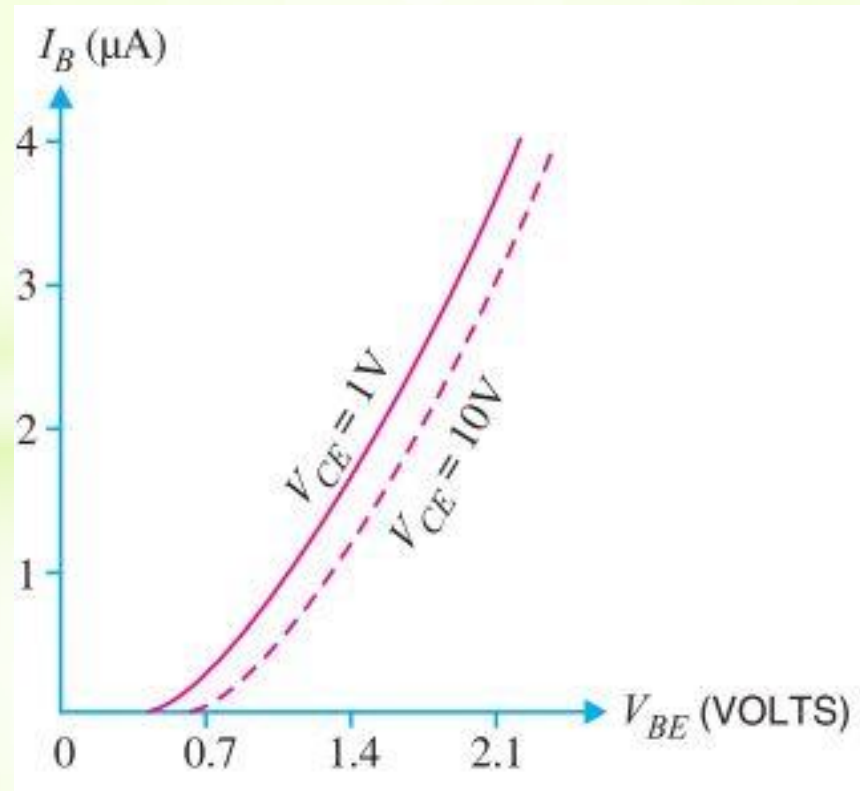
# Characteristics of Common Emitter Connection


**Input characteristic:** It is the curve between base current  $I_B$  and base-emitter voltage  $V_{BE}$  at constant collector-emitter voltage  $V_{CE}$ .






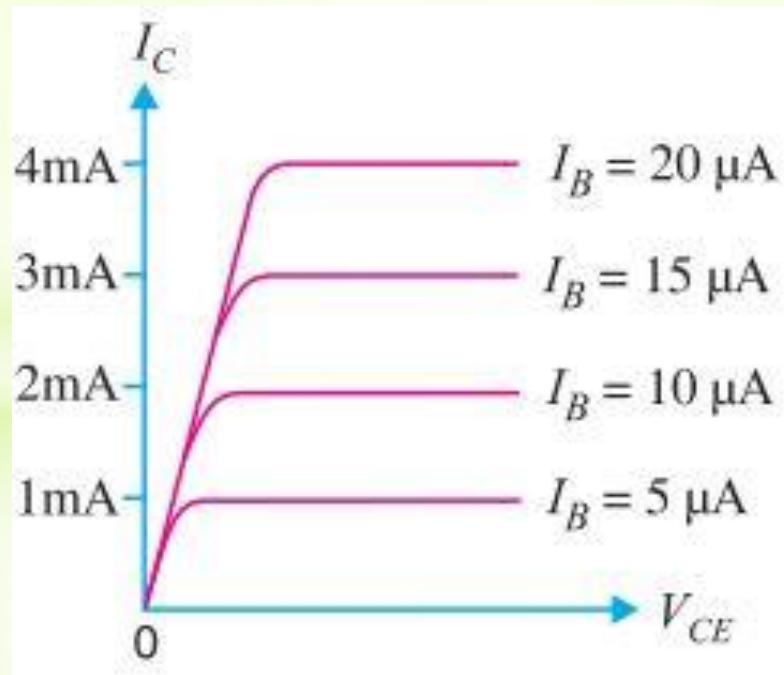
# Characteristics of Common Emitter Connection

**Output characteristic:** It is the curve between collector current  $I_C$  and collector-emitter voltage  $V_{CE}$  at constant base current  $I_B$ .


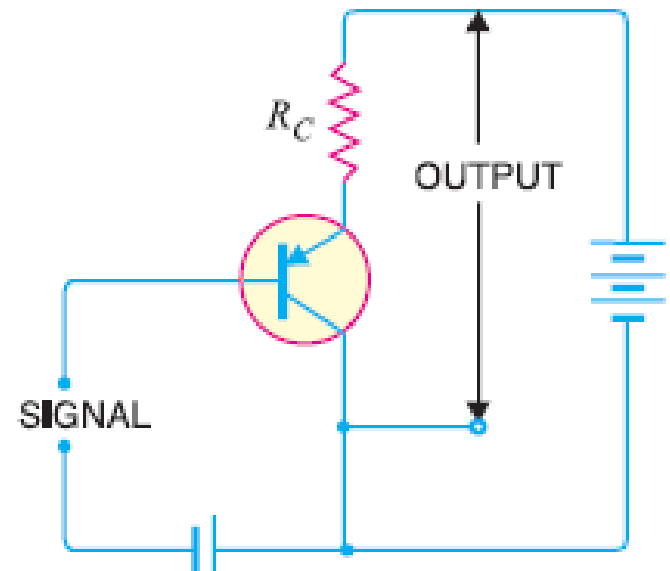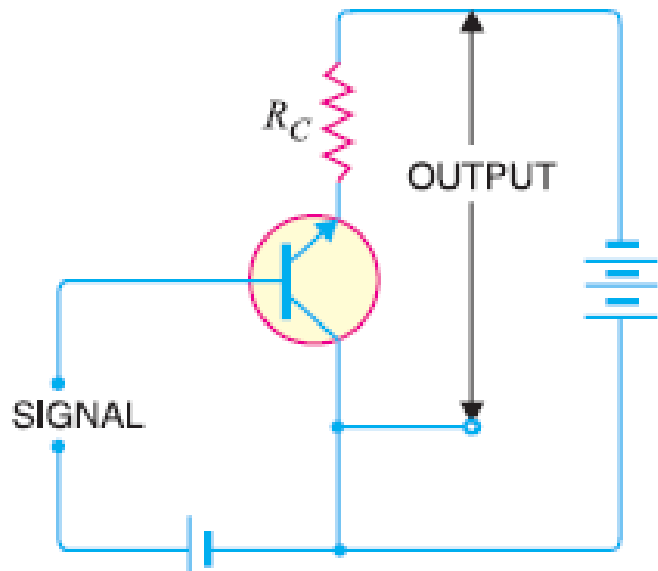
# Common Collector Connection

In this circuit arrangement, input is applied between base and collector while output is taken between the emitter and collector. Here, collector of the transistor is common to both input and output circuits and hence the name common collector connection. Fig. 8.32 (i) shows common collector *npn* transistor circuit whereas Fig. 8.32 (ii) shows common collector *pnp* circuit.



# Current amplification factor $\gamma$

(i) **Current amplification factor  $\gamma$ .** In common collector circuit, input current is the base current  $I_B$  and output current is the emitter current  $I_E$ . Therefore, current amplification in this circuit arrangement can be defined as under :

*The ratio of change in emitter current ( $\Delta I_E$ ) to the change in base current ( $\Delta I_B$ ) is known as **current amplification factor** in common collector (CC) arrangement i.e.*

$$\gamma = \frac{\Delta I_E}{\Delta I_B}$$

### Relation between $\gamma$ and $\alpha$

$$\gamma = \frac{\Delta I_E}{\Delta I_B} \quad \dots(i)$$

$$\alpha = \frac{\Delta I_C}{\Delta I_E} \quad \dots(ii)$$

Now

$$I_E = I_B + I_C$$

or

$$\Delta I_E = \Delta I_B + \Delta I_C$$

or

$$\Delta I_B = \Delta I_E - \Delta I_C$$

Substituting the value of  $\Delta I_B$  in exp. (i), we get,

$$\gamma = \frac{\Delta I_E}{\Delta I_E - \Delta I_C}$$

Dividing the numerator and denominator of R.H.S. by  $\Delta I_E$ , we get,

$$\gamma = \frac{\frac{\Delta I_E}{\Delta I_E}}{\frac{\Delta I_E}{\Delta I_E} - \frac{\Delta I_C}{\Delta I_E}} = \frac{1}{1 - \alpha} \quad \left( \text{Q } \alpha = \frac{\Delta I_C}{\Delta I_E} \right)$$

$\therefore$

$$\gamma = \frac{1}{1 - \alpha}$$

# Comparison of Transistor Connections

S. No.	Characteristic	Common base	Common emitter	Common collector
1.	Input resistance	Low (about 100 $\Omega$ )	Low (about 750 $\Omega$ )	Very high (about 750 k $\Omega$ )
2.	Output resistance	Very high (about 450 k $\Omega$ )	High (about 45 k $\Omega$ )	Low (about 50 $\Omega$ )
3.	Voltage gain	about 150	about 500	less than 1
4.	Applications	For high frequency applications	For audio frequency applications	For impedance matching
5.	Current gain	No (less than 1)	High ( $\beta$ )	Appreciable

# Transistor as Switch

When using BJT as a switch, usually two levels of control signal are employed. With one level, the transistor operates in the cut-off region (open) whereas with the other level, it operates in the saturation region and acts as a short-circuit. Fig. 57.44 (b) shows the condition when control signal  $v_i = 0$ . In this case, the  $BE$  junction is reverse-biased and the transistor is open and, hence acts as an open switch. However, as shown in Fig. 57.44 (c) if  $v_i$  equals a positive voltage of sufficient magnitude to produce saturation *i.e.* if  $v_i = v_i$  the transistor acts as a closed switch.

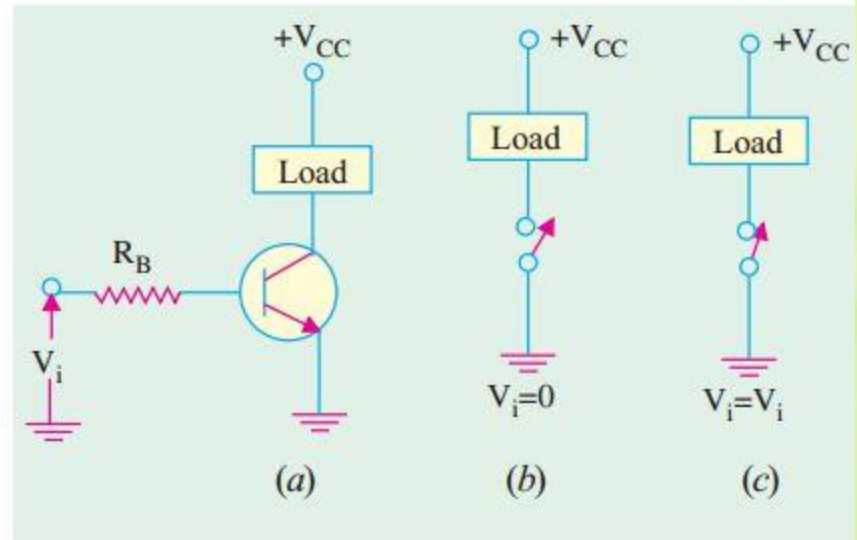


Fig. 57.44



# Applications of BJT

- **Logic circuits**
- **Switch**
- **Amplifier**
- **Oscillator**
- **Multivibrator**
- **Modulator**
- **Demodulator**
- **Time delay circuit**