

CSE-1102

Analog Electronics





Shishir Mallick

Lecturer

Dept. of CSE

Bangladesh University

CE Transistor Characteristics

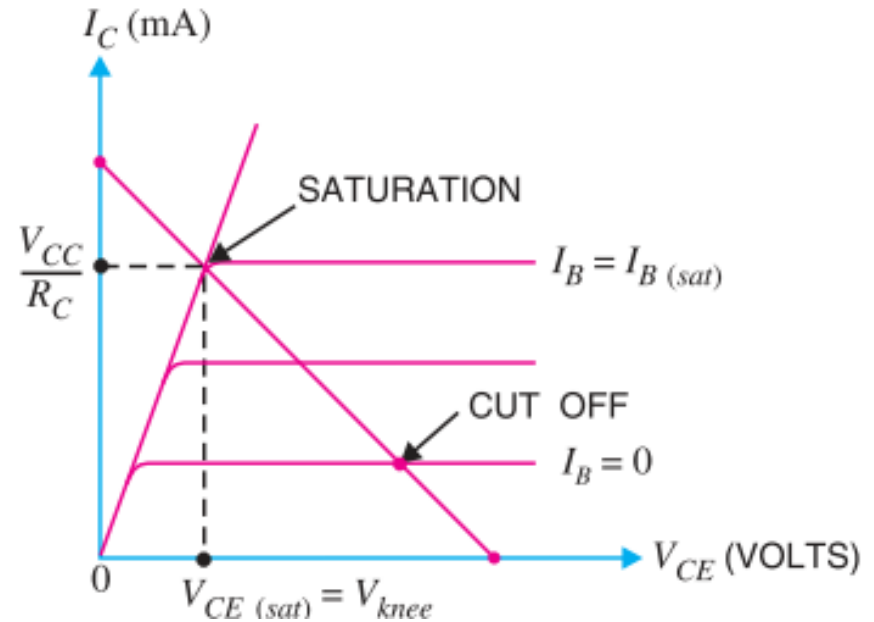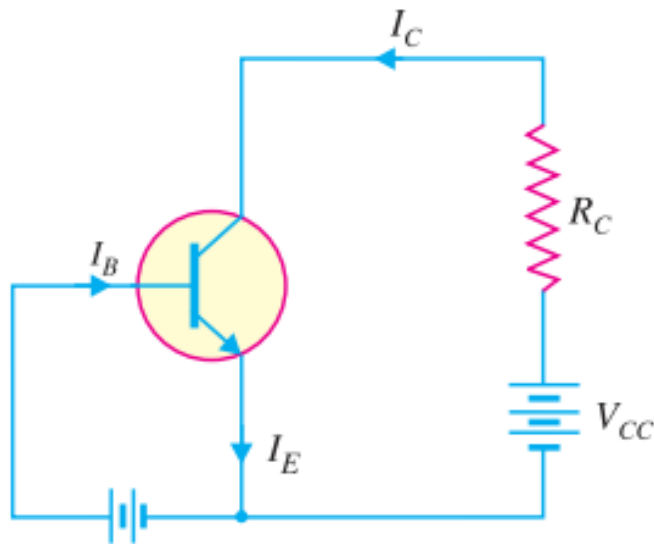




Cut off: The point where the load line intersects the $I_B = 0$ curve is known as cut off. At cut off, the base-emitter junction no longer remains forward biased and normal transistor action is lost.

$$V_{CE(\text{cut off})} = V_{CC}$$


Saturation: The point where the load line intersects the $I_B = I_{B(\text{sat})}$ curve is called saturation. At this point, the base current is maximum and so is the collector current. At saturation, collector-base junction no longer remains reverse biased and normal transistor action is lost.

Active region: The region between cut off and saturation is known as active region. In the active region, collector-base junction remains reverse biased while base-emitter junction remains forward biased. Consequently, the transistor will function normally in this region.


CE Transistor Characteristics

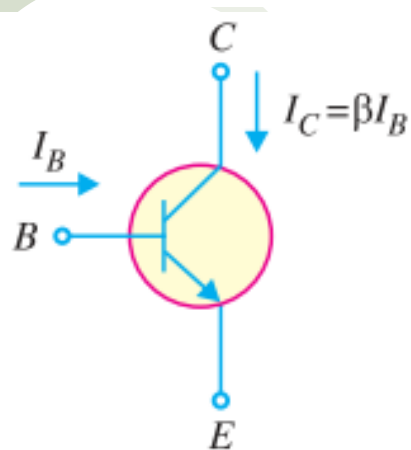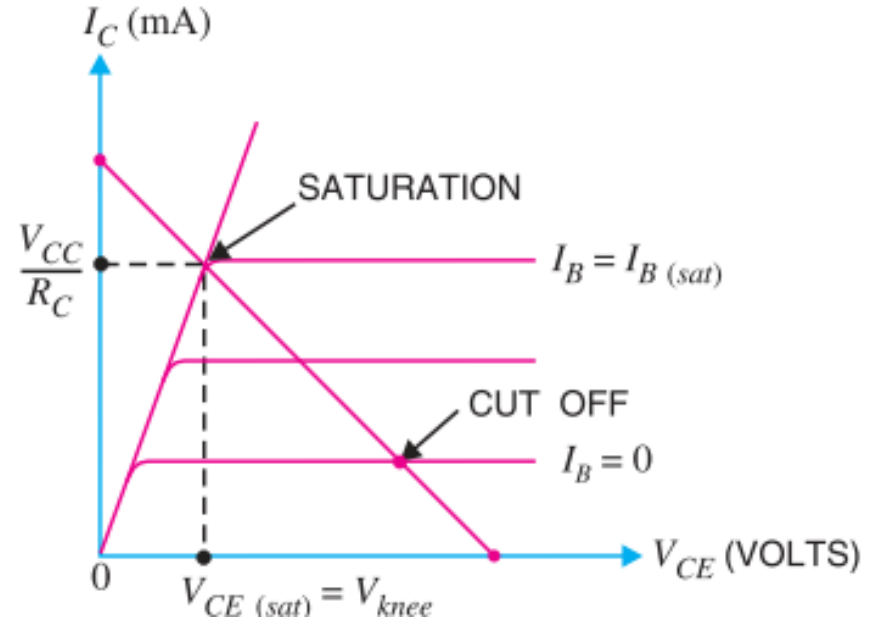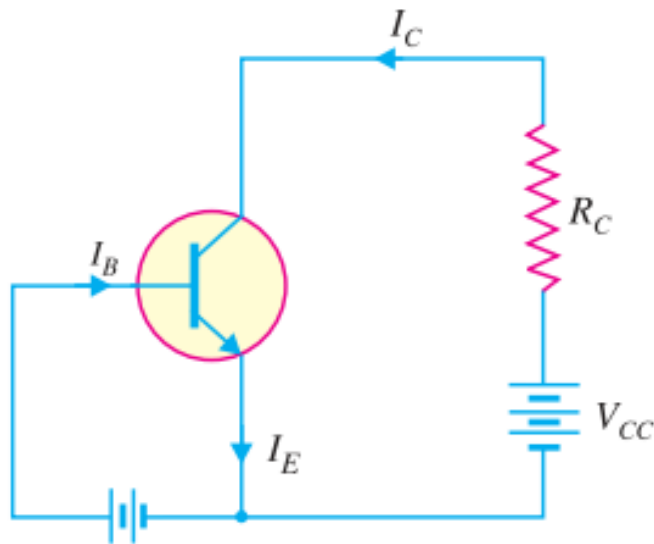

(i) ACTIVE

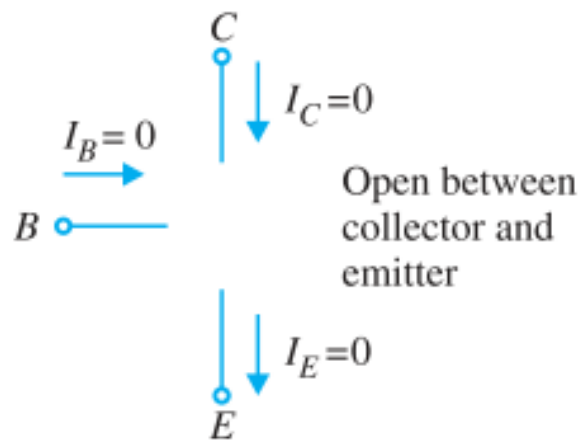


(ii) CUT-OFF

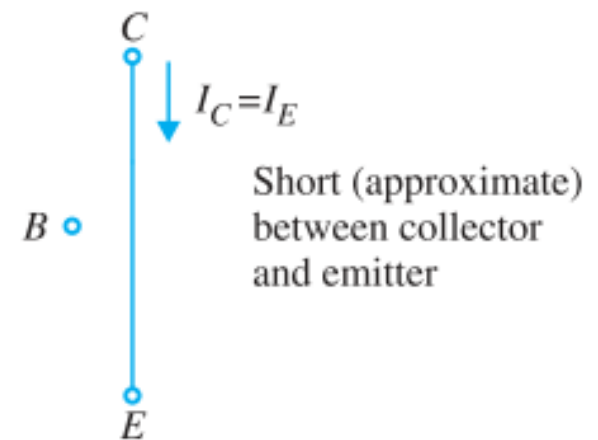

(iii) SATURATED

Example 8.32. Determine the values of $V_{CE(off)}$ and $I_{C(sat)}$ for the circuit shown in Fig. 8.53.

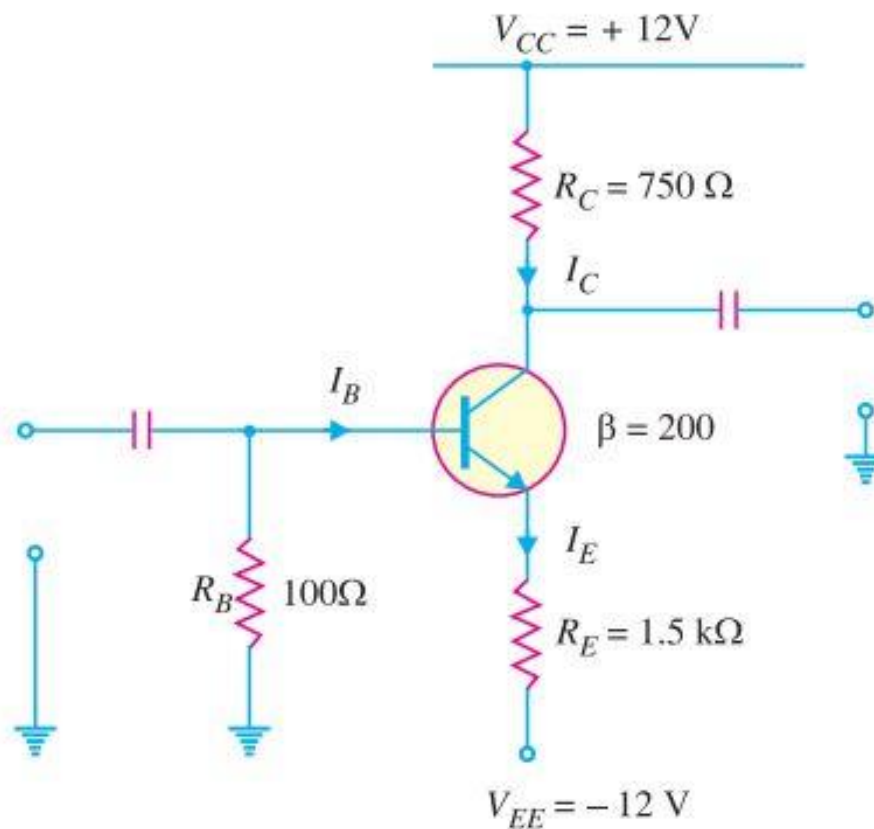

Example 8.32. Determine the values of $V_{CE(off)}$ and $I_{C(sat)}$ for the circuit shown in Fig. 8.53.

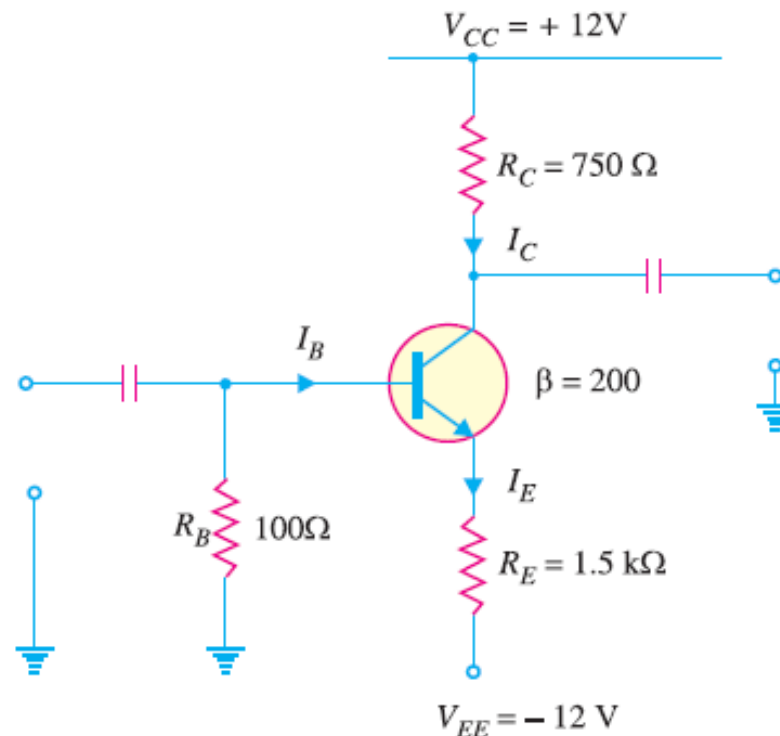


Fig. 8.53

Solution. Applying Kirchhoff's voltage law to the collector side of the circuit in Fig. 8.53, we have,

$$V_{CC} - I_C R_C - V_{CE} - I_C R_E + V_{EE} = 0$$

$$\text{or} \quad V_{CE} = V_{CC} + V_{EE} - I_C (R_C + R_E) \quad \dots (i)$$

We have $V_{CE(off)}$ when $I_C = 0$. Therefore, putting $I_C = 0$ in eq. (i), we have,


$$V_{CE(off)} = V_{CC} + V_{EE} = 12 + 12 = \mathbf{24V}$$

We have $I_{C(sat)}$ when $V_{CE} = 0$.


$$\therefore I_{C(sat)} = \frac{V_{CC} + V_{EE}}{R_C + R_E} = \frac{(12 + 12)V}{(750 + 1500)\Omega} = \mathbf{10.67\text{ mA}}$$

Problem

Example 8.33. Determine whether or not the transistor in Fig. 8.54 is in saturation. Assume $V_{knee} = 0.2V$.

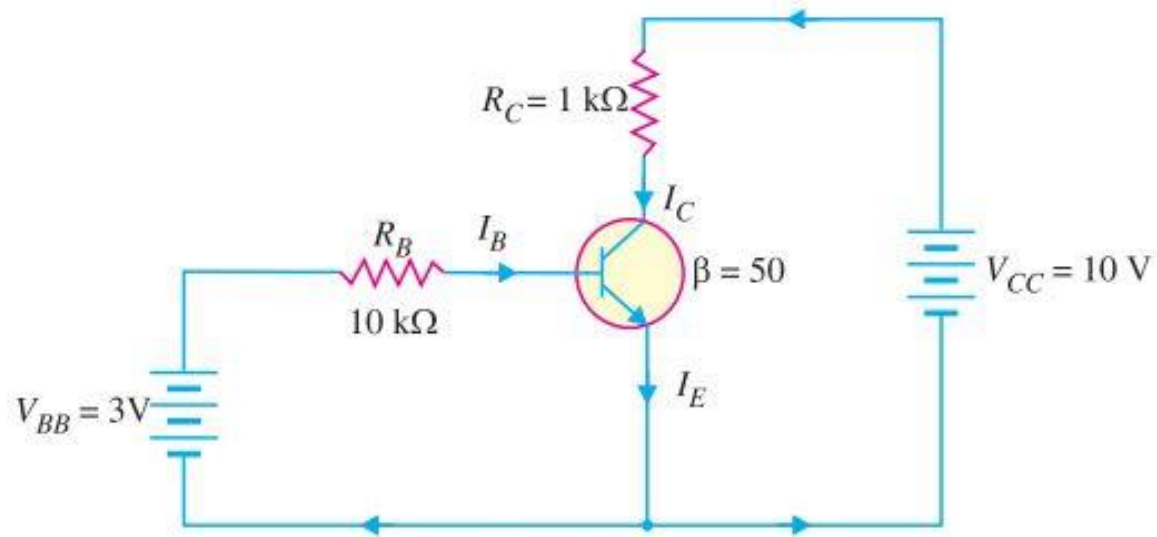

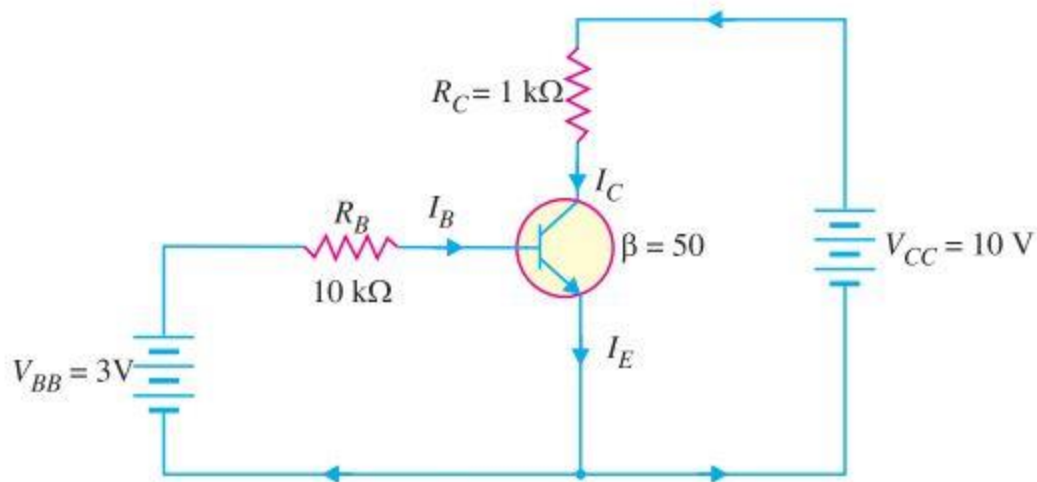Example 8.33. Determine whether or not the transistor in Fig. 8.54 is in saturation. Assume $V_{knee} = 0.2V$.



$$I_{C(sat)} = \frac{V_{CC} - V_{knee}}{R_C} = \frac{10V - 0.2V}{1k\Omega} = \frac{9.8V}{1k\Omega} = 9.8 \text{ mA}$$

Now we shall see if I_B is large enough to produce $I_{C(sat)}$.


$$\text{Now } I_B = \frac{V_{BB} - V_{BE}}{R_B} = \frac{3V - 0.7V}{10k\Omega} = \frac{2.3V}{10k\Omega} = 0.23 \text{ mA}$$

$$\therefore I_C = \beta I_B = 50 \times 0.23 = 11.5 \text{ mA}$$

This shows that with specified β , this base current ($= 0.23 \text{ mA}$) is capable of producing I_C greater than $I_{C(sat)}$. Therefore, the transistor is **saturated**. In fact, the collector current value of 11.5 mA is never reached. If the base current value corresponding to $I_{C(sat)}$ is increased, the collector current remains at the saturated value ($= 9.8 \text{ mA}$).

Problem

Example 8.35. For the circuit in Fig. 8.57, find the base supply voltage (V_{BB}) that just puts the transistor into saturation. Assume $\beta = 200$.

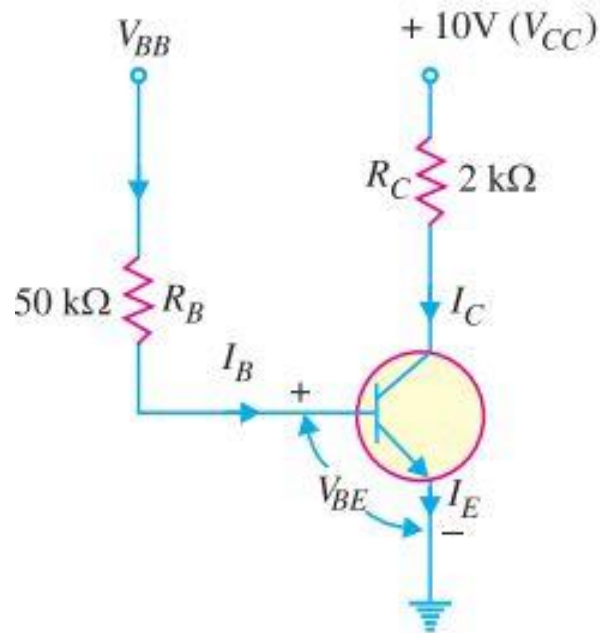

Example 8.35. For the circuit in Fig. 8.57, find the base supply voltage (V_{BB}) that just puts the transistor into saturation. Assume $\beta = 200$.

Solution. When transistor first goes into saturation, we can assume that the collector shorts to the emitter (i.e. $V_{CE} = 0$) but the collector current is still β times the base current.

$$\begin{aligned} I_{C(sat)} &= \frac{V_{CC} - V_{CE}}{R_C} = \frac{V_{CC} - 0}{R_C} \\ &= \frac{10\text{ V} - 0}{2\text{ k}\Omega} = 5\text{ mA} \end{aligned}$$

The base current I_B corresponding to $I_{C(sat)}$ ($=5\text{ mA}$) is

$$I_B = \frac{I_{C(sat)}}{\beta} = \frac{5\text{ mA}}{200} = 0.025\text{ mA}$$

Applying Kirchhoff's voltage law to the base circuit, we have,

$$V_{BB} - I_B R_B - V_{BE} = 0$$

$$\begin{aligned} \text{or } V_{BB} &= V_{BE} + I_B R_B \\ &= 0.7\text{ V} + 0.025\text{ mA} \times 50\text{ k}\Omega = 0.7 + 1.25 = 1.95\text{ V} \end{aligned}$$

Therefore, for $V_{BB} \geq 1.95$, the transistor will be in *saturation*.


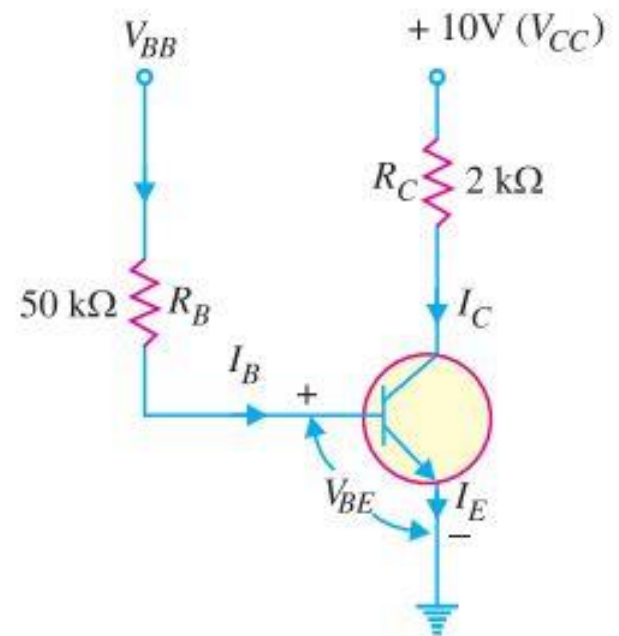


Fig. 8.57

Problem

Example. 8.36. Determine the state of the transistor in Fig. 8.58 for the following values of collector resistor :

- (i) $R_C = 2\text{ k}\Omega$ (ii) $R_C = 4\text{ k}\Omega$ (iii) $R_C = 8\text{ k}\Omega$

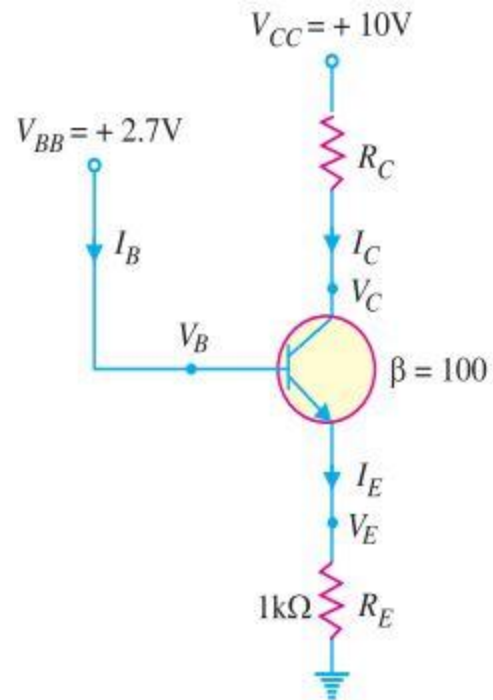

Example. 8.36. Determine the state of the transistor in Fig. 8.58 for the following values of collector resistor :

(i) $R_C = 2 \text{ k}\Omega$ (ii) $R_C = 4 \text{ k}\Omega$ (iii) $R_C = 8 \text{ k}\Omega$

Solution. Since I_E does not depend on the value of the collector resistor R_C , the emitter current (I_E) is the same for all three parts.

$$\begin{aligned}\text{Emitter voltage, } V_E &= V_B - V_{BE} = V_{BB} - V_{BE} \\ &= 2.7\text{V} - 0.7\text{V} = 2\text{V}\end{aligned}$$

Also
$$I_E = \frac{V_E}{R_E} = \frac{2\text{V}}{1 \text{ k}\Omega} = 2 \text{ mA}$$

(i) When $R_C = 2 \text{ k}\Omega$. Suppose the transistor is active.

$$\therefore I_C = I_E = 2 \text{ mA}$$

$$\therefore I_B = I_C / \beta = 2 \text{ mA} / 100 = 0.02 \text{ mA}$$

$$\begin{aligned}\text{Collector voltage, } V_C &= V_{CC} - I_C R_C \\ &= 10\text{V} - 2\text{ mA} \times 2\text{ k}\Omega = 10\text{V} - 4\text{V} = 6\text{V}\end{aligned}$$

Since $V_C (= 6\text{V})$ is greater than $V_E (= 2\text{V})$, the transistor is **active**. Therefore, our assumption that transistor is active is correct.

(ii) When $R_C = 4\text{ k}\Omega$. Suppose the transistor is active.

$$\begin{aligned}\therefore \quad I_C &= 2\text{mA and } I_B = 0.02\text{ mA ... as found above} \\ \text{Collector voltage, } V_C &= V_{CC} - I_C R_C \\ &= 10\text{V} - 2\text{ mA} \times 4\text{ k}\Omega = 10\text{V} - 8\text{V} = 2\text{V}\end{aligned}$$

Since $V_C = V_E$, the transistor is just at the edge of **saturation**. We know that at the edge of saturation, the relation between the transistor currents is the same as in the **active state**. Both answers are correct.

(iii) When $R_C = 8\text{ k}\Omega$. Suppose the transistor is active.

$$\begin{aligned}\therefore \quad I_C &= 2\text{mA} ; I_B = 0.02\text{ mA ... as found earlier.} \\ \text{Collector voltage, } V_C &= V_{CC} - I_C R_C \\ &= 10\text{V} - 2\text{ mA} \times 8\text{ k}\Omega = 10\text{V} - 16\text{V} = -6\text{V}\end{aligned}$$

Since $V_C < V_E$, the transistor is **saturated** and our assumption is not correct.

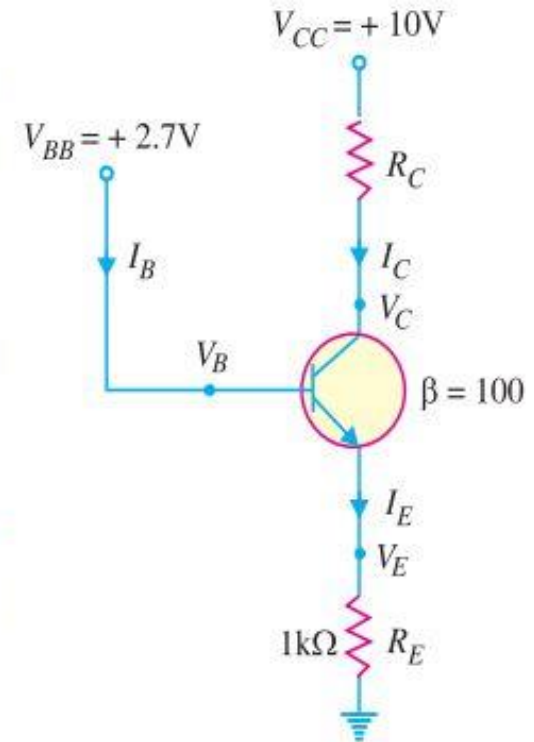



Fig. 8.58

Problem

Example 8.37. In the circuit shown in Fig. 8.59, V_{BB} is set equal to the following values :

(i) $V_{BB} = 0.5V$ (ii) $V_{BB} = 1.5V$ (iii) $V_{BB} = 3V$

Determine the state of the transistor for each value of the base supply voltage V_{BB} .

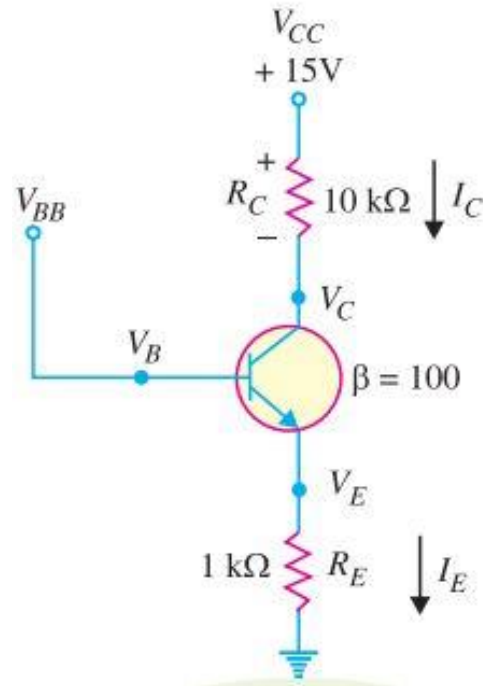

Example 8.37. In the circuit shown in Fig. 8.59, V_{BB} is set equal to the following values :

(i) $V_{BB} = 0.5V$ (ii) $V_{BB} = 1.5V$ (iii) $V_{BB} = 3V$

Determine the state of the transistor for each value of the base supply voltage V_{BB} .

Solution. The state of the transistor also depends on the base supply voltage V_{BB} .

(i) For $V_{BB} = 0.5V$

Because the base voltage $V_B (= V_{BB} = 0.5V)$ is less than $0.7V$, the transistor is **cut-off**.

(ii) For $V_{BB} = 1.5V$

The base voltage V_B controls the emitter voltage V_E which controls the emitter current I_E .

$$\text{Now } V_E = V_B - 0.7V = 1.5V - 0.7V = 0.8V$$

$$\therefore I_E = \frac{V_E}{R_E} = \frac{0.8V}{1k\Omega} = 0.8\text{ mA}$$

If the transistor is active, we have,

$$I_C = I_E = 0.8\text{ mA and } I_B = I_C/\beta = 0.8/100 = 0.008\text{ mA}$$

$$\therefore \text{ Collector voltage, } V_C = V_{CC} - I_C R_C$$

$$= 15V - 0.8\text{ mA} \times 10k\Omega = 15V - 8V = 7V$$

Since $V_C > V_E$, the transistor is **active** and our assumption is correct.

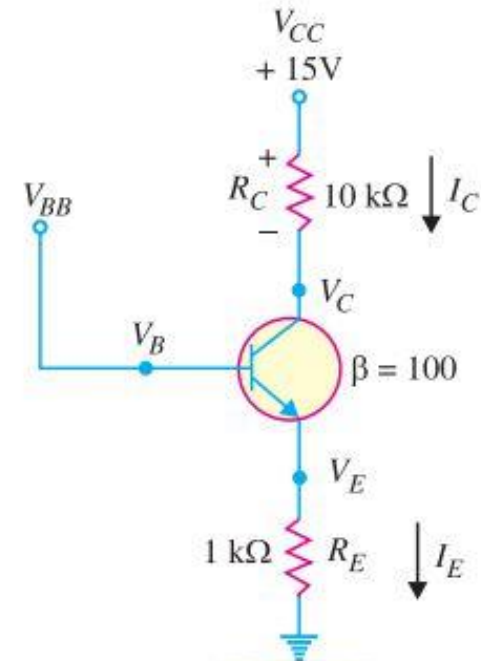


Fig. 8.59

(iii) For $V_{BB} = 3V$

$$V_E = V_B - 0.7V = 3V - 0.7V = 2.3V$$

$$\therefore I_E = \frac{V_E}{R_E} = \frac{2.3V}{1k\Omega} = 2.3 \text{ mA}$$




Assuming the transistor is active, we have,

$$I_C = I_E = 2.3 \text{ mA} \quad ; \quad I_B = I_C / \beta = 2.3 / 100 = 0.023 \text{ mA}$$

$$\begin{aligned} \text{Collector voltage, } V_C &= V_{CC} - I_C R_C \\ &= 15V - 2.3 \text{ mA} \times 10 \text{ k}\Omega = 15V - 23V = -8V \end{aligned}$$

Since $V_C < V_E$, the transistor is **saturated** and our assumption is not correct.

Transistor Lead Identification

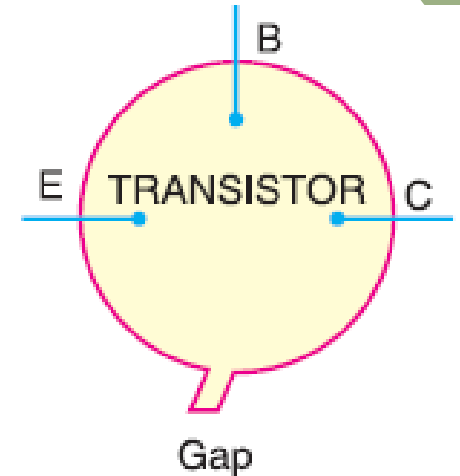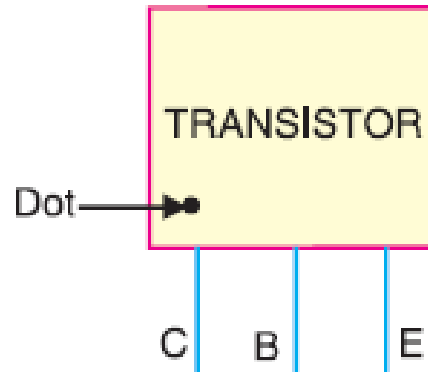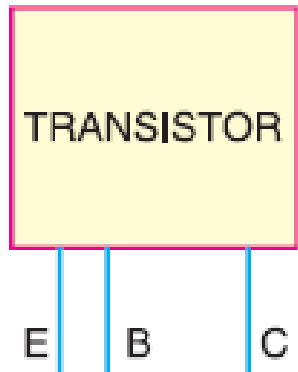

- ❖ **When the leads of a transistor are in the same plane and unevenly spaced,** The central lead is the base lead. The collector lead is identified by the larger spacing existing between it and the base lead. The remaining lead is the emitter.
- ❖ **When the leads of a transistor are in the same plane but evenly spaced,** the central lead is the base, the lead identified by dot is the collector and the remaining lead is the emitter.
- ❖ **When the leads of a transistor are spaced around the circumference of a circle,** the three leads are generally in E-B-C order clockwise from a gap.

Thank You All