

CSE-1102

Analog Electronics



Outlines

- ❖ Transistor Biasing
- ❖ Methods of Transistor Biasing

Transistor Biasing

The proper flow of zero signal collector current and the maintenance of proper collector emitter voltage during the passage of signal is known as transistor biasing.

Essentials of a Transistor Biasing Circuit:


- a) It should ensure proper zero signal collector current.
- b) It should ensure that V_{CE} does not fall below 0.5 V for Ge transistors and 1 V for silicon transistors at any instant.
- c) It should ensure the stabilization of operating point.

Methods of Transistor Biasing

- (i) Base resistor method
- (ii) Emitter bias method
- (iii) Biasing with collector-feedback resistor
- (iv) Voltage-divider bias


(i) Base Resistor Method

- ❖ A high resistance R_B is connected between the base and +ve end of supply for npn transistor.
- ❖ The required value of zero signal base current I_B can be made to flow by selecting the proper value of base resistor R_B .

 

Problem 14.1

Example 9.6. Calculate the values of three currents in the circuit shown in Fig. 9.9.

 

Example 9.6. Calculate the values of three currents in the circuit shown in Fig. 9.9.

Solution. Applying Kirchhoff's voltage law to the base side and taking resistances in $k\Omega$ and currents in mA, we have,

 


Fig. 9.9

$$V_{CC} = I_B R_B + V_{BE} + I_E \times 1$$

or $10 = 1000 I_B + 0 + (I_C + I_B)$

or $10 = 1000 I_B + (\beta I_B + I_B)$

or $10 = 1000 I_B + (100 I_B + I_B)$

or $10 = 1101 I_B$

$\therefore I_B = 10/1101 = 0.0091 \text{ mA}$

$$I_C = \beta I_B = 100 \times 0.0091 = 0.91 \text{ mA}$$

$$I_E = I_C + I_B = 0.91 + 0.0091 = 0.919 \text{ mA}$$

Problem 14.2

Example 9.7. Design base resistor bias circuit for a CE amplifier such that operating point is $V_{CE} = 8V$ and $I_C = 2\text{ mA}$. You are supplied with a fixed $15V$ d.c. supply and a silicon transistor with $\beta = 100$. Take base-emitter voltage $V_{BE} = 0.6V$. Calculate also the value of load resistance that would be employed.

Example 9.7. Design base resistor bias circuit for a CE amplifier such that operating point is $V_{CE} = 8V$ and $I_C = 2\text{ mA}$. You are supplied with a fixed $15V$ d.c. supply and a silicon transistor with $\beta = 100$. Take base-emitter voltage $V_{BE} = 0.6V$. Calculate also the value of load resistance that would be employed.

Solution. Fig. 9.10 shows CE amplifier using base resistor method of biasing.

$$V_{CC} = 15\text{ V} ; \beta = 100 ; V_{BE} = 0.6\text{ V}$$

$$V_{CE} = 8\text{ V} ; I_C = 2\text{ mA} ; R_C = ? ; R_B = ?$$

$$V_{CC} = V_{CE} + I_C R_C$$

or

$$15\text{ V} = 8\text{ V} + 2\text{ mA} \times R_C$$

\therefore


$$R_C = \frac{(15 - 8)\text{ V}}{2\text{ mA}} = \mathbf{3.5\text{ k}\Omega}$$

$$I_B = I_C / \beta = 2 / 100 = 0.02\text{ mA}$$

$$V_{CC} = I_B R_B + V_{BE}$$


\therefore

$$R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{(15 - 0.6)\text{ V}}{0.02\text{ mA}} = \mathbf{720\text{ k}\Omega}$$

 


Problem 14.3

 Example 9.10. Fig. 9.13 (i) shows the base resistor transistor circuit. The device (i.e. transistor) has the characteristics shown in Fig. 9.13 (ii). Determine V_{CC} , R_C and R_B .



(i)

 

(ii)

Example 9.10. Fig. 9.13 (i) shows the base resistor transistor circuit. The device (i.e. transistor) has the characteristics shown in Fig. 9.13 (ii). Determine V_{CC} , R_C and R_B .

 


Fig. 9.13

Solution. From the d.c load line, $V_{CC} = 20\text{V}$.

$$\text{Max. } I_C = \frac{V_{CC}}{R_C} \text{ (when } V_{CE} = 0\text{V)}$$


$$\therefore R_C = \frac{V_{CC}}{\text{Max. } I_C} = \frac{20\text{V}}{8\text{mA}} = 2.5 \text{ k}\Omega$$

$$\text{Now } I_B = \frac{V_{CC} - V_{BE}}{R_B}$$

$$\therefore R_B = \frac{V_{CC} - V_{BE}}{I_B} = \frac{20\text{V} - 0.7\text{V}}{40 \mu\text{A}} = \frac{19.3\text{V}}{40 \mu\text{A}} = 482.5 \text{ k}\Omega$$


(ii) Emitter Bias Circuit

Fig. 9.15 shows the emitter bias circuit. This circuit differs from base-bias circuit in two important respects. First, it uses two separate d.c. voltage sources ; one positive ($+V_{CC}$) and the other negative ($-V_{EE}$). Normally, the two supply voltages will be equal. For example, if $V_{CC} = +20\text{V}$ (d.c.), then $V_{EE} = -20\text{V}$ (d.c.). Secondly, there is a resistor R_E in the emitter circuit.

 

Problem 14.4

Example 9.12. For the emitter bias circuit shown in Fig. 9.18, find I_E , I_C , V_C and V_{CE} for $\beta = 85$ and $V_{BE} = 0.7V$.

 

Example 9.12. For the emitter bias circuit shown in Fig. 9.18, find I_E , I_C , V_C and V_{CE} for $\beta = 85$ and $V_{BE} = 0.7V$.

$$-I_B R_B - V_{BE} - I_E R_E + V_{EE} = 0$$

$$V_{EE} = I_B R_B + V_{BE} + I_E R_E$$

Now $I_C \simeq I_E$ and $I_C = \beta I_B \therefore I_B \simeq \frac{I_E}{\beta}$

Putting $I_B = I_E/\beta$ in the above equation,

$$V_{EE} = \left(\frac{I_E}{\beta} \right) R_B + I_E R_E + V_{BE}$$

or $V_{EE} - V_{BE} = I_E (R_B/\beta + R_E)$

$$\therefore I_E = \frac{V_{EE} - V_{BE}}{R_E + R_B/\beta}$$

Since $I_C \simeq I_E$, we have,

$$I_C = \frac{V_{EE} - V_{BE}}{R_E + R_B/\beta}$$


$$I_C \simeq I_E = \frac{V_{EE} - V_{BE}}{R_E + R_B/\beta} = \frac{20V - 0.7V}{10 \text{ k}\Omega + 100 \text{ k}\Omega/85} = \mathbf{1.73 \text{ mA}}$$

$$V_C = V_{CC} - I_C R_C = 20V - (1.73 \text{ mA}) (4.7 \text{ k}\Omega) = \mathbf{11.9V}$$


$$V_E = -V_{EE} + I_E R_E = -20V + (1.73 \text{ mA}) (10 \text{ k}\Omega) = -2.7V$$

$$\therefore V_{CE} = V_C - V_E = 11.9 - (-2.7V) = \mathbf{14.6V}$$

 Note that operating point (or Q – point) of the circuit is 14.6V, 1.73 mA.




(iii) Biasing with Collector Feedback Resistor

 

Problem 14.5

Example 9.14. Fig. 9.20 shows a silicon transistor biased by collector feedback resistor method. Determine the operating point. Given that $\beta = 100$.

 

Example 9.14. Fig. 9.20 shows a silicon transistor biased by collector feedback resistor method. Determine the operating point. Given that $\beta = 100$.

Solution. $V_{CC} = 20\text{V}$, $R_B = 100\text{ k}\Omega$, $R_C = 1\text{ k}\Omega$

Since it is a silicon transistor, $V_{BE} = 0.7\text{ V}$.

Assuming I_B to be in mA and using the relation,

$$R_B = \frac{V_{CC} - V_{BE} - \beta I_B R_C}{I_B}$$

or $100 \times I_B = 20 - 0.7 - 100 \times I_B \times 1$

or $200 I_B = 19.3$

or $I_B = \frac{19.3}{200} = 0.096\text{ mA}$

\therefore Collector current, $I_C = \beta I_B = 100 \times 0.096 = 9.6\text{ mA}$

Collector-emitter voltage is

$$\begin{aligned} V_{CE} &= V_{CC} - I_C R_C \\ &= 20 - 9.6\text{ mA} \times 1\text{ k}\Omega \\ &= 10.4\text{ V} \end{aligned}$$

\therefore Operating point is **10.4 V, 9.6 mA**.


 


Fig. 9.20

(iv) Voltage-divider bias

 


(iv) Voltage-divider bias


- (i) Two resistors R_1 and R_2 are connected across the supply voltage V_{cc} and provide biasing.
- (ii) The voltage drop across R_2 forward biases the base-emitter junction.
- (iii) This causes the base current and hence collector current flow in the zero signal conditions.

 Problem 14.6

Calculate the emitter current in the voltage divider circuit shown in Fig. Also find the value of V_{CE} and collector potential V_C .



 Calculate the emitter current in the voltage divider circuit shown in Fig. Also find the value of V_{CE} and collector potential V_C .



$$\text{Voltage across } R_2, V_2 = \left(\frac{V_{CC}}{R_1 + R_2} \right) R_2 = \left(\frac{20}{10 + 10} \right) 10 = 10\text{ V}$$

Now $V_2 = V_{BE} + I_E R_E$
 As V_{BE} is generally small, therefore, it can be neglected.

$$\therefore I_E = \frac{V_2}{R_E} = \frac{10\text{ V}}{5\text{ k}\Omega} = \mathbf{2\text{ mA}}$$

$$\begin{aligned} \text{Now } I_C &\simeq I_E = 2\text{ mA} \\ \therefore V_{CE} &= V_{CC} - I_C (R_C + R_E) = 20 - 2\text{ mA} (6\text{ k}\Omega) \\ &= 20 - 12 = \mathbf{8\text{ V}} \end{aligned}$$

$$\begin{aligned} \text{Collector potential, } V_C &= V_{CC} - I_C R_C = 20 - 2\text{ mA} \times 1\text{ k}\Omega \\ &= 20 - 2 = \mathbf{18\text{ V}} \end{aligned}$$



Thank You All