
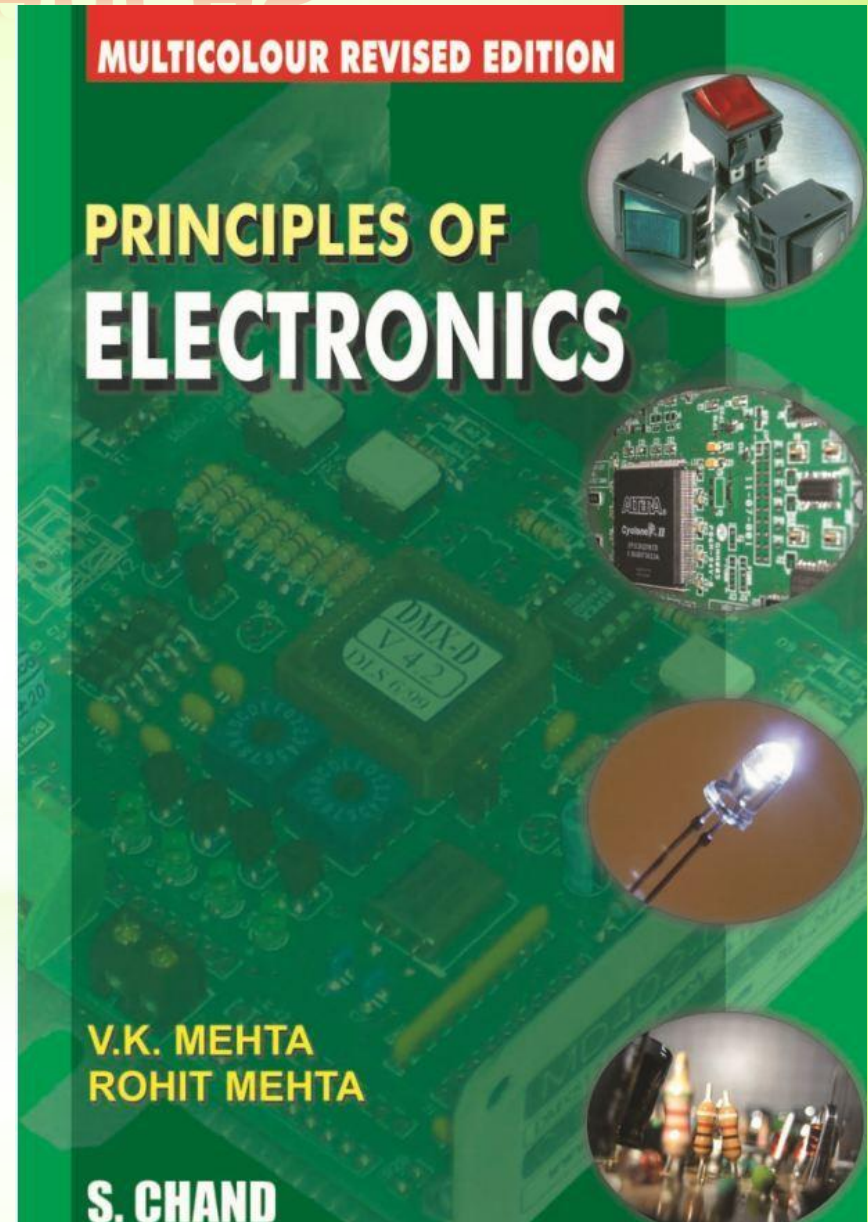


# Analog Electronics

# References

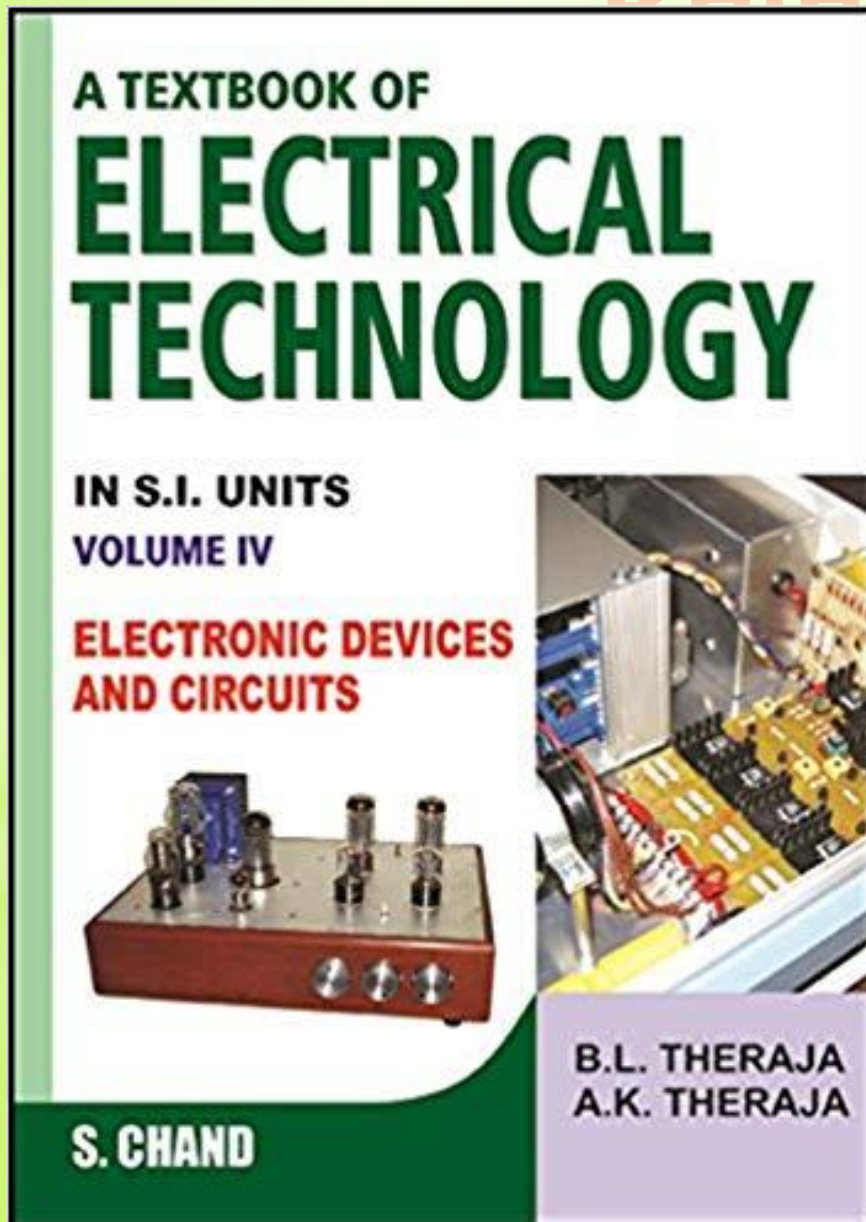

# Transistor Load Line Analysis

The value of collector-emitter voltage  $V_{CE}$  at any time is given by ;

$$V_{CE} = V_{CC} - I_C R_C \quad \dots(i)$$

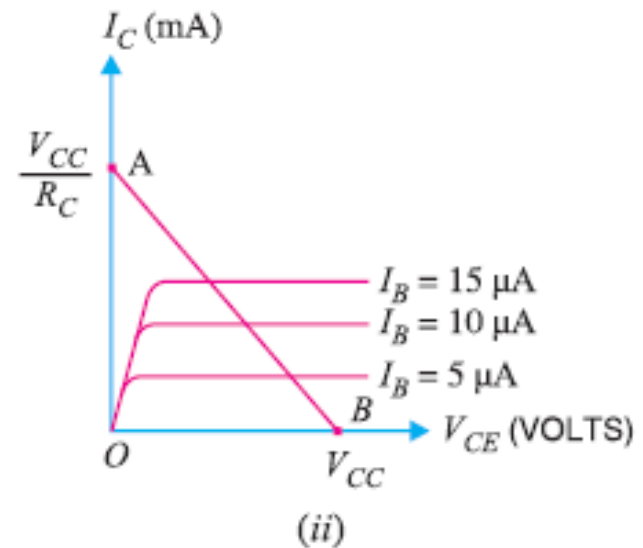
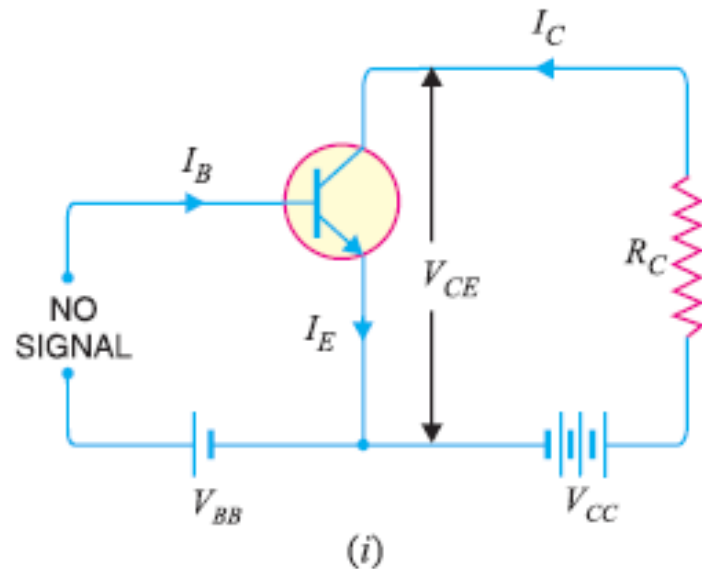


Fig. 8.35

As  $V_{CC}$  and  $R_C$  are fixed values, therefore, it is a first degree equation and can be represented by a straight line on the output characteristics. This is known as *d.c. load line* and determines the locus of  $V_{CE} - I_C$  points for any given value of  $R_C$ . To add load line, we need two end points of the straight line. These two points can be located as under :

(i) When the collector current  $I_C = 0$ , then collector-emitter voltage is maximum and is equal to  $V_{CC}$  i.e.

$$\begin{aligned} \text{Max. } V_{CE} &= V_{CC} - I_C R_C \\ &= V_{CC} \quad (\because I_C = 0) \end{aligned}$$

This gives the first point B ( $OB = V_{CC}$ ) on the collector-emitter voltage axis as shown in Fig. 8.35 (ii).

# Transistor Load Line Analysis

(ii) When collector-emitter voltage  $V_{CE} = 0$ , the collector current is maximum and is equal to  $V_{CC}/R_C$  i.e.

$$V_{CE} = V_{CC} - I_C R_C$$

$$\text{or} \quad 0 = V_{CC} - I_C R_C$$

$$\therefore \quad \text{Max. } I_C = V_{CC}/R_C$$

This gives the second point  $A$  ( $OA = V_{CC}/R_C$ ) on the collector current axis as shown in Fig. 8.35 (ii). By joining these two points, d.c. \*load line  $AB$  is constructed.

**Importance.** The current ( $I_C$ ) and voltage ( $V_{CE}$ ) conditions in the transistor circuit are represented by some point on the output characteristics. The same information can be obtained from the load line. Thus when  $I_C$  is maximum ( $= V_{CC}/R_C$ ), then  $V_{CE} = 0$  as shown in Fig. 8.36. If  $I_C = 0$ , then  $V_{CE}$  is maximum and is equal to  $V_{CC}$ . For any other value of collector current say  $OC$ , the collector-emitter voltage  $V_{CE} = OD$ . It follows, therefore, that load line gives a far more convenient and direct solution to the problem.


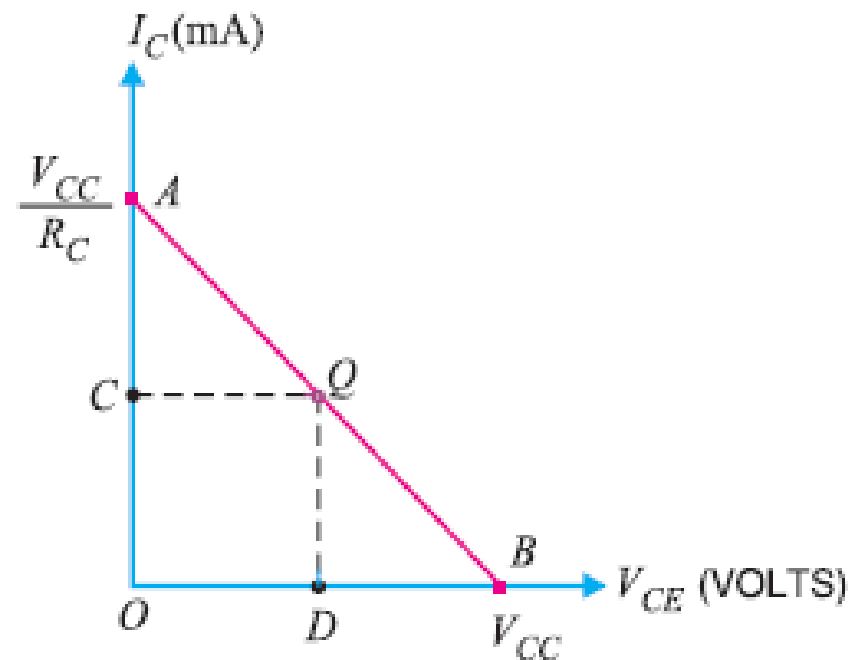


Fig. 8.36
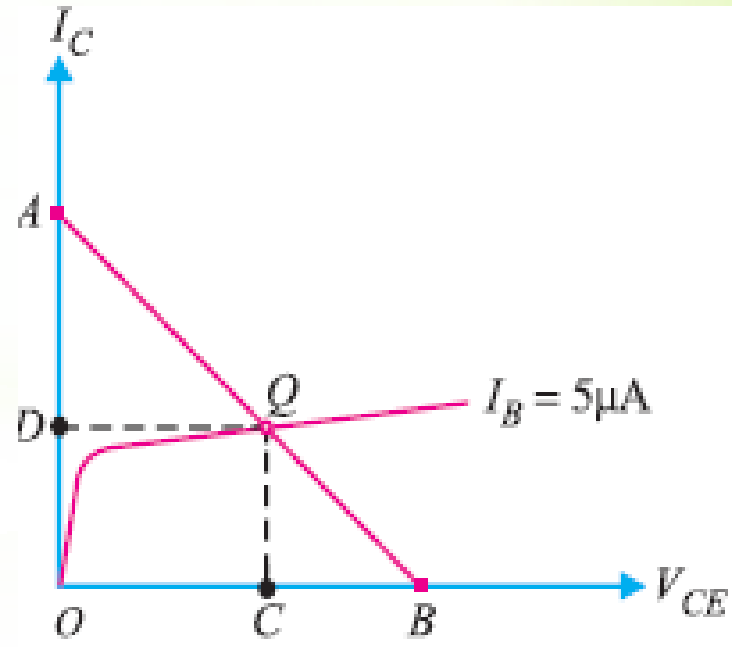
# Operating Point

The zero signal values of  $I_C$  and  $V_{CE}$  are known as the operating point.


It is also called quiescent (silent) point or Q-point because it is the point on  $I_C - V_{CE}$  characteristic when the transistor is silent i.e. in the absence of the signal.





P1

**Example 8.22.** For the circuit shown in Fig. 8.38 (i), draw the d.c. load line.

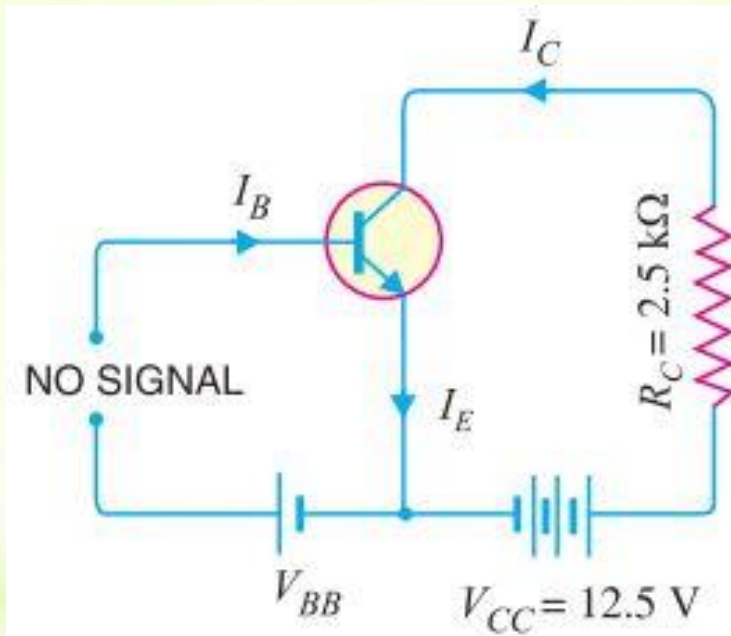

**Example 8.22.** For the circuit shown in Fig. 8.38 (i), draw the d.c. load line.



**Solution.** The collector-emitter voltage  $V_{CE}$  is given by ;

$$V_{CE} = V_{CC} - I_C R_C$$

When  $I_C = 0$ , then,

$$V_{CE} = V_{CC} = 12.5 \text{ V}$$

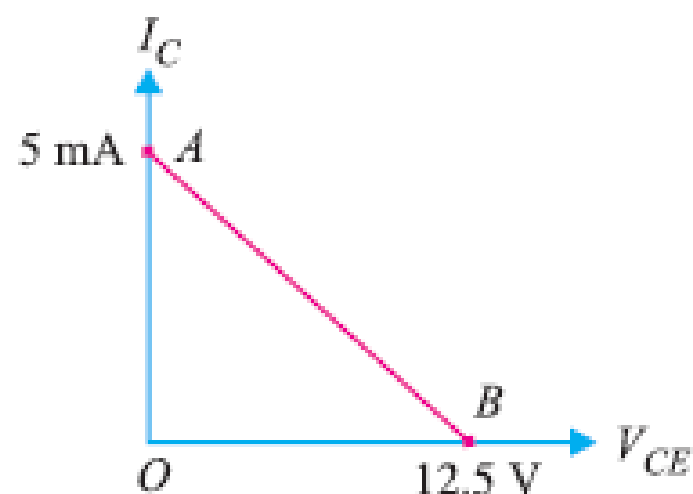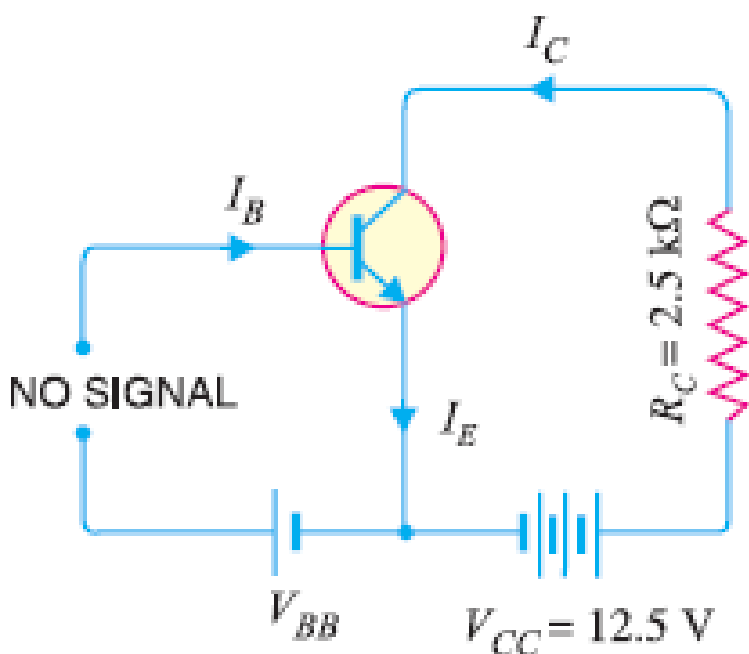This locates the point  $B$  of the load line on the collector-emitter voltage axis.




When  $V_{CE} = 0$ , then,

$$I_C = V_{CC}/R_C = 12.5 \text{ V}/2.5 \text{ k}\Omega = 5 \text{ mA}$$

This locates the point  $A$  of the load line on the collector current axis. By joining these two points, we get the d.c. load line  $AB$  as shown in Fig. 8.38 (ii).

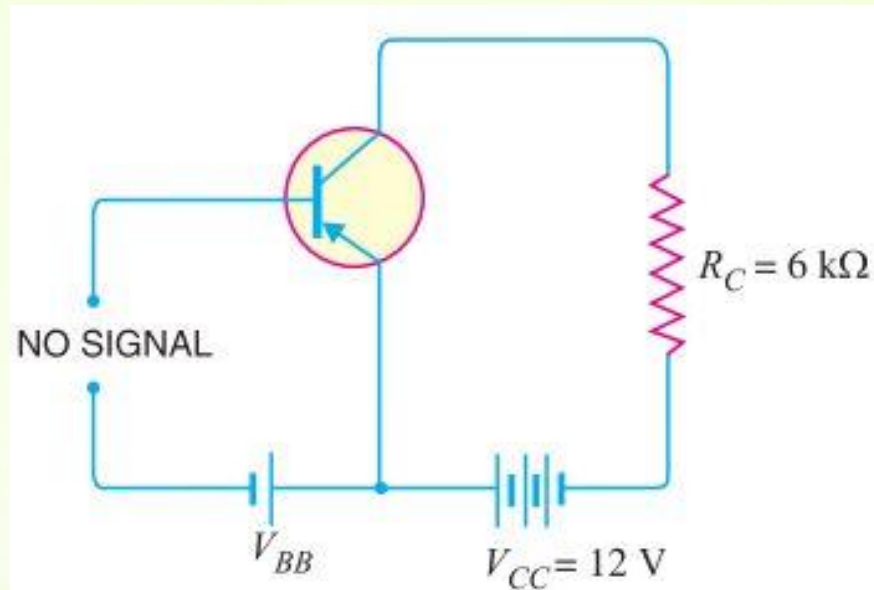**Example 8.23.** In the circuit diagram shown in Fig. 8.39 (i), if  $V_{CC} = 12V$  and  $R_C = 6\text{ k}\Omega$ , draw the d.c. load line. What will be the Q point if zero signal base current is  $20\mu A$  and  $\beta = 50$  ?





**Example 8.23.** In the circuit diagram shown in Fig. 8.39 (i), if  $V_{CC} = 12\text{ V}$  and  $R_C = 6\text{ k}\Omega$ , draw the d.c. load line. What will be the  $Q$  point if zero signal base current is  $20\mu\text{A}$  and  $\beta = 50$ ?

**Solution.** The collector-emitter voltage  $V_{CE}$  is given by :



$$V_{CE} = V_{CC} - I_C R_C$$

When  $I_C = 0$ ,  $V_{CE} = V_{CC} = 12\text{ V}$ . This locates the point  $B$  of the load line. When  $V_{CE} = 0$ ,  $I_C = V_{CC}/R_C = 12\text{ V}/6\text{ k}\Omega = 2\text{ mA}$ . This locates the point  $A$  of the load line. By joining these two points, load line  $AB$  is constructed as shown in Fig. 8.39 (ii).

Zero signal base current,  $I_B = 20\mu\text{A} = 0.02\text{ mA}$

Current amplification factor,  $\beta = 50$

$\therefore$  Zero signal collector current,  $I_C = \beta I_B = 50 \times 0.02 = 1\text{ mA}$

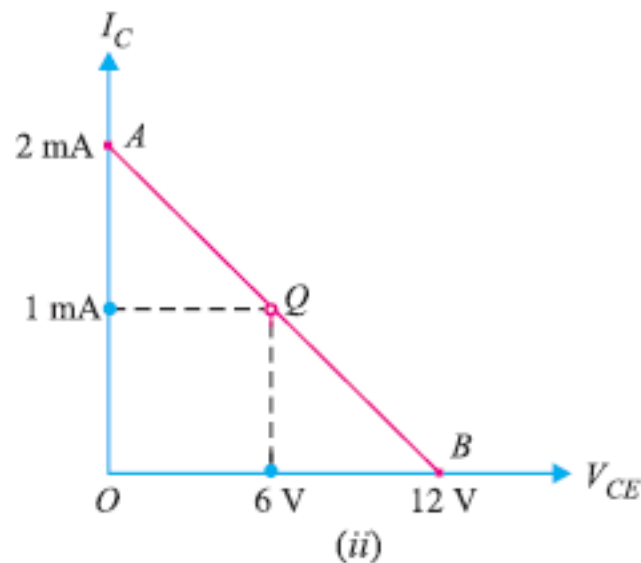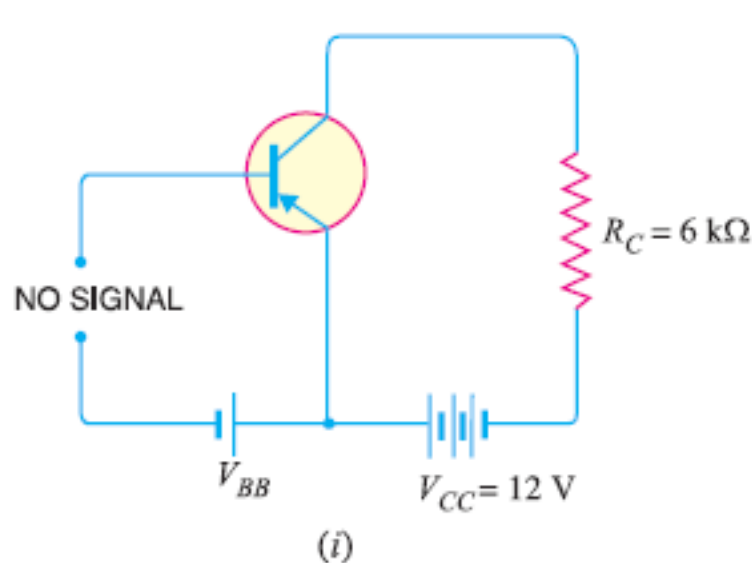

**Fig. 8.39**

Zero signal collector-emitter voltage is

$$V_{CE} = V_{CC} - I_C R_C = 12 - 1\text{ mA} \times 6\text{ k}\Omega = 6\text{ V}$$

$\therefore$  Operating point is **6 V, 1 mA**.

Fig. 8.39 (ii) shows the  $Q$  point. Its co-ordinates are  $I_C = 1\text{ mA}$  and  $V_{CE} = 6\text{ V}$ .

**Example 8.24.** *In a transistor circuit, collector load is  $4\text{ k}\Omega$  whereas quiescent current (zero signal collector current) is  $1\text{mA}$ .*

- (i) What is the operating point if  $V_{CC} = 10\text{ V}$  ?*
- (ii) What will be the operating point if  $R_C = 5\text{ k}\Omega$  ?*

**Example 8.24.** In a transistor circuit, collector load is  $4\text{ k}\Omega$  whereas quiescent current (zero signal collector current) is  $1\text{ mA}$ .

- (i) What is the operating point if  $V_{CC} = 10\text{ V}$ ?
- (ii) What will be the operating point if  $R_C = 5\text{ k}\Omega$ ?

**Solution.**

$$V_{CC} = 10\text{ V}, I_C = 1\text{ mA}$$

- (i) When collector load  $R_C = 4\text{ k}\Omega$ , then,

$$V_{CE} = V_{CC} - I_C R_C = 10 - 1\text{ mA} \times 4\text{ k}\Omega = 10 - 4 = 6\text{ V}$$

$\therefore$  Operating point is **6 V, 1 mA**.

- (ii) When collector load  $R_C = 5\text{ k}\Omega$ , then,

$$V_{CE} = V_{CC} - I_C R_C = 10 - 1\text{ mA} \times 5\text{ k}\Omega = 10 - 5 = 5\text{ V}$$

$\therefore$  Operating point is **5 V, 1 mA**.

# Thank You All